


Lecture 05: Circuit Solution by Circuit Reduction

Sources Connected in Series and in Parallel :


Both circuits are invalid. Why?

Circuit (a) violates KVL \Rightarrow *ideal* voltage sources cannot be combined in *parallel*
(unless they have the same voltage)

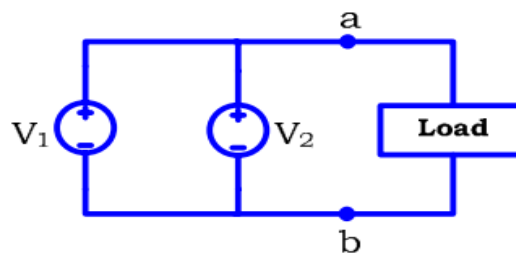Circuit (b) violates KCL \Rightarrow *ideal* current sources cannot be combined in *series*
(unless they have the same current)



(a)

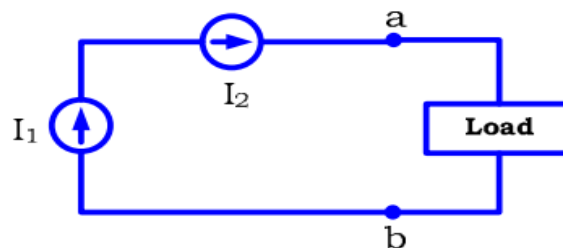

(b)

Figure 1

We can connect ideal voltage sources in *series*.


Voltage sources in *series* can be reduced to a single voltage source

$$V_{eq} = V_1 - V_2 + V_3 + V_4$$


Lecture 05: Circuit Solution by Circuit Reduction

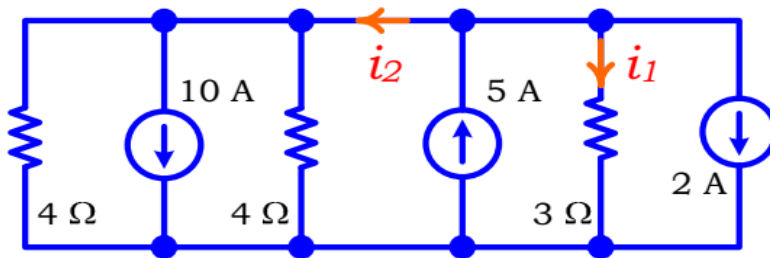Example 1

Determine the currents i_1 and i_2 in the circuit of Fig. ...



(a)

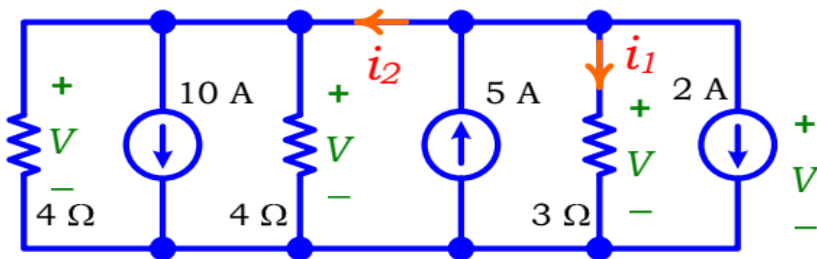

(b)

Solution:

$$V = \frac{-10A + 5A - 2A}{\frac{1}{4}S + \frac{1}{4}S + \frac{1}{3}S}$$

$$= \frac{-7A}{\frac{5}{6}S} = -8.4V$$

Ohm's law gives the currents through the resistors. Current i_1 is labeled with the passive sign convention with respect to voltage V . Hence

$$i_1 = \frac{V}{3\Omega}$$

$$= \frac{-8.4A}{3\Omega} = -2.8A$$

Circuit i_2 is the sum of the currents through the 3 ohm resistor, the 5-A current source, and the 2-A current source. Applying KCL yields:

$$i_2 = 5A - i_1 - 2A = 5.8A$$


This can also be calculated as the sum of the currents through the 4-ohm resistors and the 10-A source:

$$i_2 = \frac{V}{4\Omega} + \frac{V}{4\Omega} + 10 = 5.8A$$

Lecture 05: Circuit Solution by Circuit Reduction

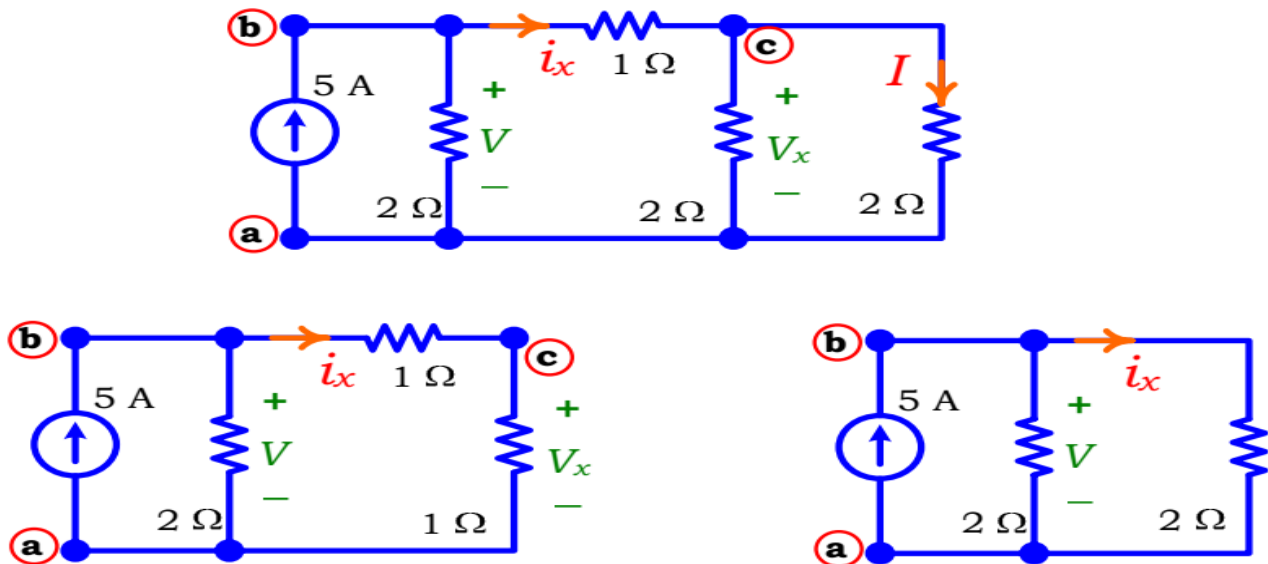Example 2

Determine voltages V and v_x and currents I and i_x in the circuit of Fig. ...



Solution:

Combine the 2 resistors in // (2 ohm resistors) to get a resistor of 1 Ohm. Circuit in step 1. Note that to find the current I which has been lost, we have to come back to the original circuit once we find v_x which remains after circuit reduction. Similarly i_x remains.

Finally add the equivalent resistor to the 1 Ohm series resistor to get 1 + 1 or 2 Ohm resistor, circuit in step2. Note that node c and voltage v_x have disappeared in this reduction, but voltage V remains since it is across the parallel combination. Also current i_x remains. No more reduction is required since we have a single node now and we can therefore determine V as:

$$V = \frac{5A}{\frac{1}{2}\Omega + \frac{1}{2}\Omega} = 5V$$

The current i_x can also be determined using Ohm's law as:

$$i_x = \frac{V}{2\Omega} = \frac{5}{2}A$$

Moving back to Step 1, we determine the voltage v_x using Ohm's law as:

$$v_x = i_x \times 1\Omega = \frac{5}{2}V$$

The current I can now be determined from the original circuit as

$$I = \frac{v_x}{2\Omega} = \frac{5}{4}A$$

Lecture 05: Circuit Solution by Circuit Reduction

Equivalent Resistance of N Resistors in Series:

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{i=1}^N R_i$$

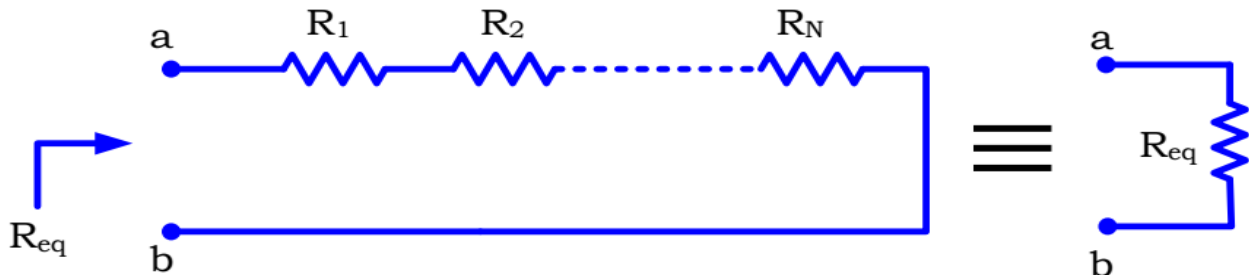


Figure 3

Equivalent Resistance of N Resistors in Parallel:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = \sum_{i=1}^N \frac{1}{R_i}$$

Special Case: If *two* resistors R_1 & R_2 are in parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow R_{eq} = \frac{\text{Product}}{\text{Sum}}$$

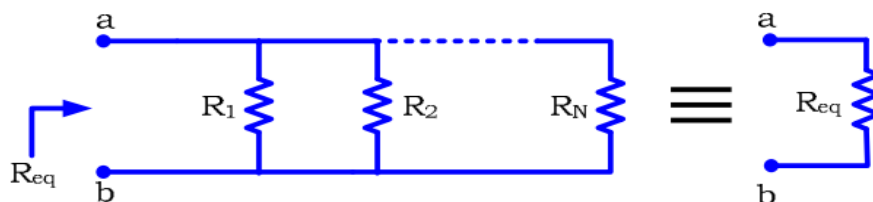


Figure 4

Example 1:

Calculate the equivalent resistance seen to the right of $a-b$.

Lecture 05: Circuit Solution by Circuit Reduction

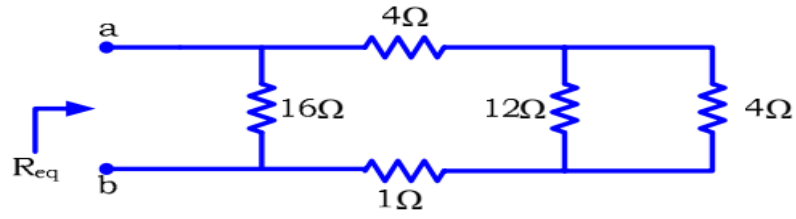


Figure 5

Solution:

$$12\Omega \text{ \& \ } 4\Omega \text{ in parallel} \Rightarrow \frac{12 \times 4}{12 + 4} = \frac{48}{16} = 3\Omega$$

$$4\Omega \text{ \& \ } 3\Omega \text{ \& \ } 1\Omega \text{ in series} \Rightarrow 4 + 3 + 1 = 8\Omega$$

$$16\Omega \text{ \& \ } 8\Omega \text{ in parallel} \Rightarrow \frac{16 \times 8}{16 + 8} = \frac{16 \times 8}{24} = \frac{16}{3} = 5.33\Omega$$

$$\therefore R_{eq} = 5.33\Omega$$

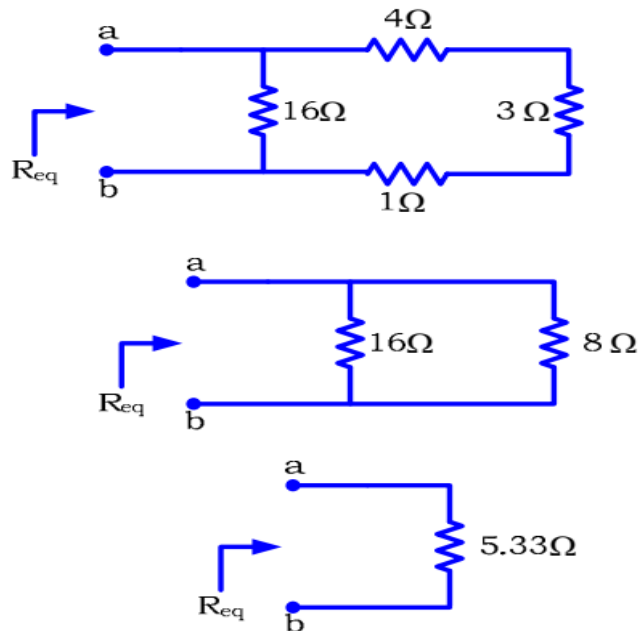


Figure 6

Conductance

The conductance G of a resistor is the reciprocal of the resistance R

$$G = \frac{1}{R}$$

Lecture 05: Circuit Solution by Circuit Reduction

Unit of G is $\frac{1}{\Omega}$ or Semen [S] $\Rightarrow \frac{1}{\Omega} \equiv S$

For N conductances in series

$$\frac{1}{G_{eq}} = \sum_{i=1}^N \frac{1}{G_i}$$

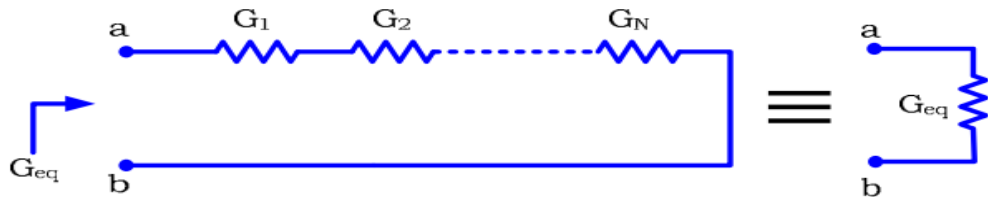


Figure 7

For N conductances in parallel

$$G_{eq} = \sum_{i=1}^N G_i$$

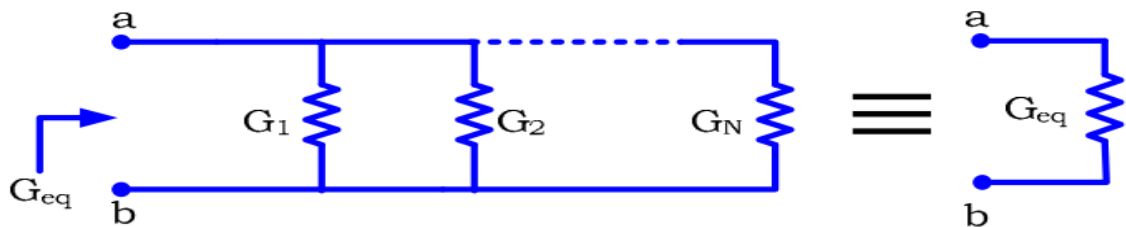


Figure 8

Power absorbed by a resistor:


Using circuit a) $p_R = +iv = +i(iR) = i^2 R = \frac{v^2}{R}$

Using circuit b) $p_R = -iv = -i(-iR) = i^2 R = \frac{v^2}{R}$

$$\therefore p_R = \frac{v^2}{R} = i^2 R \quad (\text{regardless of the direction of } i \text{ and the polarity of } v)$$

$\therefore p_R \geq 0 \Rightarrow$ a resistor *does not generate* electric power, it *always absorbs* it.

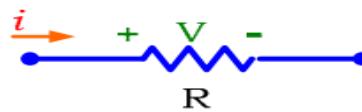Lecture 05: Circuit Solution by Circuit Reduction



(a)



(b)

Figure 9

Example 2:

In the given circuit, calculate:

- G_{eq} seen by the voltage source
- R_{eq}
- the power absorbed by the load

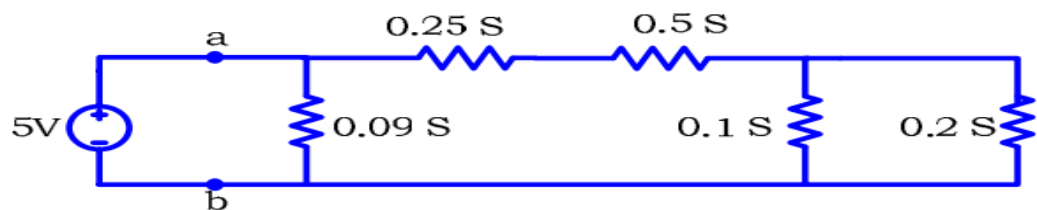


Figure 10

Solution

a)

$$0.1S \text{ \& } 0.2S \text{ (parallel)} \Rightarrow 0.1 + 0.2 = 0.3S$$

$$0.25S \text{ \& } 0.5S \text{ \& } 0.3S \text{ (series)} \Rightarrow \frac{1}{0.25} + \frac{1}{0.5} + \frac{1}{0.3} = 4 + 2 + 3.33 = 9.33 \Rightarrow$$

$$\frac{1}{9.33} = 0.107S$$

$$0.107S \text{ \& } 0.09S \text{ (parallel)} \Rightarrow 0.107 + 0.09 = 0.197S$$

$$\therefore G_{eq} = 0.197S$$

Lecture 05: Circuit Solution by Circuit Reduction

$$\text{b) } R_{eq} = \frac{1}{G_{eq}} = \frac{1}{0.197} = 5.08\Omega$$

$$\text{c) } P_{5.08\Omega} = \frac{v^2}{R} = \frac{(5)^2}{5.08} = 4.97W$$

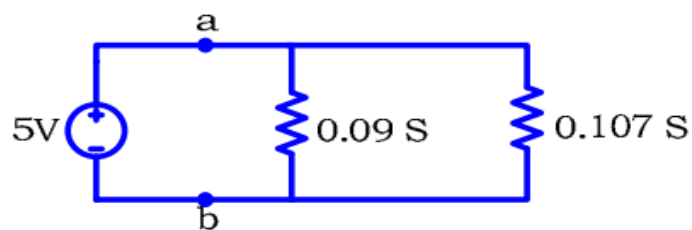
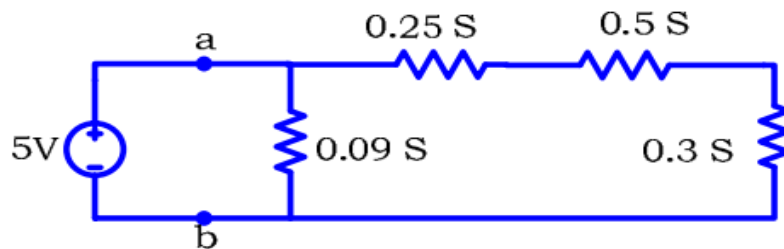


Figure 11

The meaning of the series connection

3Ω & $6V$ are in series.

$10V$ & $5A$ are in series.

4Ω & $20V$ & 5Ω are in series.

Why?

$6V$ & 2Ω are *not* in series.

2Ω & $11V$ are *not* in series.

Why?

Lecture 05: Circuit Solution by Circuit Reduction

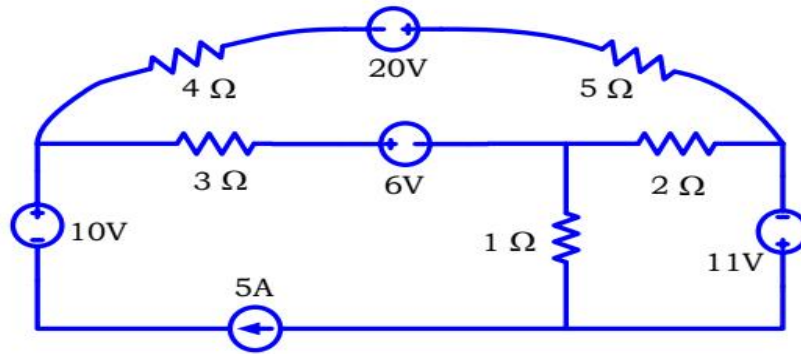


Figure 12

3Ω & $6V$ are in series \Rightarrow the *same current* I_1 passes through them.

$10V$ & $5A$ are in series \Rightarrow the *same current* $5A$ passes through them.

4Ω & $20V$ & 5Ω are in series \Rightarrow the *same current* I_4 passes through them.

$6V$ & 2Ω are *not* in series \Rightarrow *different currents* I_1 & I_3 pass through them.

2Ω & $11V$ are *not* in series. \Rightarrow *different currents* I_3 & I_5 pass through them.

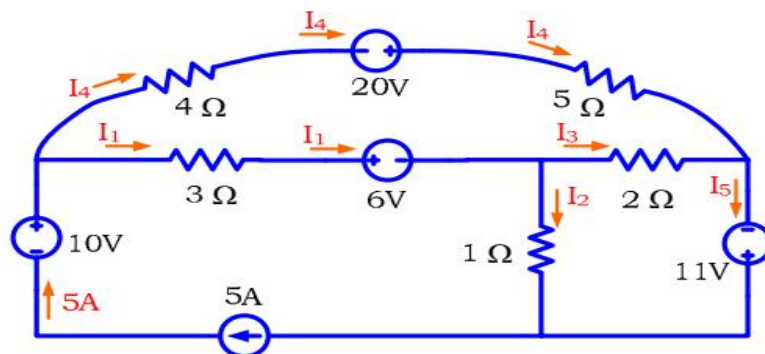


Figure 13

The meaning of the parallel connection

$3A$ & 4Ω are in parallel

6Ω & 8Ω are in parallel

$2V$ & 8Ω are *not* in parallel

Why?

Lecture 05: Circuit Solution by Circuit Reduction

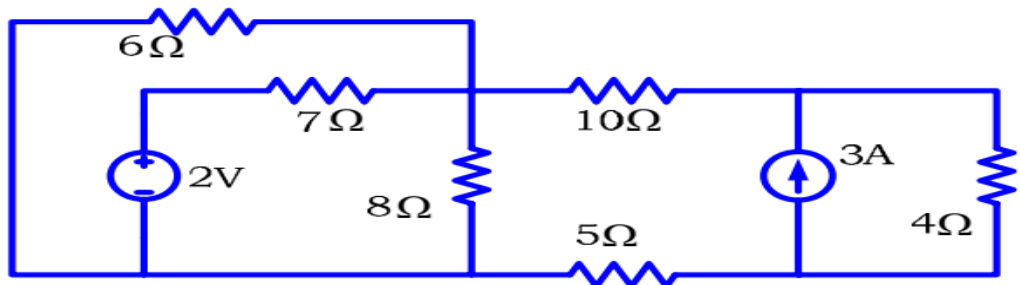


Figure 14

The *same voltage* appears across $3A$ & $4\Omega \Rightarrow$ they are in parallel

The *same voltage* appears across 6Ω & $8\Omega \Rightarrow$ they are in parallel

Different voltages appear across $2V$ & $8\Omega \Rightarrow$ they are *not* in parallel

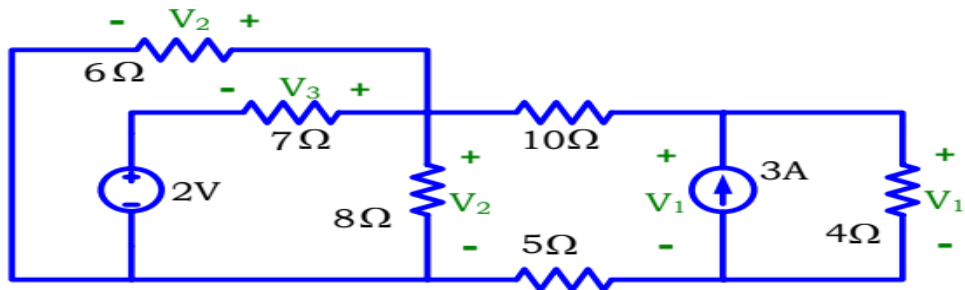


Figure 15

Example 3:

Calculate:

- the power absorbed by the 3Ω resistor
- the *equivalent resistance* seen by the $10V$ voltage source

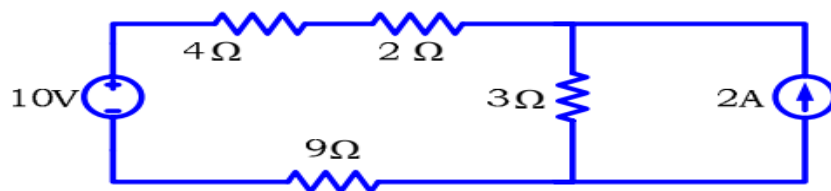


Figure 16

Lecture 05: Circuit Solution by Circuit Reduction

Solution:

a)

2Ω & 4Ω & 9Ω are in series $\Rightarrow 2+4+9=15\Omega$

Define v_1 & v_2 & i_1 & i_2 (*arbitrary choice of voltage polarity and current direction*)

$$\text{KVL} \quad \Rightarrow \quad -10 + v_1 + v_2 = 0$$

$$\text{Ohm's Law} \quad \Rightarrow \quad -10 + 15i_1 + 3i_2 = 0 \quad (1)$$

$$\text{KCL} \quad \Rightarrow \quad i_1 + 3 = i_2 \quad (2)$$

$$\text{Solving (1) \& (2)} \quad \Rightarrow \quad -10 + 15(i_2 - 3) + 3i_2 = 0 \quad \Rightarrow \quad 18i_2 = 55 \quad \Rightarrow$$

$$i_2 = \frac{55}{18} = 3.056A$$

$$\therefore P_{3\Omega} = 3i_2^2 = 3(3.056)^2 = 28.02W$$

b)

$$\text{Using (3)} \quad \Rightarrow \quad i_1 = i_2 - 3 = 3.056 - 3 = 0.056A$$

$$\therefore R_{eq} = +\frac{v}{i_1} = +\frac{10}{0.056} = 178.57\Omega$$

