

Lecture 09: Thevenin Equivalent Circuits

Thevenin Equivalent Circuit:

Given an electrical circuit \Rightarrow split it into circuits A & B

Call circuit B “*the load*”

Notice that circuits A & B are connected by the *two* terminals *a* & *b*

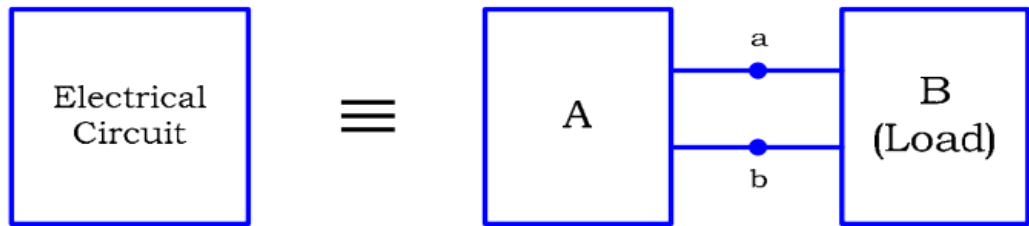


Figure 1

Thevenin theorem:

In general, it is possible to replace circuit A with a voltage source in series with a resistor.

The voltage source is labeled V_{th} (Thevenin voltage)

The resistance is labeled R_{th} (Thevenin resistance)

The new circuit is called the *Thevenin Equivalent Circuit* (TEC) of circuit A

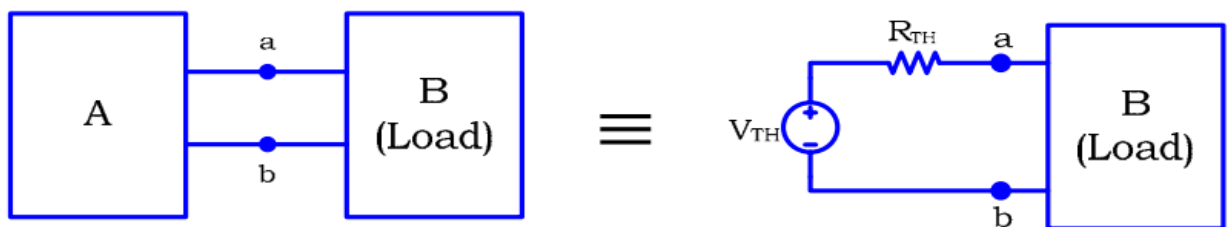


Figure 2

We will consider *four* methods for finding the TEC.

Only two methods will be presented in this class.

Finding the TEC (Method 1):

Lecture 09: Thevenin Equivalent Circuits

Calculate 1) $V_{th} = V_{oc}$ & 2) $R_{th} = \frac{V_{oc}}{i_{sc}}$

1) Calculate V_{th} :

First we remove the load (circuit B)

The terminals a & b become *open-circuited* (no load)

The resulting voltage across the terminals a & b is labeled V_{oc} (Open-circuit voltage)

Current through the *open circuit* is zero \Rightarrow no current flows through R_{th}

$$\text{KVL} \Rightarrow -V_{th} + 0R_{th} + V_{oc} = 0 \Rightarrow V_{th} = V_{oc}$$

We calculate the *open circuit voltage* of circuit A and equate it to V_{th} .



Figure 3

2) Calculate R_{th} using $R_{th} = \frac{V_{oc}}{i_{sc}}$

Remove the load and place a *short circuit* across “ $a - b$ ”

The current that flows in the short circuit is labeled i_{sc}

The voltage across the *short circuit* is zero

$$\text{KVL} \Rightarrow -V_{th} + i_{sc}R_{th} + 0 = 0 \Rightarrow V_{th} = i_{sc}R_{th}$$

$$\therefore R_{th} = \frac{V_{th}}{i_{sc}} \quad [\text{this can be used to calculate } R_{th}]$$



Figure 4

Summary:

Lecture 09: Thevenin Equivalent Circuits

1) Calculate $V_{oc} = V_{th}$

2) Calculate $i_{sc} \Rightarrow$ use $R_{th} = \frac{V_{oc}}{i_{sc}} = \frac{V_{th}}{i_{sc}}$

Example 1:

Calculate the TEC *seen* by the 3Ω resistor.

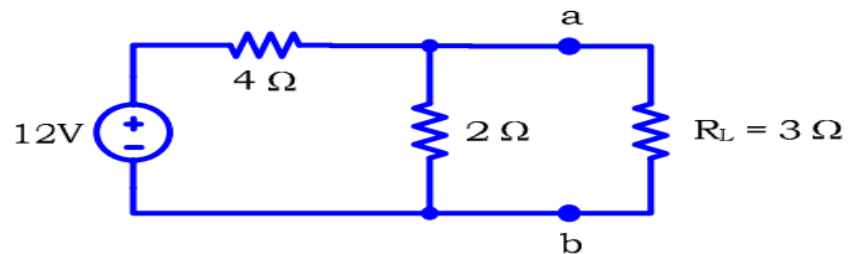


Figure 5

Solution:

Remove the 3Ω load

The voltage V_{oc} is also across the 2Ω resistor

$$\text{VDR} \Rightarrow V_{oc} = \frac{2}{2+4}(12) = 4V$$

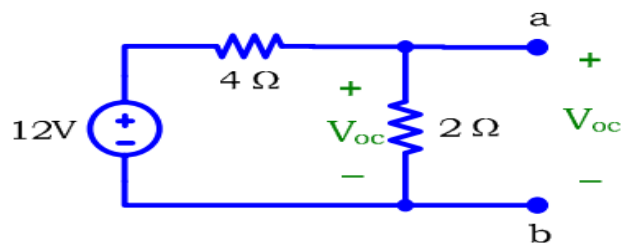


Figure 6

Place a short circuit

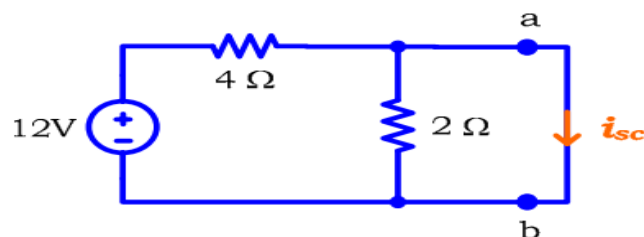


Figure 7

Lecture 09: Thevenin Equivalent Circuits

$$2\Omega \parallel \text{short circuit} \Rightarrow R_{eq} = \frac{0 \times 2}{0 + 2} = 0\Omega \text{ (short circuit)}$$

[A short circuit in parallel with *any resistance* is equivalent to a short circuit]

$$\therefore i_{sc} = \frac{12}{4} = 3A$$

$$\therefore R_{eq} = \frac{V_{oc}}{i_{sc}} = \frac{4}{3} = 1.333\Omega$$

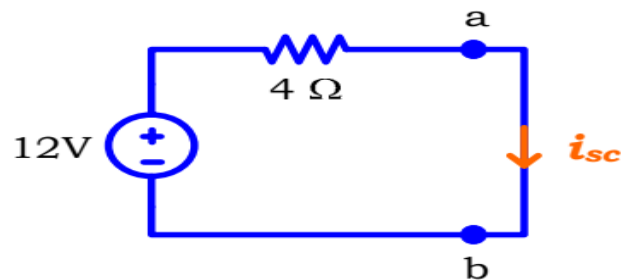


Figure 8

\therefore the TEC seen by the 3Ω resistance is:

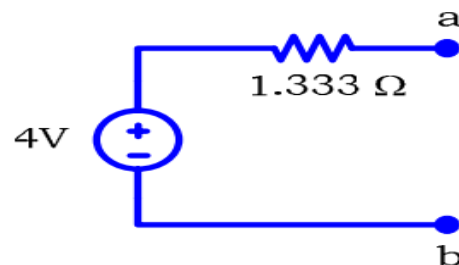


Figure 9

Example 2:

Calculate the TEC to the left of “ $a - b$ ” [load has already been removed].

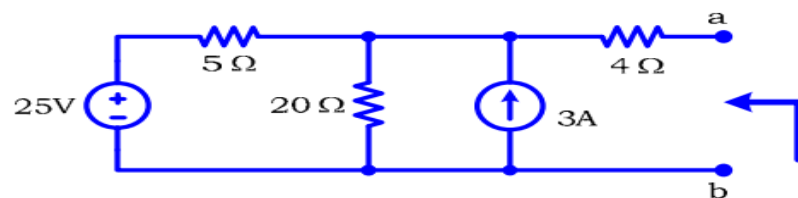


Figure 10

The current through the 4Ω resistor is zero, because of the open circuit.

Lecture 09: Thevenin Equivalent Circuits

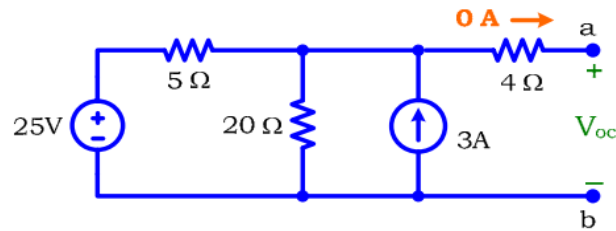


Figure 11

Voltage drop across 4Ω is zero (why?)

KVL \Rightarrow Voltage across the $3A$ & 20Ω is V_{oc}

We can calculate V_{oc} by any method we choose, let us use KVL, KCL & Ohm's law.

[Also, the mesh analysis is *efficient* in this case, because we have only *one actual* unknown. Why?].

The $3A$ current completely goes to the left (why?)

Assume current i through 5Ω

KCL \Rightarrow current through 20Ω is $(i+3)$

$$\text{KVL} \Rightarrow -25 + 5i + 20(i+3) = 0 \Rightarrow i = -\frac{7}{5}A$$

$$\text{Ohm's law} \Rightarrow V_{oc} = 20(i+3) = 20\left(-\frac{7}{5} + 3\right) = 32V$$

$$\therefore V_{th} = V_{oc} = 32V$$

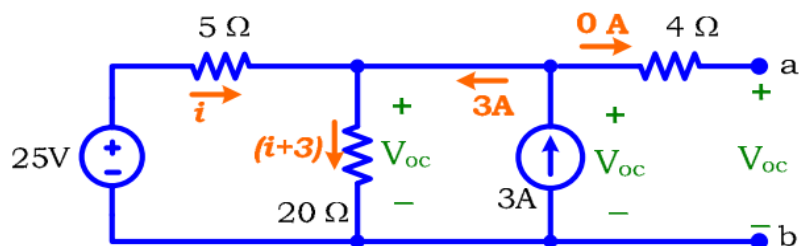


Figure 12

Place a short circuit across “ $a-b$ ”

We can calculate i_{sc} by any method we choose

Let us use the NA

Lecture 09: Thevenin Equivalent Circuits

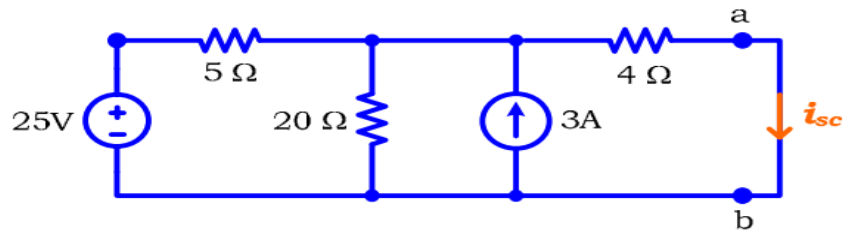


Figure 13

Using the reference node as shown \Rightarrow only V_2 is unknown.

$$\text{KCL at node 2} \Rightarrow \frac{V_2 - 25}{5} + \frac{V_2}{20} - 3 + \frac{V_2 - 0}{4} = 0 \Rightarrow V_2 = 16V$$

$$\therefore i_{sc} = \frac{V_2 - 0}{4} = \frac{16}{4} = 4A$$

$$\therefore R_{eq} = \frac{V_{oc}}{i_{sc}} = \frac{32}{4} = 8\Omega$$

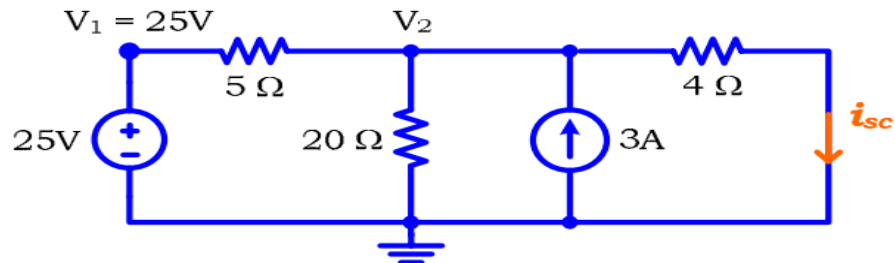


Figure 14

The resulting TEC is:

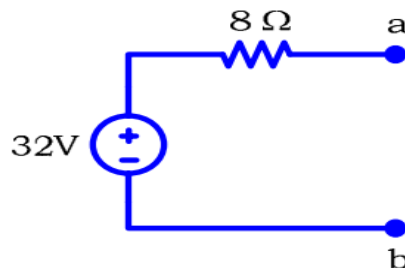


Figure 15

Finding the TEC (Method 2):

We can also use ST to find the TEC. This is the second method.

Example 3:

Repeat the previous example using ST to find the TEC.

Lecture 09: Thevenin Equivalent Circuits

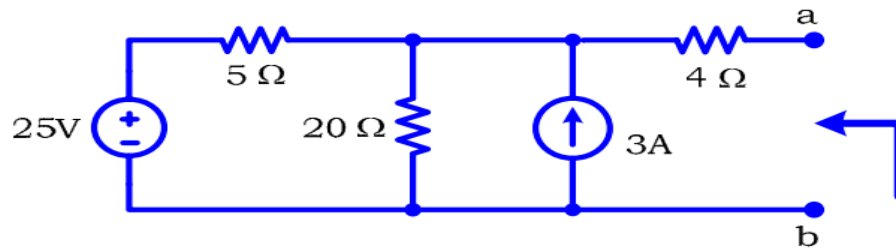


Figure 10

Solution:

$$ST \Rightarrow I = \frac{25}{5} = 5A$$

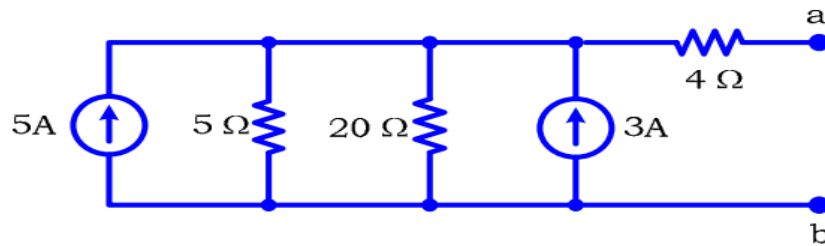


Figure 16

$$3A \parallel 5A \Rightarrow 8A$$

$$5\Omega \parallel 20\Omega \Rightarrow \frac{5 \times 20}{5 + 20} = \frac{100}{25} = 4\Omega$$

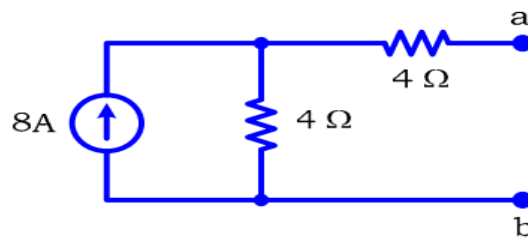


Figure 17

$$ST \Rightarrow V = 8 \times 4 = 32V$$

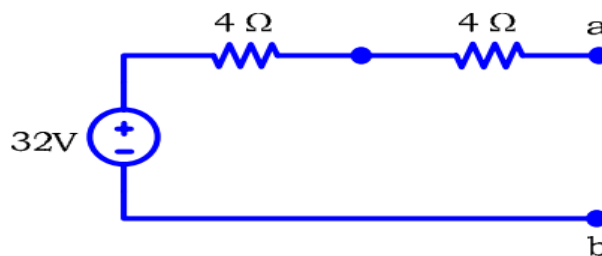


Figure 18

Lecture 09: Thevenin Equivalent Circuits

$$4 + 4 = 8\Omega$$

The circuit is reduced to a voltage source in series with a resistor.

$$\therefore V_{th} = 32V \quad \& \quad R_{th} = 8\Omega$$

Same answer as before.

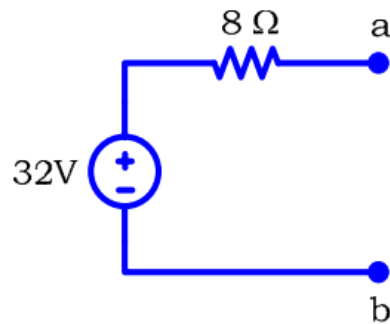


Figure 19

Using ST, we are able to find V_{th} & R_{th} *simultaneously*.

Methods 1 & 2 are *not always* applicable. They have certain limitations.

In the coming classes, we will present the *other two* methods for finding the TEC and also discuss the *limitations* and *advantages* of the *four* methods.