

Lecture 08: Superposition

The Superposition Principle:

Consider a multi-input multi-output general circuit.

The inputs $S_1, S_2, S_3, \dots, S_N$ represent either *independent* voltage or current sources

The outputs $O_1, O_2, O_3, \dots, O_M$ represent the remaining voltages and currents

For instance, O_1 may be current through a resistor, and O_2 may be voltage across a current source

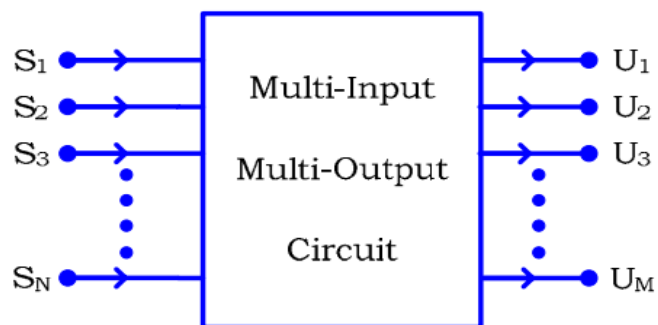


Figure 1

For simplicity, let us consider a *single-output* circuit, with one output quantity, U

All the inputs $S_1, S_2, S_3, \dots, S_N$ affect the output U

In other words, U has *some contribution* from *each* of the sources $S_1, S_2, S_3, \dots, S_N$

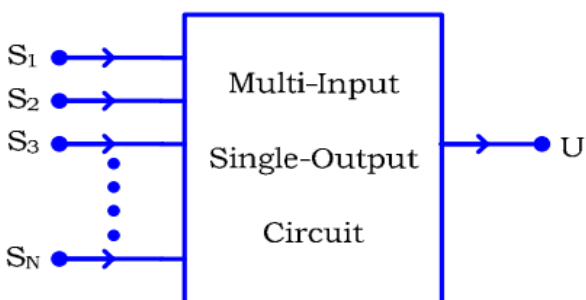


Figure 2

The contribution of S_1 to U is labeled U_1

The contribution of S_2 to U is labeled U_2

Lecture 08: Superposition

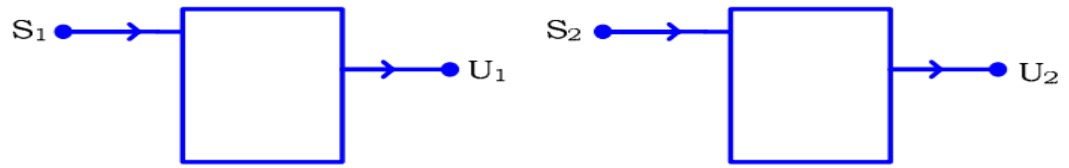


Figure 3

In general, the contribution of S_i to U is labeled U_i

⇓

$$U = U_1 + U_2 + U_3 + \dots + U_N$$

This is called the *Superposition Principle*.

This principle is valid for *linear circuits only*.

All the circuits covered in this course are linear circuits.

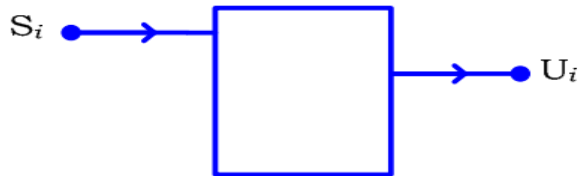


Figure 4

The output U may be *current or voltage*, but it *cannot be power or energy*.

Thus, the SP principle *applies* to currents and voltages, but it *does not* apply to power or energy.

To calculate $U_1 \Rightarrow$ set *all independent* sources to zero except S_1

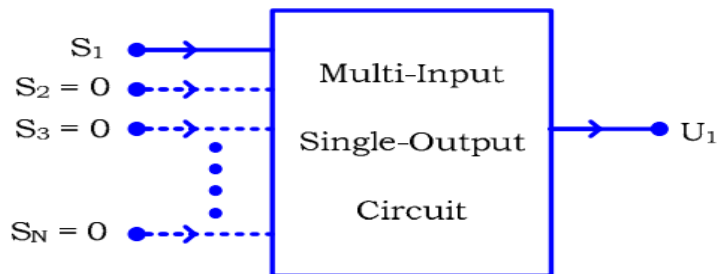


Figure 5

To calculate $U_2 \Rightarrow$ set *all independent* sources to zero except S_2

Lecture 08: Superposition

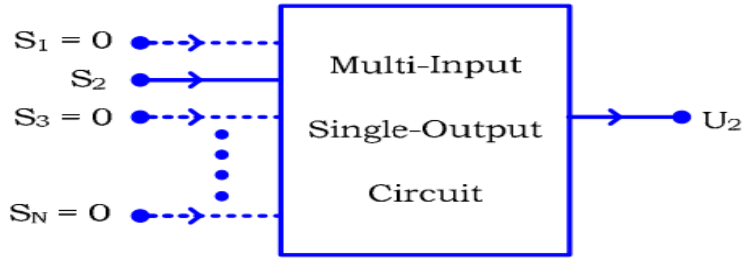


Figure 6

To calculate $U_i \Rightarrow$ set all independent sources to zero except S_i

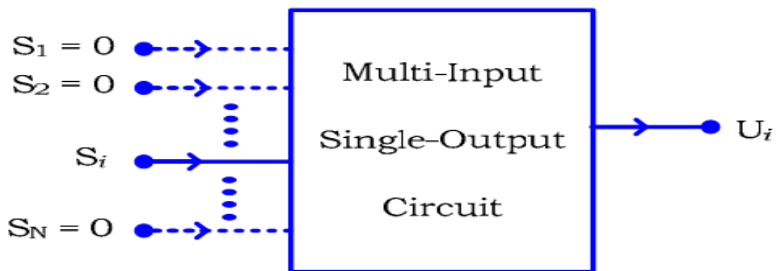


Figure 7

To set a voltage source to zero \Rightarrow replace it with a short circuit

To set a current source to zero \Rightarrow replace it with an open circuit

Extension of SP to multi-output circuits is straightforward.

Example 1:

Calculate I using SP.

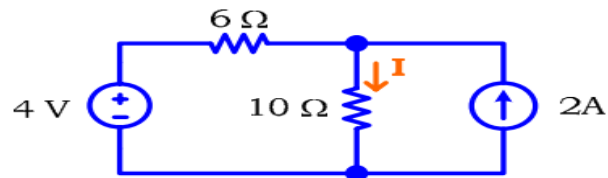


Figure 8

Solution:

First calculate $I' = I|_{4V}$ (current I due to only the $4V$ source)

Set the remaining independent sources to zero \Rightarrow replace $2A$ with an open circuit

Lecture 08: Superposition

$$I' = \frac{4}{6+10} = 0.25A$$

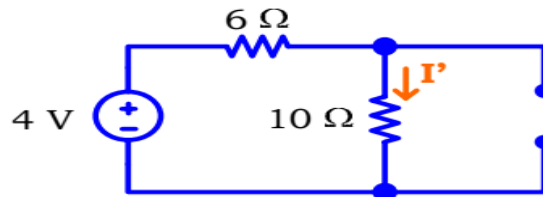


Figure 9

Next calculate $I'' = I|_{2A}$ (current I due to only the 2A source)

Set the remaining independent sources to zero \Rightarrow replace 4V with a short circuit

$$\text{CDR} \Rightarrow I'' = \frac{6}{6+10} \times 2 = \frac{12}{16} = 0.75A$$

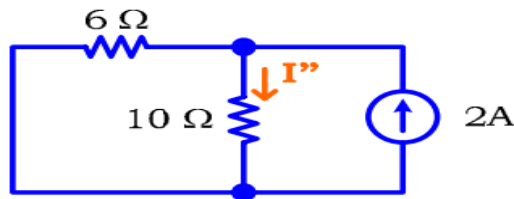


Figure 10

$$\therefore I = I' + I'' = 0.25 + 0.75 = 1.00A$$

Example 2:

Calculate I using SP.

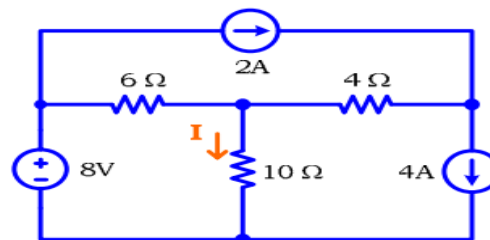


Figure 11

Solution:

$$\text{Calculate: } I' = I|_{8V}$$

Lecture 08: Superposition

$2A$ & $4A \Rightarrow$ replaced by open circuits

Current through 4Ω is zero (why?)

The 4Ω has no effect $\Rightarrow 6\Omega$ & 10Ω are *in series*

$$\therefore I' = \frac{8}{6+10} = 0.5A$$

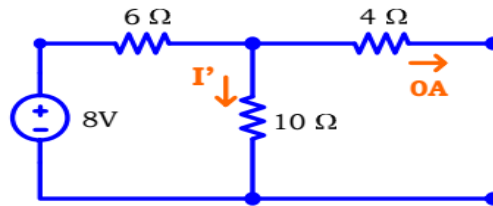


Figure 12

Next calculate: $I' = I|_{4A}$

$8V \Rightarrow$ replaced by a short circuit

$2A \Rightarrow$ replaced by an open circuit

4Ω *in series* with $4A \Rightarrow$ equivalent to $4A$

$$\text{CDR} \Rightarrow I'' = -\frac{6}{6+10} \times 4 = -1.5A$$

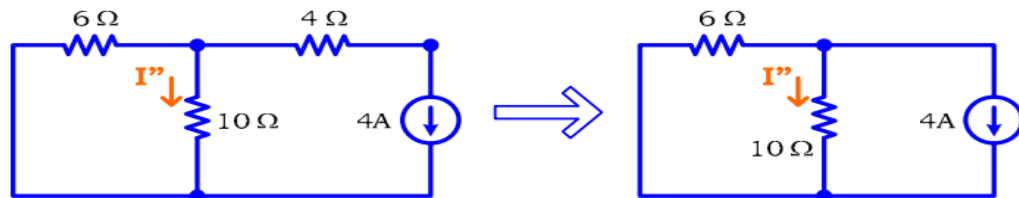


Figure 13

Finally calculate: $I''' = I|_{2A}$

$8V \Rightarrow$ replaced by a short circuit

$4A \Rightarrow$ replaced by an open circuit

4Ω *in series* with $2A \Rightarrow$ equivalent to $2A$

$$\text{CDR} \Rightarrow I''' = \frac{6}{6+10} \times 2 = 0.75A$$

Lecture 08: Superposition

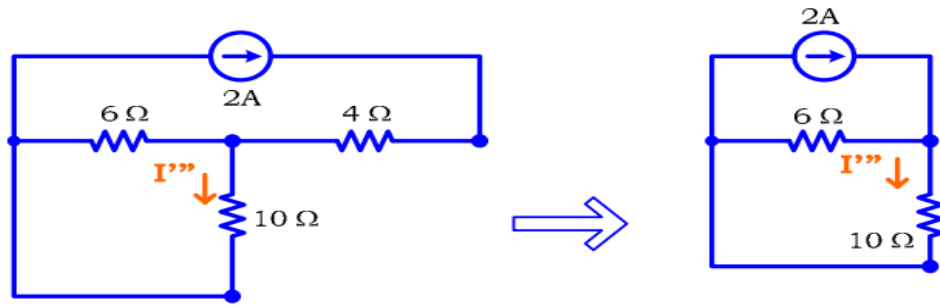


Figure 14

$$\therefore I = I' + I'' + I''' = (0.5) + (-1.5) + (0.75) = -0.25 A$$

Example 3:

Calculate:

- $P' = P_{5\Omega} |_{8V}$ (Power absorbed by the 5Ω resistor due only the $8V$ source)
- $P'' = P_{5\Omega} |_{10V}$ (Power absorbed by the 5Ω resistor due only the $10V$ source)
- Show that $P \neq P' + P''$

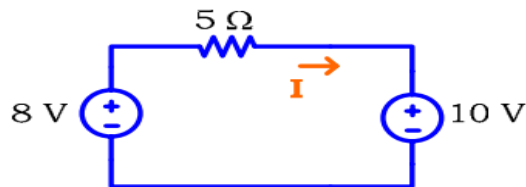


Figure 20

Solution:

$$\text{a) } I' = \frac{8}{5} = 1.6 A \quad \Rightarrow \quad P' = (1.6)^2 5 = 12.8 W$$

$$\text{b) } I'' = -\frac{10}{5} = -2 A \quad \Rightarrow \quad P'' = (-2)^2 5 = 20 W$$

$$\text{c) } I = I' + I'' = 1.6 - 2 = -0.4 A \quad \Rightarrow \quad P = (-0.4)^2 5 = 0.8 W$$

$$P' + P'' = 12.8 + 20 = 32.8$$

Lecture 08: Superposition

$$\therefore P \neq P' + P''$$

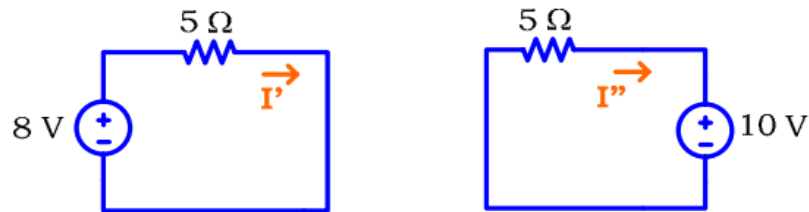


Figure 21

Therefore, for power calculation, we can use SP to calculate *total* currents and voltages, from which we can calculate the power.

From the previous examples we can draw the following conclusions:

- 1- The number of partial-circuits *equals* the number of *independent* sources.
- 2- The *algebraic sign* of the unknown *must be* accounted for.
- 3- The voltage *polarity* and the current *direction* remain the *same* in *all* partial-circuits.
- 4- *Dependent* sources are *never* set to zero.
- 5- SP is *not* applicable to Power (or to energy).