

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL

The Voltage Divider Rule (VDR)

The total voltage across the *series* resistors R_1, R_2, \dots, R_N is V .

$$i = \frac{V}{R_{eq}} = \frac{V}{\sum_{i=1}^N R_i}$$

$$v_x = iR_x = \frac{V}{\sum_{i=1}^N R_i} R_x = \left(\frac{R_x}{\sum_{i=1}^N R_i} \right) V$$

$$\text{VDR} \Rightarrow v_x = \left(\frac{R_x}{\sum_{i=1}^N R_i} \right) V$$

$$\text{VDR} \Rightarrow v_{resistor} = \frac{\text{resistor}}{\text{sum}} \times (\text{total voltage})$$

The VDR is valid for *any* number of resistors in *series*.

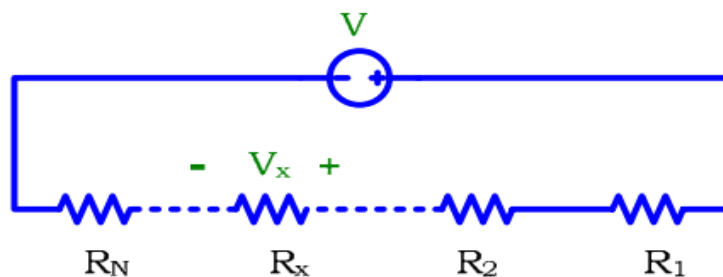


Figure 10

Example 3:

Calculate v_1 & v_2

$$\text{VDR} \Rightarrow v_1 = \frac{4}{4+6} \times 30 = 12V$$

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL

$$\text{VDR} \Rightarrow v_2 = \frac{6}{4+6} \times 30 = 18V$$

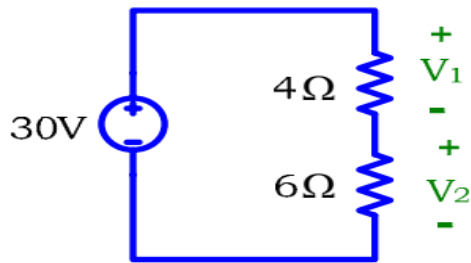


Figure 11

VDR \Rightarrow Higher voltage drop across the *higher* resistance.

Example 4:

Calculate the unknown voltages.

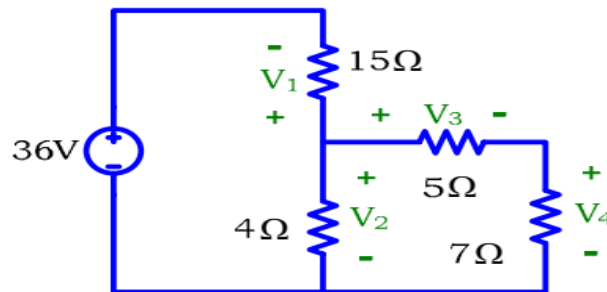


Figure 12

Solution:

$$5 + 7 = 12\Omega \Rightarrow R_1 = \frac{4 \times 12}{4 + 12} = 3\Omega$$

$$\text{VDR} \Rightarrow v_1 = -\frac{15}{15+3} \times 36 \text{ (a minus sign is required here. Why?)} \Rightarrow v_1 = -30V$$

$$\text{VDR} \Rightarrow v_2 = \frac{3}{15+3} \times 36 \Rightarrow v_2 = 6V$$

$$\text{Check: KVL} \Rightarrow -36 - v_1 + v_2 = -36 - (-30) + (6) = -36 + 30 + 6 = 0$$

$$\text{VDR} \Rightarrow v_3 = \frac{5}{5+7} \times v_2 = \frac{5}{12} \times 6 \Rightarrow v_3 = 2.5V$$

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL

$$\text{VDR} \Rightarrow v_4 = \frac{7}{5+7} \times v_2 = \frac{7}{12} \times 6 \Rightarrow v_4 = 3.5V$$

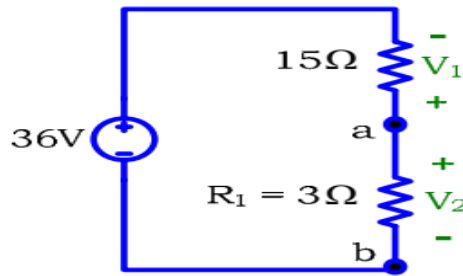
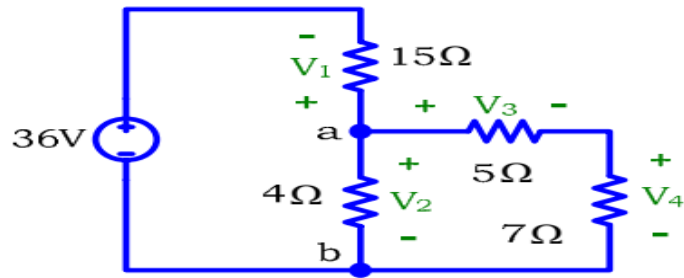


Figure 13

The Current Divider Rule (CDR)

The *total current* entering into the *parallel* combination of R_1 & R_2 is I

$$V = IR_{eq} = I \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1} \quad \& \quad I_2 = \frac{V}{R_2}$$

$$I_1 = \frac{1}{R_1} \times \frac{R_1 R_2}{R_1 + R_2} I \Rightarrow I_1 = \frac{R_2}{R_1 + R_2} I \quad (1)$$

$$\text{Similarly} \Rightarrow I_2 = \frac{R_1}{R_1 + R_2} I \quad (2)$$

$$\text{CDR} \Rightarrow I = \frac{\text{other resistor}}{\text{sum}} \times \text{total current}$$

CDR applies to only *two* resistors in *parallel*.

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL

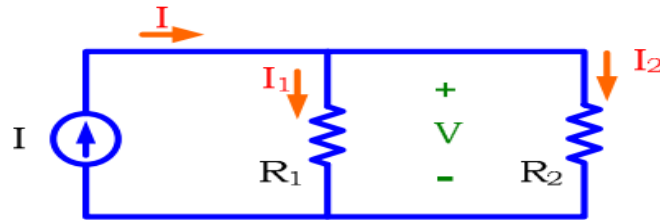


Figure 14

Example 5:

- Use CDR to calculate I_1 & I_2 .
- Verify your results by checking KCL.

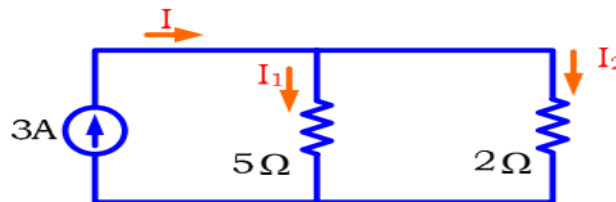


Figure 15

Solution:

a)

$$I_1 = \frac{2}{2+5} \times 3 \Rightarrow I_1 = \frac{6}{7} A$$

$$I_2 = \frac{5}{2+5} \times 3 \Rightarrow I_2 = \frac{15}{7} A$$

b)

$$\text{KCL at node "a"} \Rightarrow I_s - I_1 - I_2 = 3 - \frac{6}{7} - \frac{15}{7} = 3 - \frac{21}{7} = 0 \quad (\text{KCL verified})$$

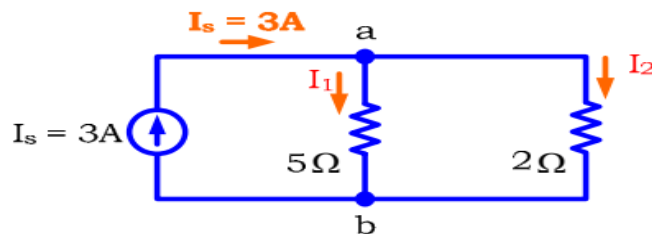


Figure 16

CDR \Rightarrow Higher current passes through the lower resistance.

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL

Example 6:

Use CDR to calculate I_1 , I_2 & I_3 .

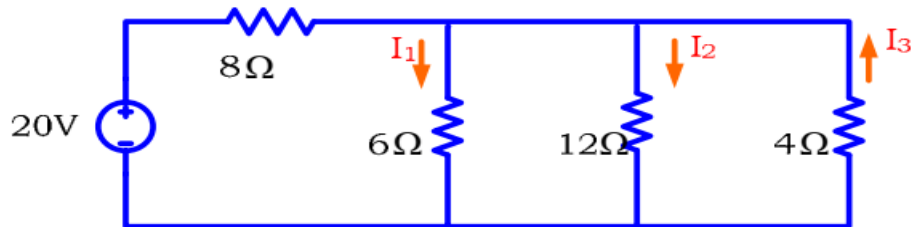


Figure 17

Solution:

$$6\Omega \text{ \& \ } 12\Omega \text{ (in parallel)} \Rightarrow \frac{6 \times 12}{6 + 12} = \frac{72}{18} = 4\Omega$$

$$4\Omega \text{ \& \ } 4\Omega \text{ (in parallel)} \Rightarrow \frac{4 \times 4}{4 + 4} = \frac{16}{8} = 2\Omega$$

$$\therefore R_{eq} = 8 + 2 = 10\Omega$$

$$I = \frac{20}{10} = 2A$$

$$\text{CDR} \Rightarrow I_4 = \frac{4}{4 + 4} \times 2 = 1A$$

$$\text{CDR} \Rightarrow I_3 = -\frac{4}{4 + 4} \times 2 = -1A \quad (\text{the minus sign is necessary in this case. Why?})$$

$$\text{CDR} \Rightarrow I_1 = \frac{12}{6 + 12} \times I_4 \quad (\text{because } I_4 \text{ is the total current through } 6\Omega \text{ \& \ } 12\Omega)$$


$$\therefore I_1 = \frac{12}{18} \times 1 = \frac{2}{3}A$$

$$\text{CDR} \Rightarrow I_2 = \frac{6}{6 + 12} \times 1 = \frac{1}{3}A$$

$$\text{Check KCL at super node} \Rightarrow I - I_1 - I_2 + I_3 = 2 - \frac{2}{3} - \frac{1}{3} + (-1) = 1 - 1 = 0 \quad (\text{KCL verified})$$

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL

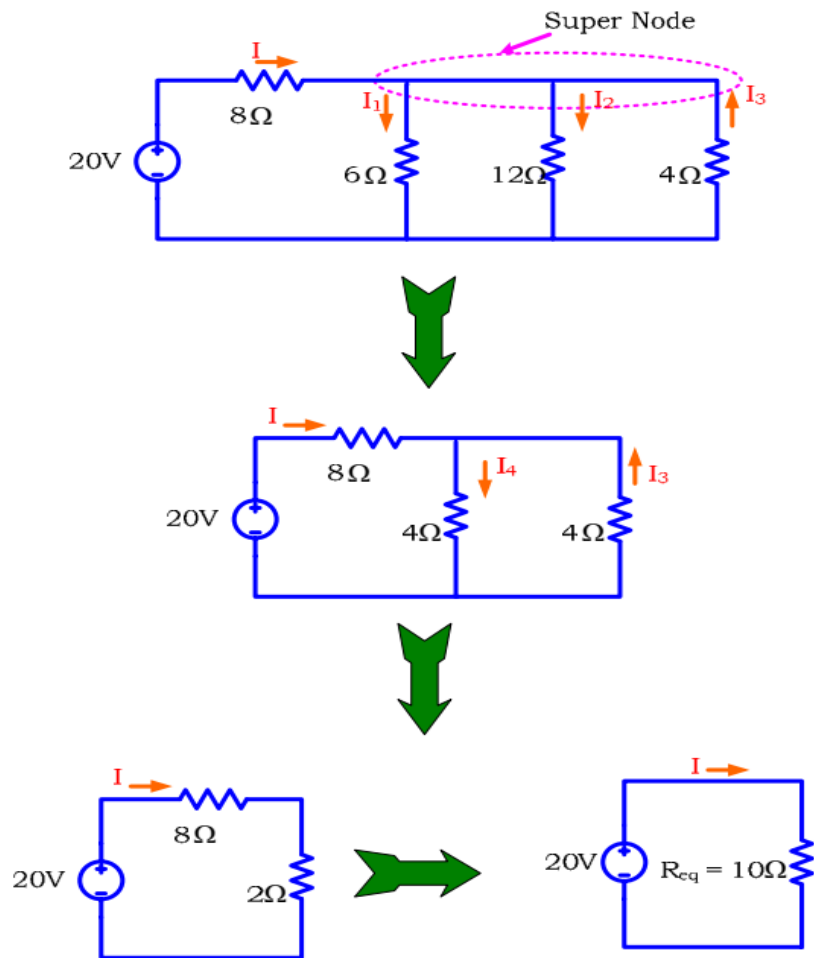Verify that the three *parallel* resistors 6Ω , 12Ω and 4Ω have the *same* voltage.



Solutions for Circuits Containing More than One Source

For Circuit with more than one source, we systematically apply KVL, KCL and Ohm's Law. It is obvious by now that:

- ✚ Currents through elements in series are equal. (Referred to as simple node)
- ✚ Voltages across elements in parallel are equal. (Referred to as simple loop)


Thus

- ✚ Apply KCL only for nonsimple nodes, ie for nodes connecting more than two elements. (Elements not in series).
- ✚ Apply KVL only for nonsimple loops, ie for loops whose elements are not connected at both pairs of nodes. (Elements not in parallel)

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL

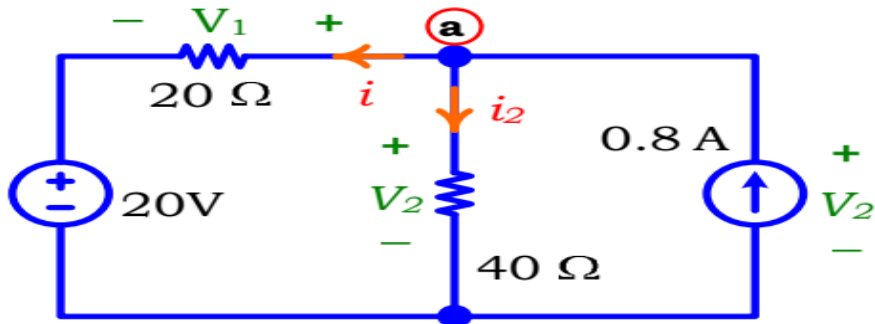Example 8

Determine the current i in the circuit of



Solution:

$$-i_2 - i + \frac{4}{5} = 0$$

$$i_2 = \frac{3}{5} A$$


$$-v_2 + v_1 + 20 = 0$$

$$-(40 \times \frac{3}{5}) + 20i + 20 = 0$$

$$i = \frac{1}{5} A$$

Example 8

Determine the current i in the circuit

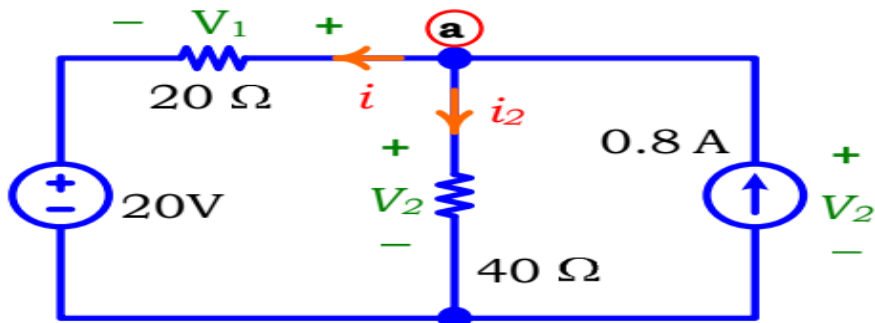

Solution:


$$i = \frac{1}{5} A$$

$$i_2 = \frac{3}{5} A$$

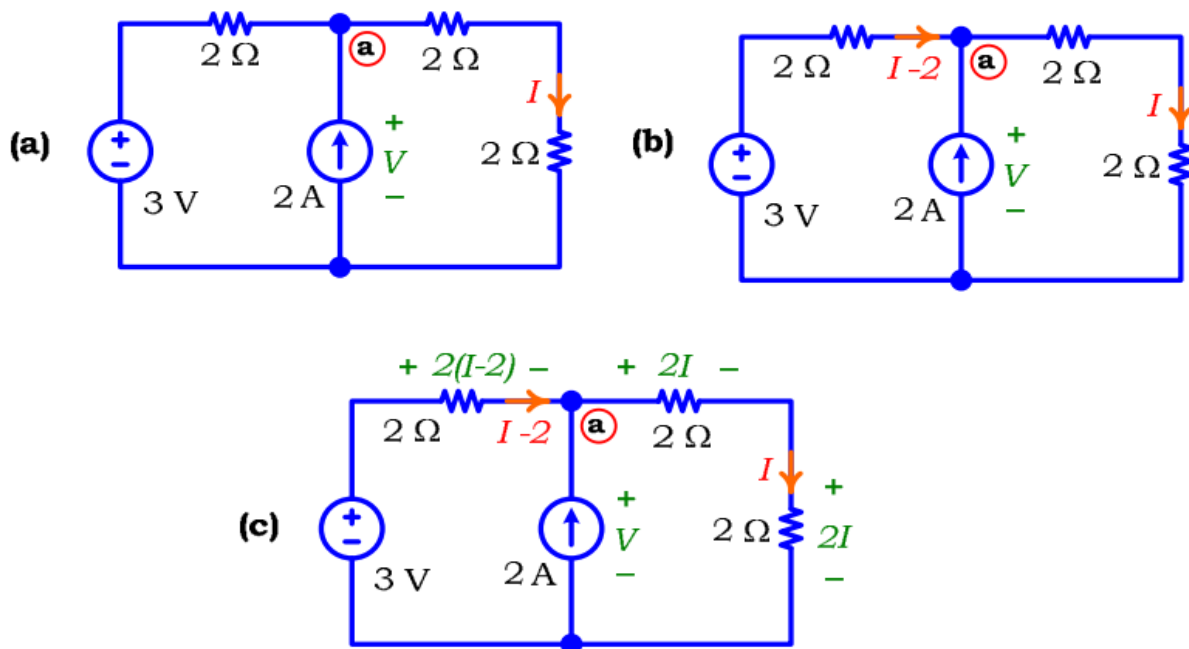Example 9

Determine the voltage V and current I in the circuit

Lecture 06: VDR, CDR & Circuit Solution by KVL and KCL



Solution:

We don't know the voltage or current associated with each resistor, so we cannot apply Ohm's law or KVL. Hence we apply KCL at the single nonsimple node a to obtain the current through the 3-V source in terms of I as I-2 as shown in Fig. Next apply Ohm's law to all resistors (in terms of I) then apply KVL around the outside loop for which we know the voltages across all elements. This yields:

$$-3V = 2(I-2) + 2I + 2I$$

Solving yields:

$$I = \frac{7}{6} A$$

Apply KVL we obtain V:

$$V = 2I + 2I$$

$$V = 3V - 2(I-2)$$

$$V = \frac{14}{3} V$$