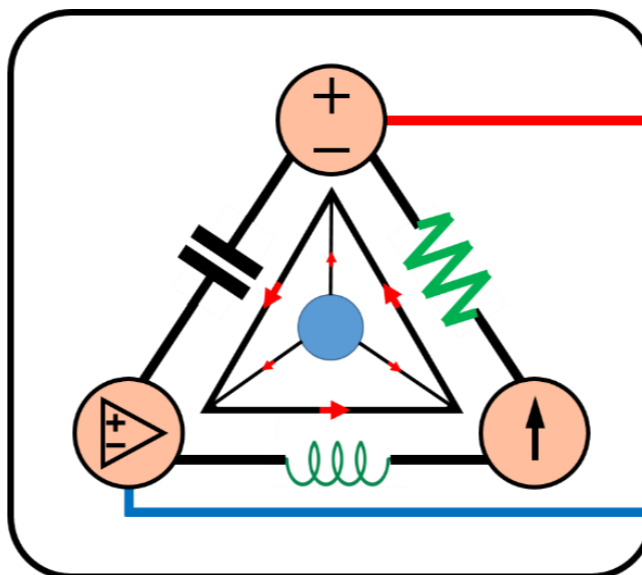


2-Mavzu: Elektr zanjiriga oid asosiy qonunlar.

(Lecture-2: Basic Laws)

2-Mavzuning 1-qismi

(Part 1 of the Lecture-2)



Lecturer: Ph.D., Yusupov Sarvarbek

*Toshkent Kimyo Xalqaro Universiteti
"Mashinasozlik texnologiyasi" kafedrasida
Toshkent shahri, Usmon Nosir, 156-uy.*

2-Mavzu: Elektr zanjiriga oid asosiy qonunlar.

(Lecture-2: Basic Laws)

O'quv rejasi:

- 2.1. Om qonuni.
- 2.2. Tugun, shaxobcha va kontur.
- 2.3. Kirxgof qonunlari.
- 2.4. Ketma-ket ulangan qarshiliklar va kuchlanishni bo'linish qoidasi.
- 2.5. Parallel ulangan qarshiliklar va tok kuchini bo'linish qoidasi.
- 2.6. Qarshiliklar yulduzini qarshiliklar uchburchagiga (Wye-Delta) o'zgartirish.
- 2.7. Qo'llanilishi.

2.1. Om qonuni.

Kuchlanish (V)

U

Kuchlanish potentsiallar farqini ifodalaydi.

$$U = \varphi_1 - \varphi_2$$


Om qonuni - o'tkazgichdan o'tayotgan o'zgarmas tok kuchi bilan uning uchlaridagi potentsiallar farqining o'zaro bog'liqligini ifodalovchi qonundir.

Tok kuchi (A)

I

Qarshilik (Ω) (Om)

R

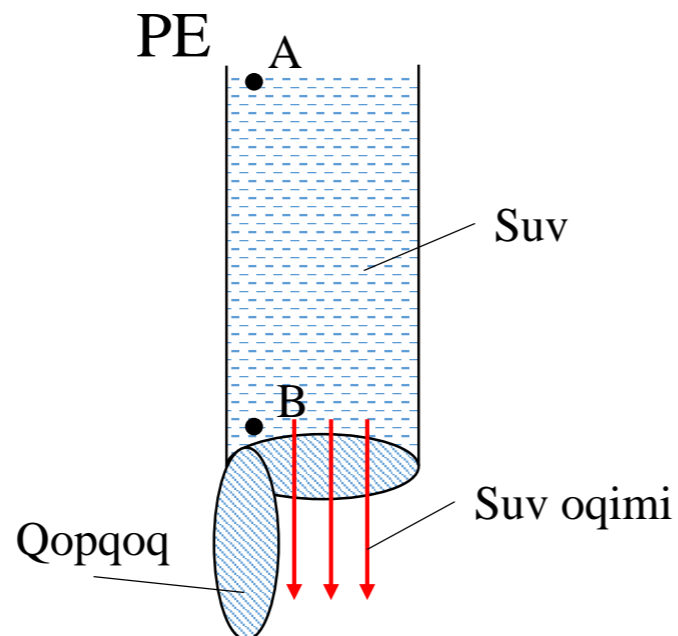

Elektron potentsial nima?

- 1 C zaryadning potentsial energiyasi;
- 1 C zaryadga to'g'ri keluvchi PE.

Tok kuchi (A)

I


Tok kuchi bu – o‘tkazgichning biror nuqtasidan yoki ko‘ndalang kesim yuzasidan 1 sekundda qancha zaryad o‘tishini bildiradi.

$$I = \frac{q}{t}$$

Kuchlanish (V)

U

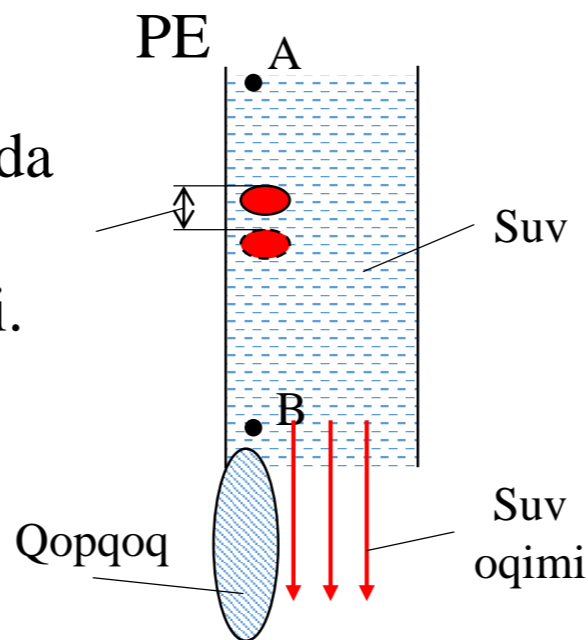t=1 s. Birlik vatq ichida qancha zaryad o‘tkanligini bildiradi.



Qarshilik (Ω) (Om)

R

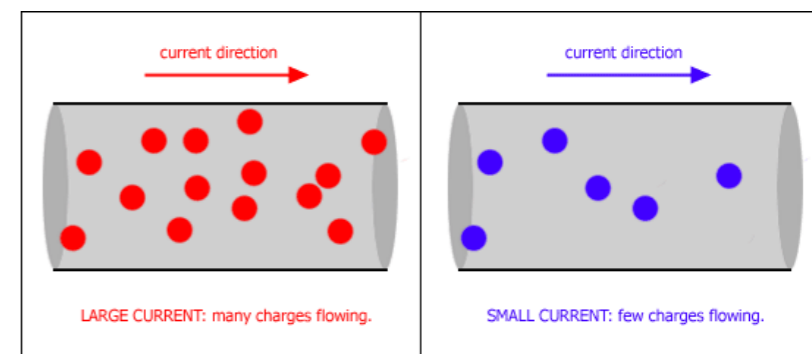



Photo source: [1] - <https://kaiserscience.files.wordpress.com/2016/03/small-vs-large-electrical-current1.gif>

➔ **Qarshilik (Ω) (Om)**

R

Qancha miqdordagi yoki qanday miqdordagi zaryad harakati davomida qarshilikka uchrashi bu elektr qarshiligi deyiladi.

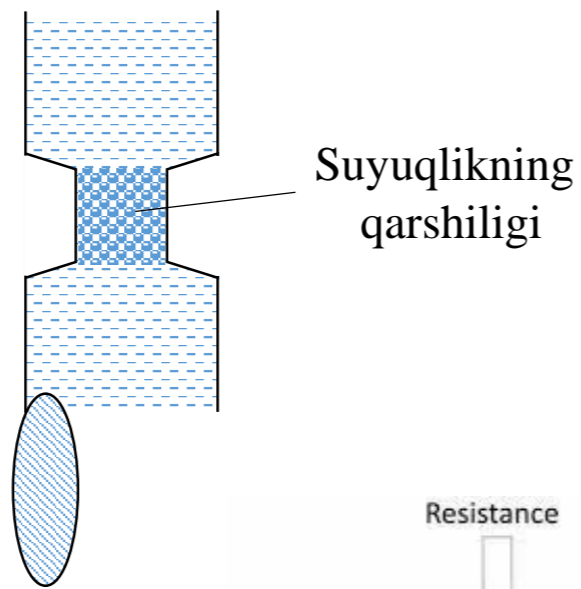➤ Qarshilik bo‘lganligi uchun bir xil vaqtda kamroq suv oqadi.



Kuchlanish (V)

U

Elektr qarshilik tushunchasi:

O‘tkazgichning atomlari tomonidan elektr zayadini tashuvchi zarrachalarga qarshilik ko‘rsatiladi.

➤ Bu jarayon to‘qnashuvlar hisobiga bo‘ladi.

Tok kuchi (A)

I

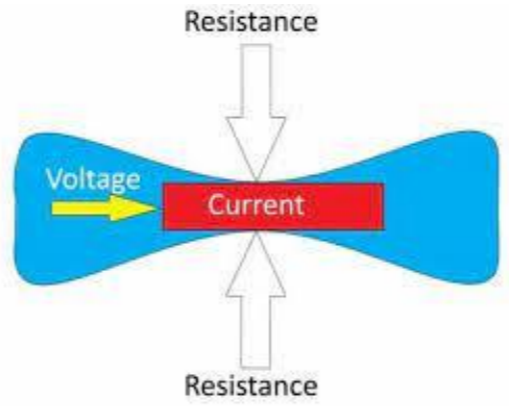


Photo source: [2] - https://encrypted-tbn0.gstatic.com/images?q=tbn:ANd9GcS4-nV0-C0OjNyzDtgR9ub-sgOMYdO16d0e6dvYPx7Vc97Or8_xJ7UUCc0aE929M7hwhZQ&usqp=CAU

Materiallar elektr zaryadining oqimiga qarshilik ko'rsatadigan xususiyatga ega.

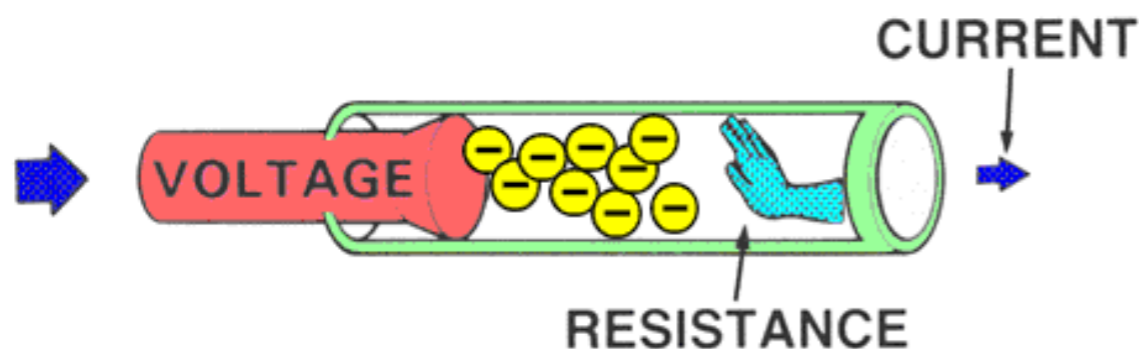


Photo source: [3] - <https://1.bp.blogspot.com/-FokgDwMszuc/XbRy5vWcuSI/AAAAAAAAAKY/Ywgu8bXYNi0MDgbMYZjDv-vbhv6UZMaZAClCBGAsYHQ/s1600/resist3.gif>

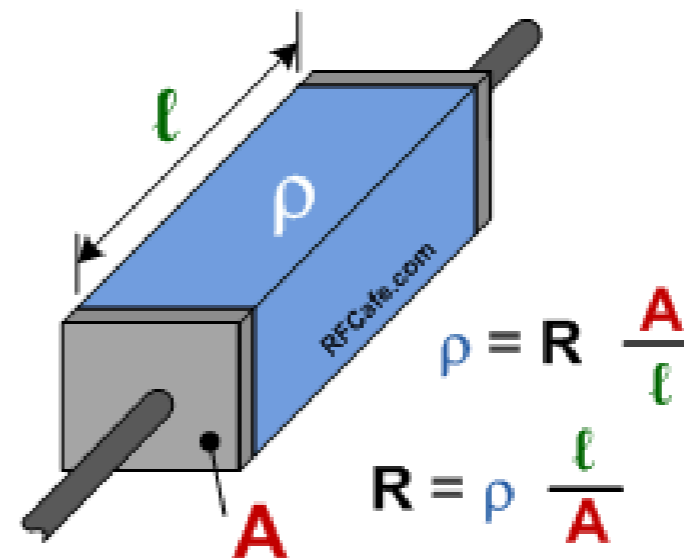



Photo source: [4] - <https://www.rfcafe.com/references/electrical/images2/resistivity.gif>

Ko'ndalang kesim yuzasi (A) bo'lgan har qanday qarshilikka ega material zichligi (ρ) ning va uning uzunligi (l) ga bog'liq (2.1-rasm, a). Biz qarshilikni quyidagi matematik shaklda ifodalaymiz:

$$R = \rho \frac{l}{A} \quad (2.1)$$

bu yerda: ρ - materialning qarshiligi Omda.

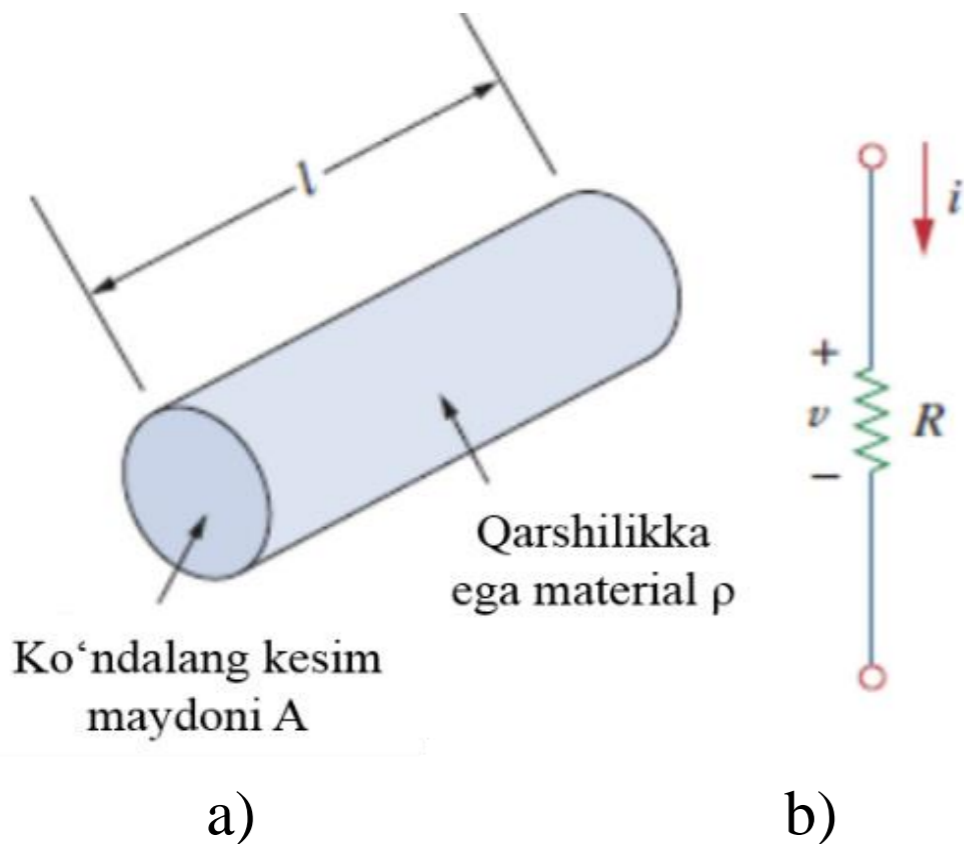SI da o'tkazuvchanlik birligi qilib simens (S) qabul qilingan.



2.1-rasm.

a) qarshilik; b) qarshilikni elektr zanjiridagi shartli belgisi.


O'tkazuvchanlik - elementning elektr tokini o'tkazish qobiliyatidir.

1 simens (S) deb, uchlarida 1 V kuchldanish bo'lganda 1 A tok o'tadigan o'tkazgichning o'tkazuvchanligiga aytiladi.

Odatda, amaliy hisoblashlarda o'tkazuvchanlikning teskari ifodasi bo'lgan kattalikdan foydalaniladi va unga o'tkazgichning qarshiligi deyiladi:

$$R = \frac{1}{G} \quad (2.2)$$

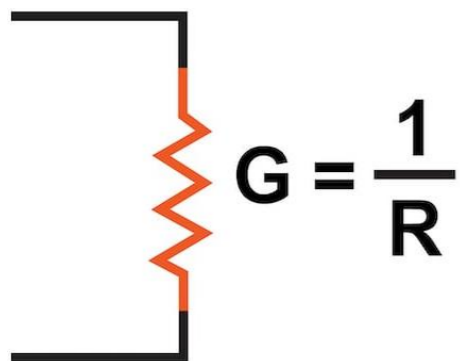Materiallarning qarshiligi yoki o‘tkazuvchanligi quyidagi xususiyatlarga ega:



➤ yaxshi o‘tkazgichlar past qarshilikka ega,

$G \uparrow$ $R \downarrow$

➤ izolyatorlar esa yuqori qarshilikka ega.

$G \downarrow$ $R \uparrow$

Umumiy materiallarning qarshiligi

2.1-jadval

Material	Qarshiligi (Om)	Ishlatilishi
Kumush	$1,64 * 10^{-8}$	o‘tkazgich
Mis	$1,72 * 10^{-8}$	o‘tkazgich
Alyuminiy	$2,8 * 10^{-8}$	o‘tkazgich
Oltin	$2,45 * 10^{-8}$	o‘tkazgich
Uglerodli	$4 * 10^{-5}$	yarim o‘tkazgich
Germaniy	$47 * 10^{-2}$	yarim o‘tkazgich
Silikon	$6,4 * 10^{-2}$	yarim o‘tkazgich
Qog'oz	10^{10}	izolyator
Slyuda	$5 * 10^{11}$	izolyator
Shisha	10^{12}	izolyator
Teflon	$3 * 10^{12}$	izolyator

Photo source: [6] - https://www.allaboutcircuits.com/uploads/thumbnails/conductance_thumbnail.jpg

Rezistor eng oddiy passiv element hisoblanadi.

Materialning oqimga chidamli harakatini modellashtirish uchun ishlatiladigan elektron element *rezistordir*. Elektr zanjirlarni qurish uchun rezistorlar odatda metall qotishmalardan va uglerod birikmalaridan tayyorlanadi.




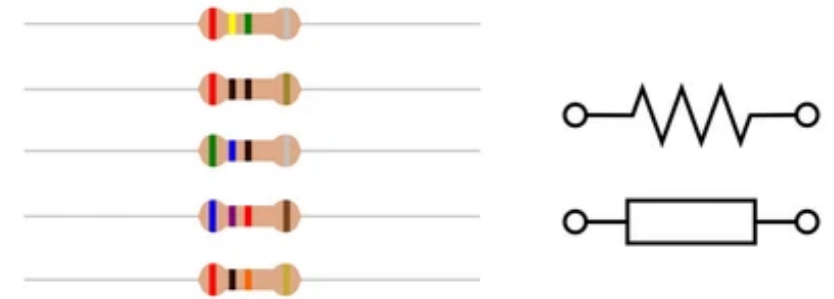
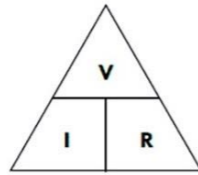
Photo source: [7] - <https://www.shutterstock.com/image-vector/resistor-isolated-electrical-parts-vector-260nw-1562914033.jpg>



Ohm's Law

$$I = \frac{V}{R}$$

Electric current = Voltage / Resistance



$$V = I \times R$$

$$I = V / R$$

$$R = V / I$$

Ohm's law triangle


Nemis fizigi Georg Simon Om (1787-1854) rezistor uchun tok kuchi va kuchlanish o'rtasidagi bog'liqlikni topgan.

Bu munosabatlar Om qonuni sifatida tanilgan.


Photo source: [8] - https://i.ytimg.com/vi/sR_uPI08a9c/maxresdefault.jpg

Om qonuni shuni ko‘rsatadiki, rezistordagi U kuchlanish rezistordan o‘tadigan tok kuchi I ga to‘g‘ridan-to‘g‘ri proporsionaldir. Ya’ni,

$$U \propto I \quad (2.3)$$

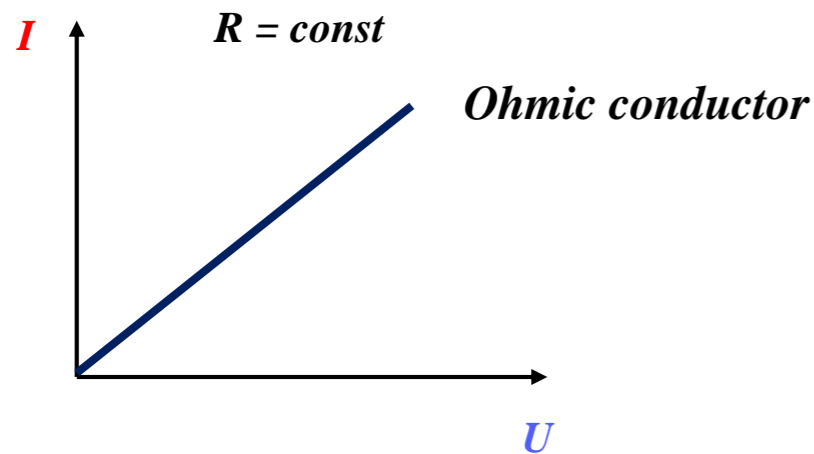

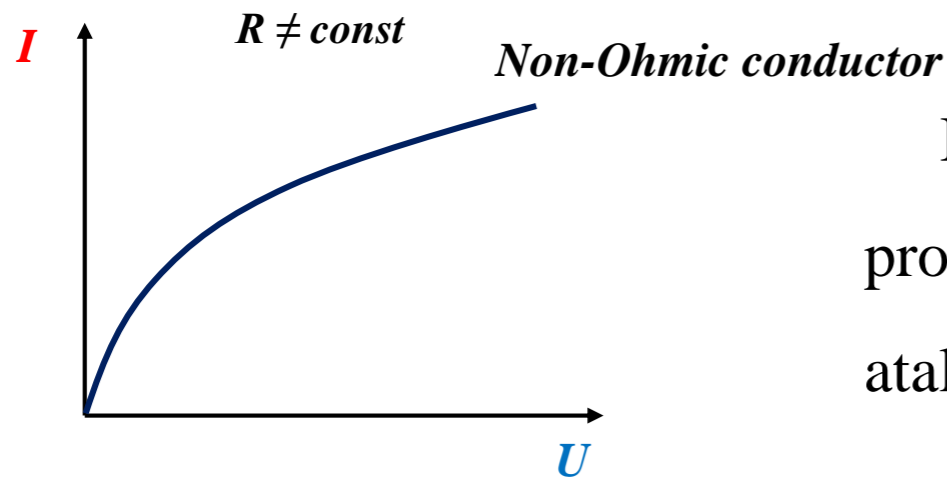Om qonuni ko‘plab o‘tkazgichlarni aniq tasvirlaydi. Ushbu qonunga amal qiladigan materiallar “omik” deb nomlanadi.



Biroq, tok kuchi va kuchlanish farq to‘g‘ridan-to‘g‘ri proporsional bo‘lmagan har qanday o‘tkazgich “nonomik” deb ataladi.

Graph and text source: [9] - <https://www.nagwa.com/en/explainers/927152480586/>

Om rezistorning qarshilik bo‘lishi uchun mutanosiblik konstantasini aniqladi.

Shunday qilib, (2.3) ifoda quyidagi ko‘rinishga ega.

$$U = I \cdot R \tag{2.4}$$

(2.4) tenglamadan xulosa qiladigan bo‘lsak,

$$R = \frac{U}{I} \tag{2.5}$$


Ohms Law Triangle

$I \rightarrow U$ ga to‘g‘ri proporsional.

$U \uparrow \quad I \uparrow$

$I \rightarrow R$ ga teskari proporsional.

$$I = \frac{U}{R}$$

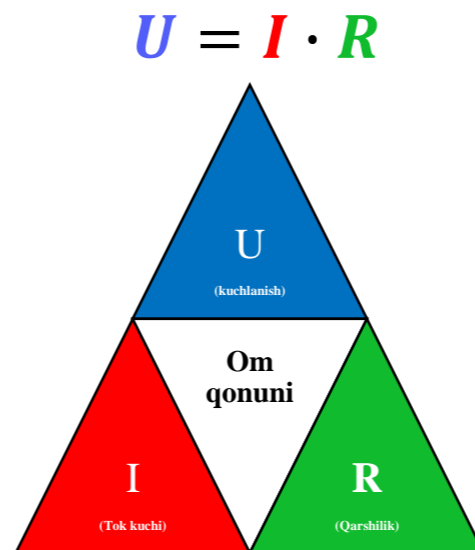

$$R = \frac{U}{I}$$

Zanjirning bir qismi uchun Om qonuniga ko'ra:

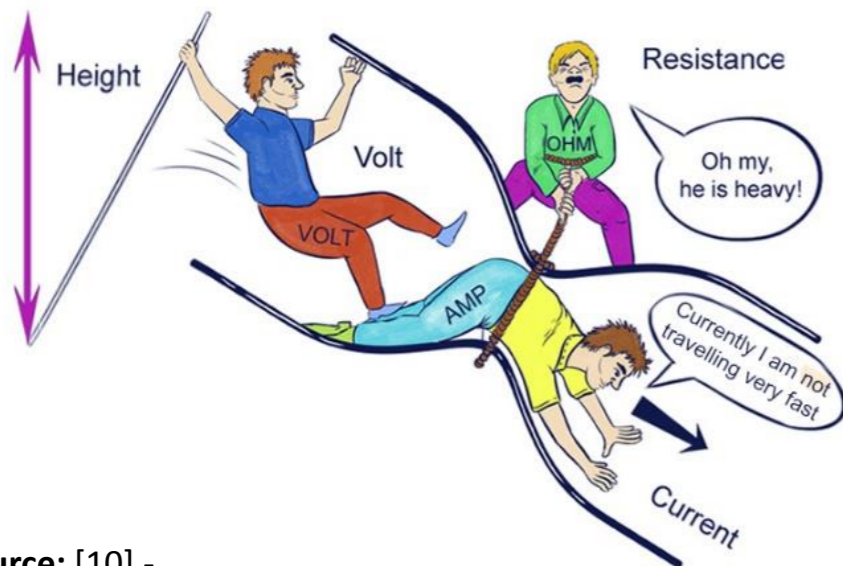


Photo source: [10] -



<https://mammothmemory.net/images/user/base/Physics/Electricity/Ohms%20law/ohms-law.c1c09ec.jpg>

Kattalik	Belgilanishi	O'lchov birligi
Tok kuchi	I	Amper (A)
Kuchlanish	U yoki E	Volt (V)
Qarshilik	R	Om (Ω)

Photo source: [11] -

https://static.wixstatic.com/media/4cbe06_fed4edf5660c483ba4081eb6709029a2~mv2.jpg/v1/fill/w_640,h_426,al_c,lg_1,q_80,enc_auto/4cbe06_fed4edf5660c483ba4081eb6709029a2~mv2.jpg

Example:

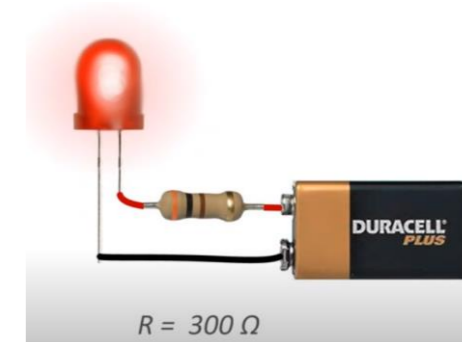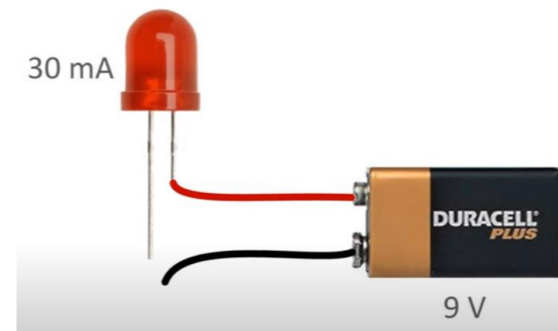

$$R = ?$$

$$R = \frac{U}{I}$$

$$R = \frac{9}{0,03} = 300 \Omega$$

Example source: [12] - <https://www.youtube.com/watch?v=Gc1wVdbV10E>

2.1.1-masala: Elektr dazmol 120 V da 2 A tok iste'mol qiladi. Uning qarshiligini toping?

Yechish: Om qonunidan foydalanib,

$$R = \frac{u}{i} = \frac{120}{2} = 60 \Omega$$


Demak, Om qonunini qo‘llash uchun biz tok kuchi yo‘nalishi va kuchlanish qutblariga diqqat bilan e‘tibor berishimiz kerak. Tok kuchining yo‘nalishi va kuchlanishning qutblari **PASSIV ISHORA KONVENSIYASI**ga mos kelishi kerak.

Bu shuni anglatadiki, $u = iR$ bo‘lishi uchun tok kuchi yuqori potensialdan pastroq potensialga o‘tadi.

Quvvat sarf bo‘ladi.

Agar tok kuchi pastroq potensialdan yuqori potensialga o‘tsa, $u = -iR$.

Quvvat ta‘minlanadi.

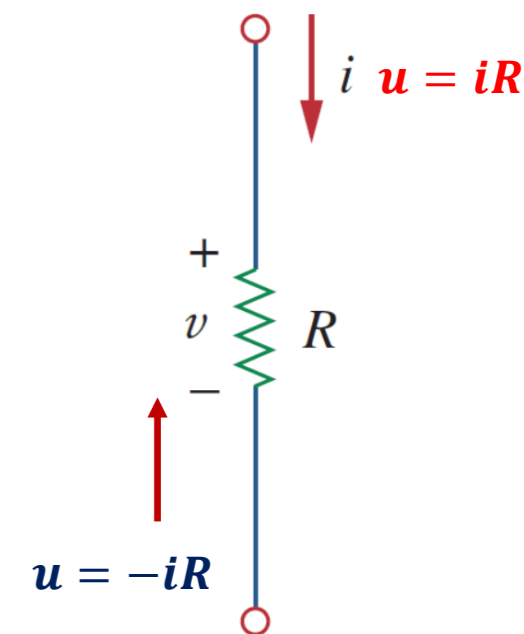

2.1-rasm, b

Photo source: [5] - Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 30.

R ning qiymati noldan cheksizgacha bo‘lishi mumkinligi sababli, R ning ikkita o‘ta mumkin bo‘lgan qiymatini ko‘rib chiqish muhimdir.

Open and Short Circuits


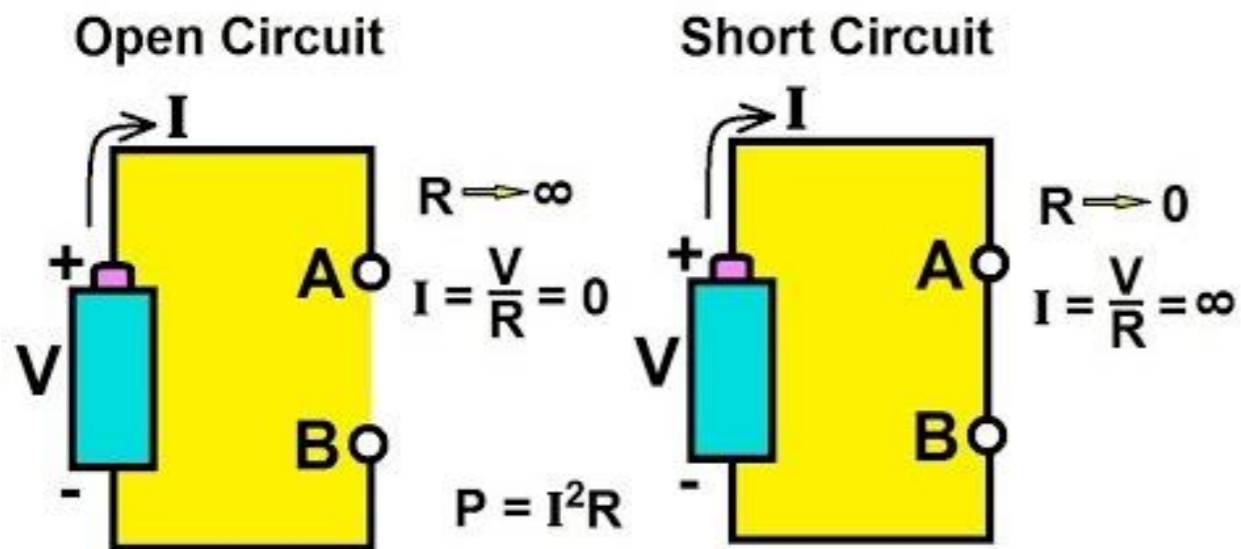



Photo source: [13]

<https://i.ytimg.com/vi/cgtSKaVTPmY/hqdefault.jpg>

Ochiq zanjir

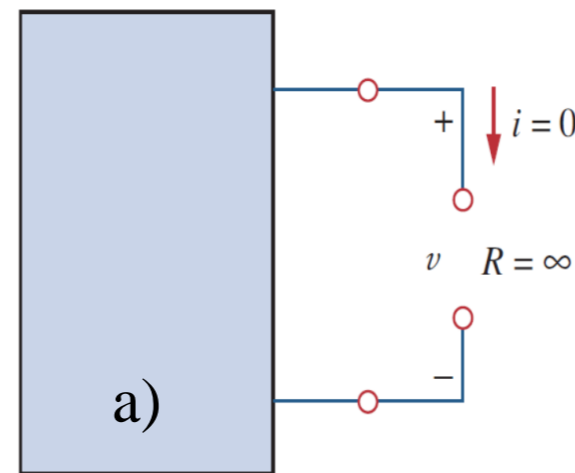

Qisqa tutashuv zanjir

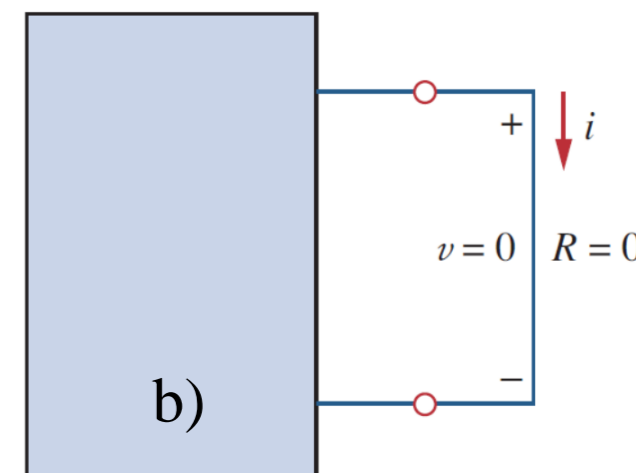


2.2-rasm.


$$i = \lim_{R \rightarrow \infty} \frac{u}{R} = 0 \quad (2.6)$$

$$u = iR = 0 \quad (2.7)$$


Photo source: [14] - Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 32.

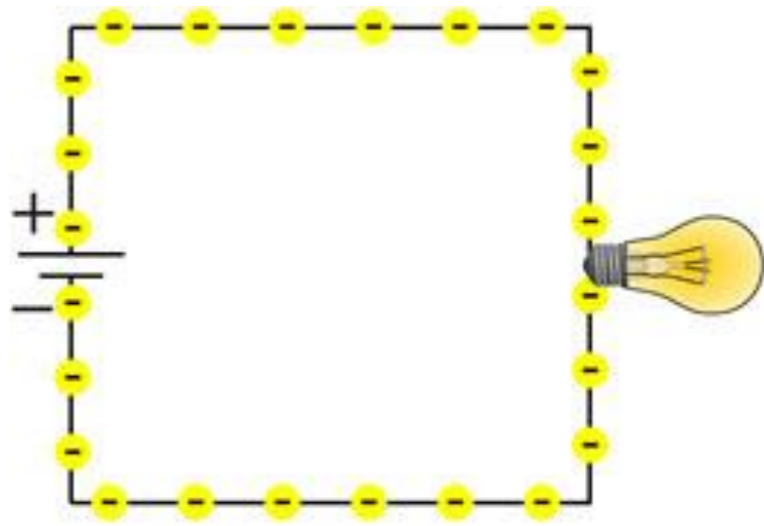

closed circuit

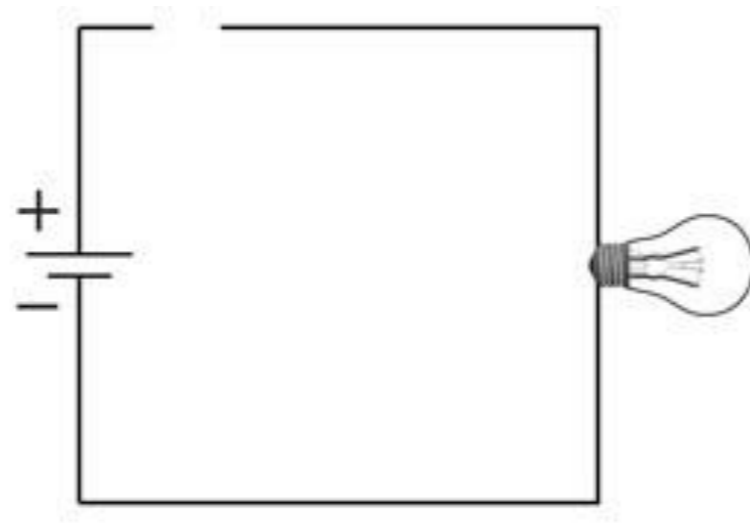

open circuit

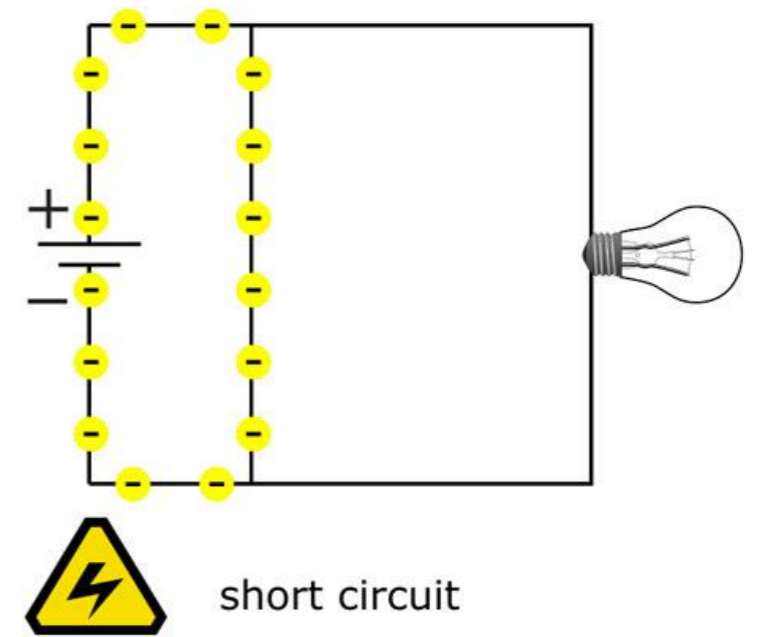

short circuit

Photo source: [15] - <https://www.dummies.com/wp-content/uploads/489264.image0.jpg>

Photo source: [16] - <https://www.dummies.com/wp-content/uploads/489267.image3.jpg>

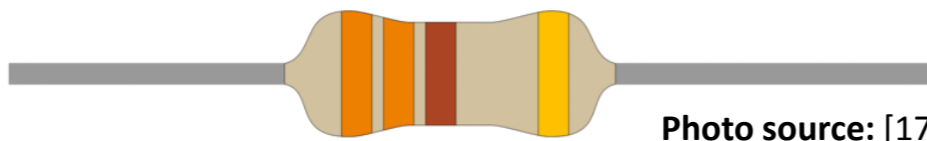


Photo source: [17] - <https://www.electrokit.com/uploads/productimage/40810/40810233.png>

Doimiy

O'zgaruvchan



Fixed Value Resistor (IEC Symbol)




Fixed Value Resistor (IEEE Symbol)




Variable Resistor (Potentiometer)



Variable Resistor (Rheostat)

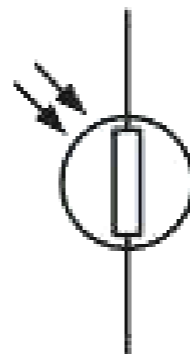

(LDR) Light Dependant Resistor

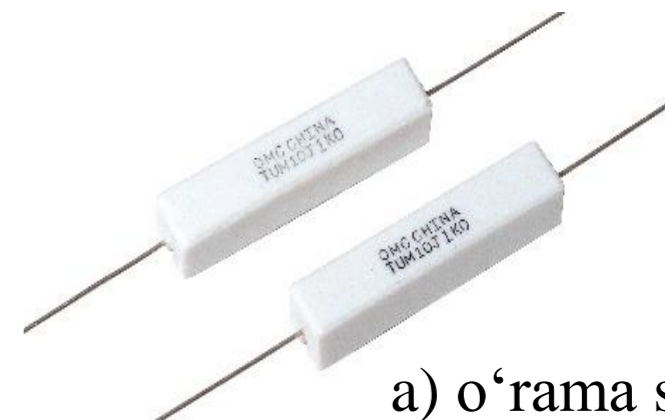


a) o'rama simli; (wire-wound type)

Photo source: [19] - https://www.ohmite.com/assets/images/buckets/TUM_1-updated.jpg

Photo source: [18] - <https://components101.com/sites/default/files/inline-images/Resistor-Symbols.png>

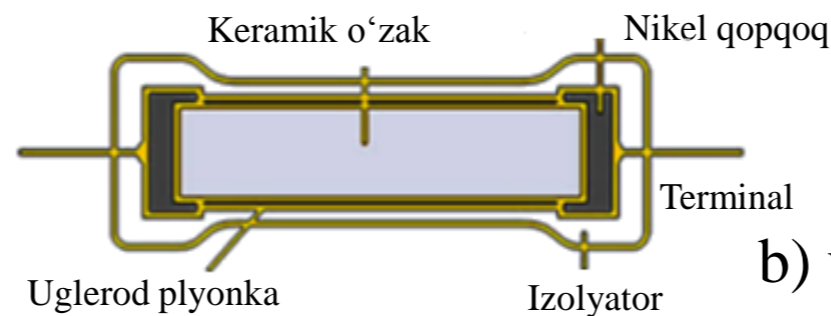Kompozitsion rezistorlar katta qarshilik kerak bo'lganda ishlatiladi.



b) uglorod plyonkali turi. (carbon film type)

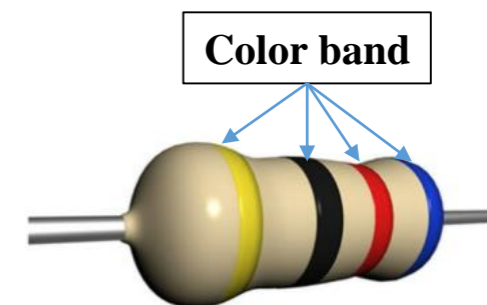


Photo source: [20] - <https://blogmedia.testbook.com/blog/wp-content/uploads/2022/10/parts-of-carbon-resistor-39aec770.png>

2.3-rasm. Doimiy rezistorlar (fixed resistors):

How to read Resistor Color Codes?

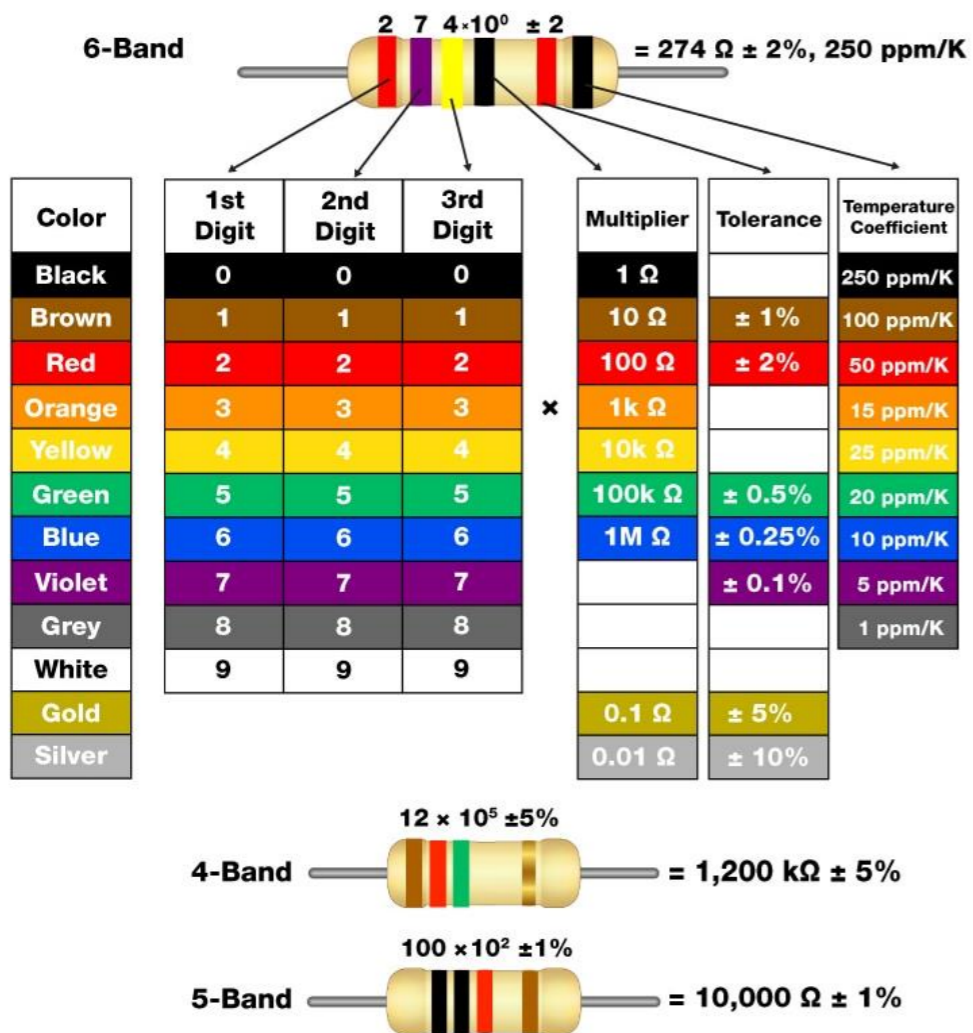


Photo source: [21] - <https://static4.arrow.com/-/media/arrow/images/miscellaneous/h/how-to-read-resistor-color-codes.jpg>

Ohms Law Pie Chart – Ohm qonun doirasi diagrammasi


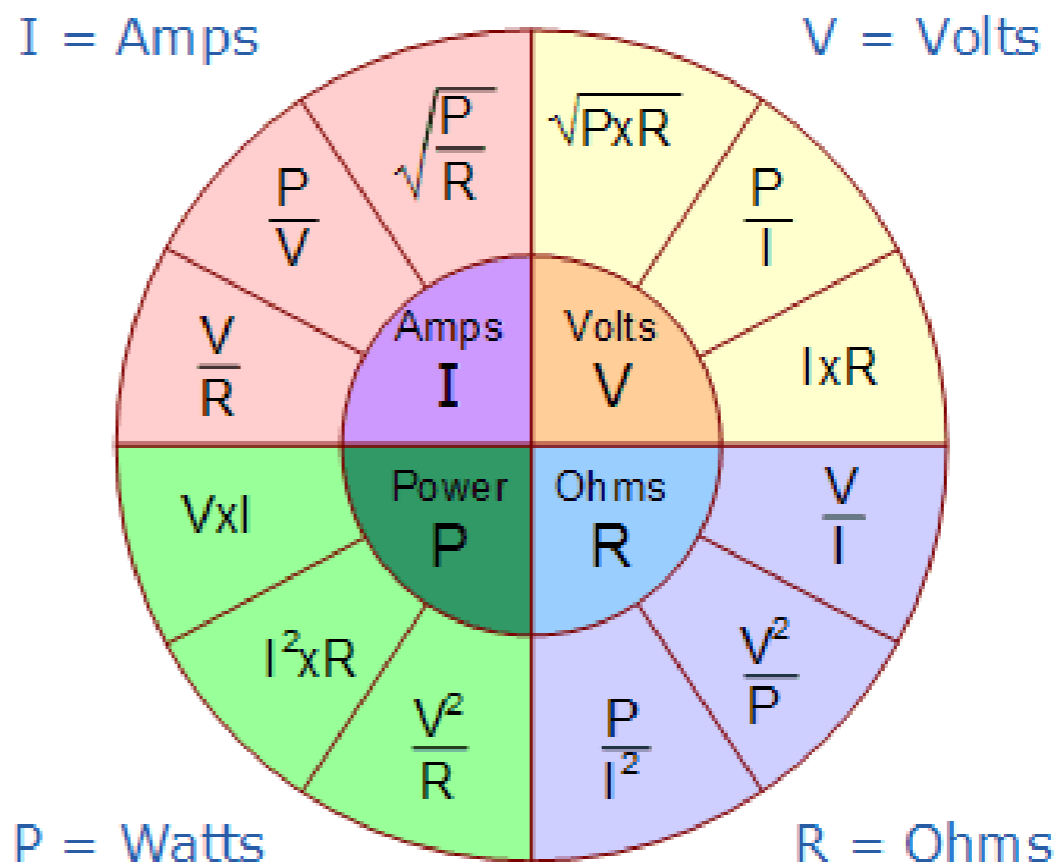


Photo source: [22] - <https://www.electronics-tutorials.ws/wp-content/uploads/2018/05/dccircuits-dcp4.gif>

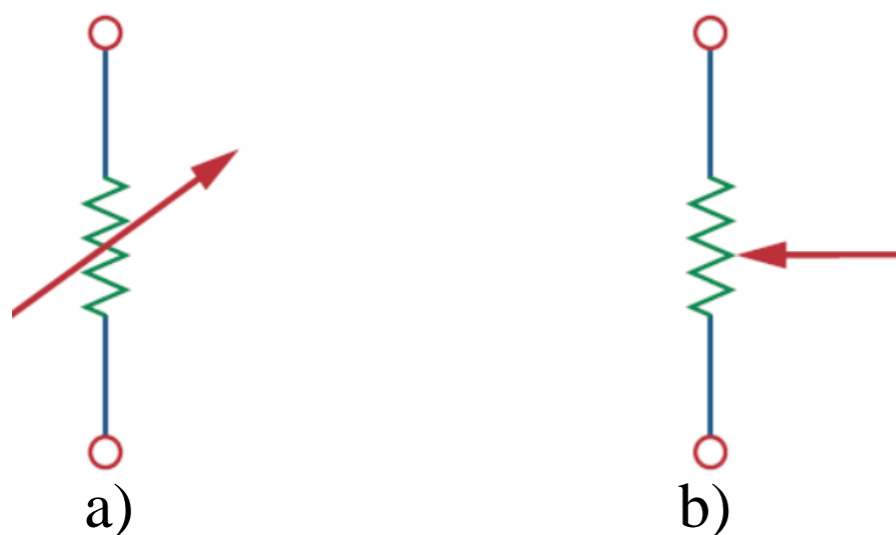O'zgaruvchan rezistorlar sozlanuvchan qarshilikka ega.



2.4-rasm. Rezistorning zanjirdagi belgisi:

- a) umumiy o'zgaruvchan rezistor;
- b) potensiometrli rezistor.

Potensiometr kontaktli uch terminalga ega elementdan tashkil topgan.

Kompozitsion turi


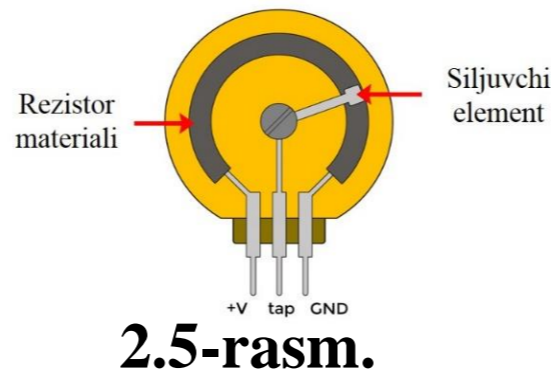


Photo source: [23] - <https://www.circuitbasics.com/wp-content/uploads/2020/05/How-a-Potentiometer-Works-1024x655.png>

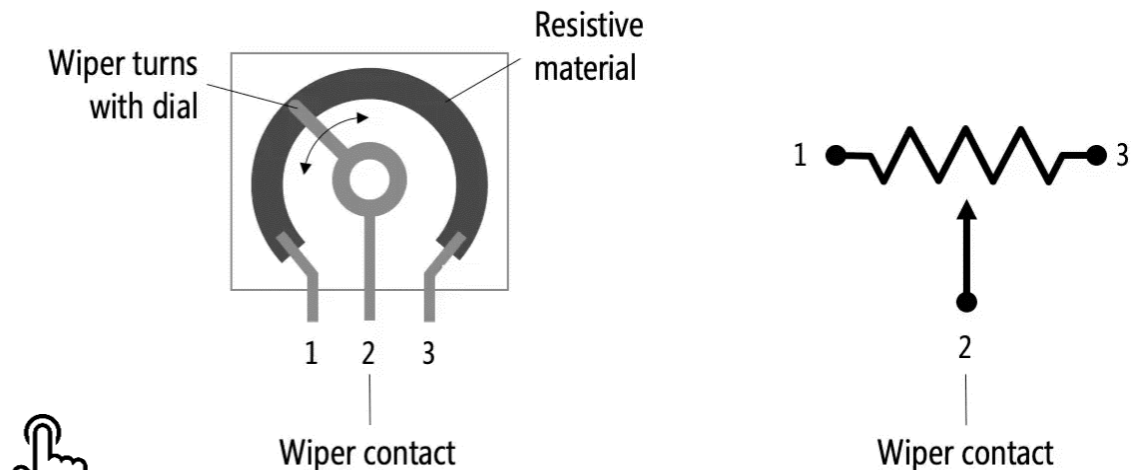

Video source: [24] - https://makeabilitylab.github.io/physcomp/electronics/assets/videos/Potentiometer_Overview_ByJonFroehlich.mp4

PHOTOCELL (light-dependent resistor)	RHEOSTAT (two-leg variable resistor)	FORCE-SENSITIVE RESISTOR (aka FSR; two-leg var resistor)	THERMISTOR RESISTOR (two-leg variable resistor)	ROTARY POTENTIOMETER (three-leg variable resistor)	SLIDE POTENTIOMETER (three-leg variable resistor)


Photo source: [25] - https://makeabilitylab.github.io/physcomp/electronics/assets/images/SchematicSymbolsOfVariableResistors_ByJonFroehlich.png

Slayder potensiometr



Photo source: [26] -

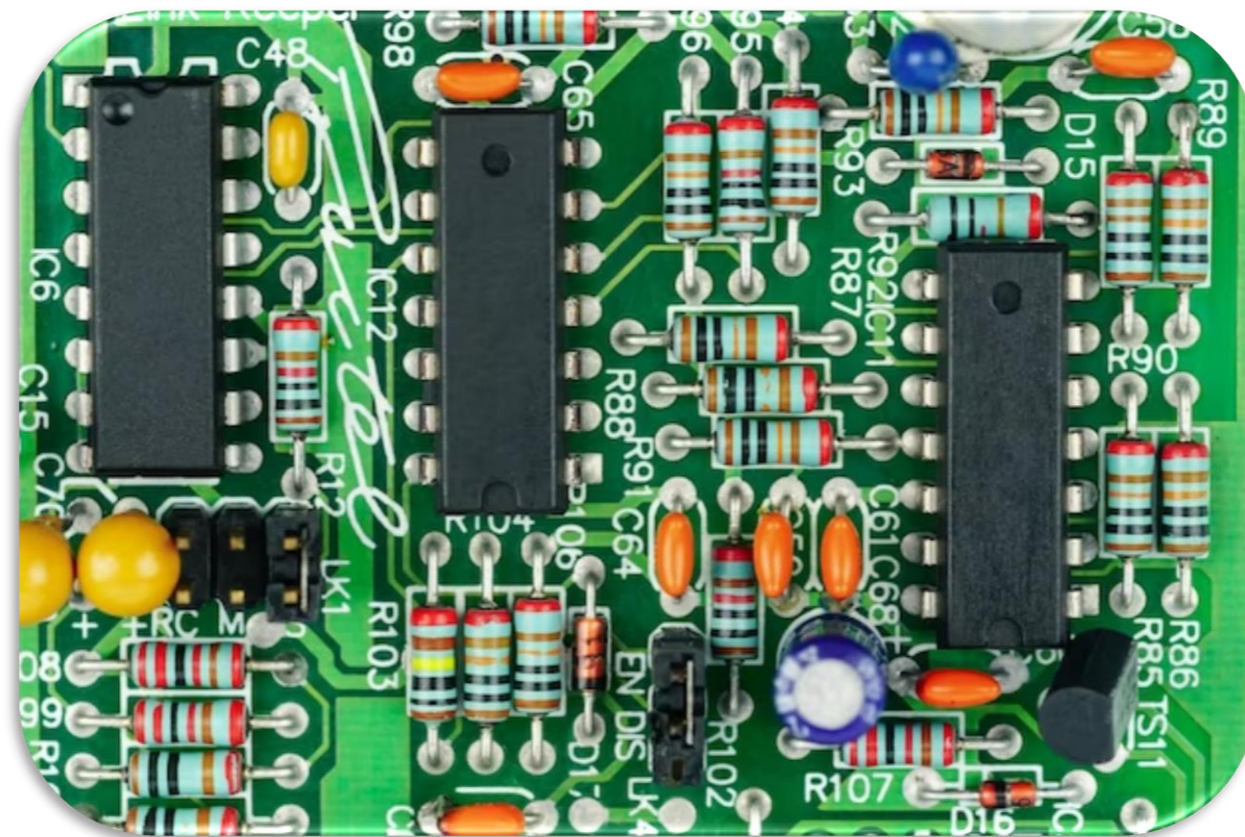https://probots.co.in/pub/media/catalog/product/cache/ca2cd736c0c15942c77daffc8cf27b66/1/k/1k_ohm_variable_resistor_potentiometer1-1000x1000.jpg



2.6-rasm. Integratsiyalashgan elektron platadagi rezistorlar.

Photo source: [28] - https://img.freepik.com/premium-photo/closeup-printed-circuit-board-with-components-such-as-resistors-integrated-circuits_483511-3552.jpg


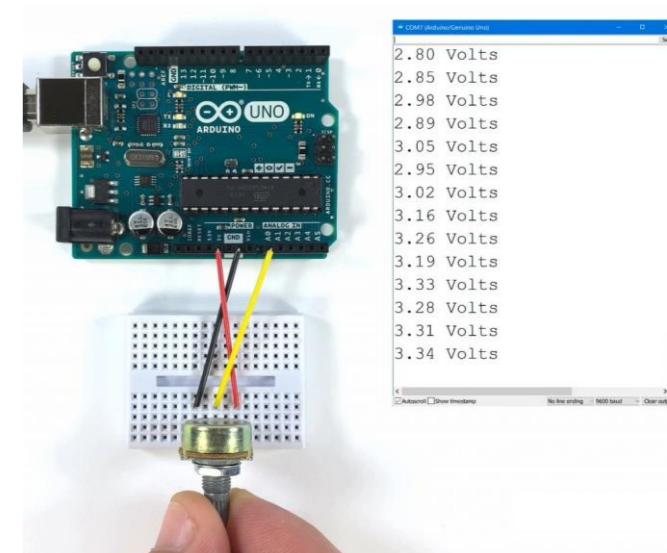


Photo source: [27] -

<https://www.circuitbasics.com/wp-content/uploads/2020/05/Potentiometer-Voltage-Output-on-Arduino-Serial-Monitor-1024x848.jpg>

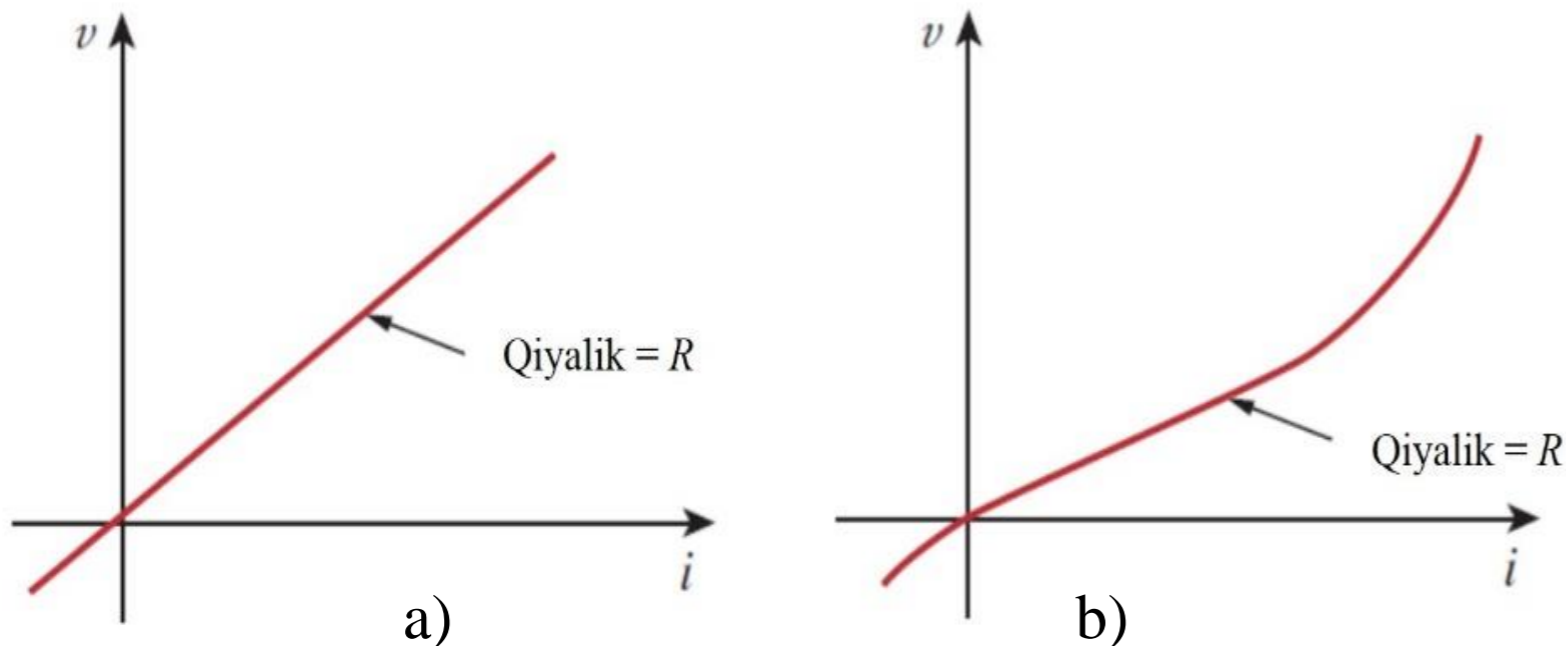Barcha rezistorlar Om qonuniga bo‘ysunmaydi.



2.7-rasm. Rezistorning $i - u$ tavsifi:

a) chiziqli rezistor; b) chiziqli bo‘lmagan rezistor.

Chiziqli bo‘lmagan qarshilikka - **lampochka** va **diodlar** misol bo‘la oladi.

Zanjir tahlilida foydali miqdor R qarshiligining o‘zaro nisbati bo‘lib, u o‘tkazuvchanlik deb nomlanadi va G bilan belgilanadi:

$$G = \frac{1}{R} = \frac{i}{u} \quad (2.8)$$

$$1 \text{ S} = 1 \text{ U} = 1 \text{ A/V} \quad (2.9)$$

$$10 \text{ } \Omega = 0,1 \text{ S}$$

$$i = Gu \quad (2.10)$$

(1.14) va (2.4) tenglamalar yordamida ifodalanishi mumkin.

$$p = u \cdot i = i \cdot R \cdot i = i^2 \cdot R = \frac{u^2}{R} \tag{2.11}$$

Rezistor tomonidan tarqaladigan quvvat G sifatida ham ifodalanishi mumkin.

$$p = u \cdot i = u \cdot u \cdot G = u^2 G = \frac{i^2}{R} \tag{2.12}$$

The Power Triangle

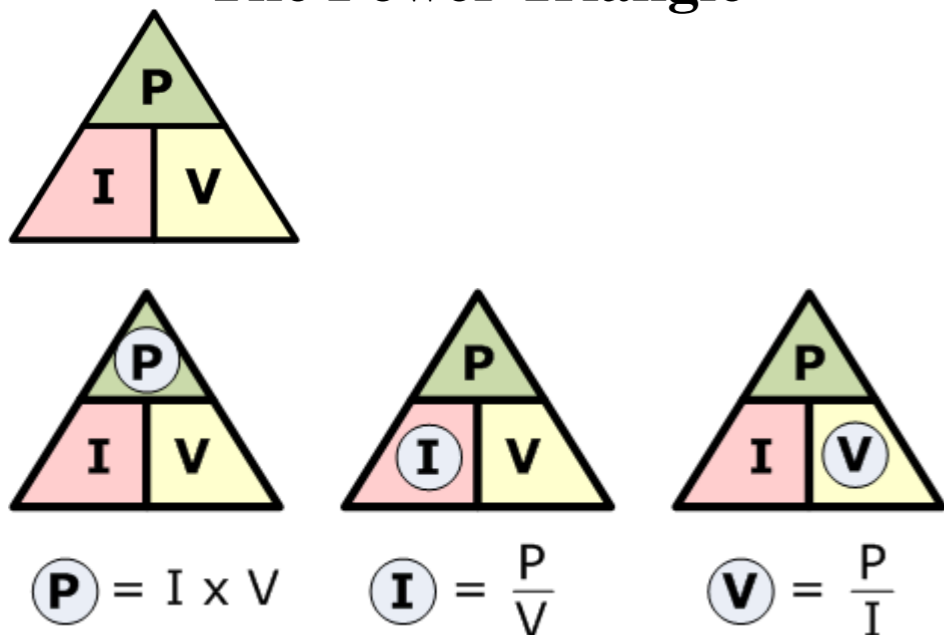



Photo source: [29] - <https://www.electronics-tutorials.ws/wp-content/uploads/2018/05/dccircuits-dcp25.gif>

Ohms Law Matrix Table

Ohms Law Formulas				
Known Values	Resistance (R)	Current (I)	Voltage (V)	Power (P)
Current & Resistance	---	---	$V = I \times R$	$P = I^2 \times R$
Voltage & Current	$R = \frac{V}{I}$	---	---	$P = V \times I$
Power & Current	$R = \frac{P}{I^2}$	---	$V = \frac{P}{I}$	---
Voltage & Resistance	---	$I = \frac{V}{R}$	---	$P = \frac{V^2}{R}$
Power & Resistance	---	$I = \sqrt{\frac{P}{R}}$	$V = \sqrt{P \times R}$	---
Voltage & Power	$R = \frac{V^2}{P}$	$I = \frac{P}{V}$	---	---

Photo source: [30] - <https://www.electronics-tutorials.ws/wp-content/uploads/2018/05/dccircuits-dcp4a.gif>

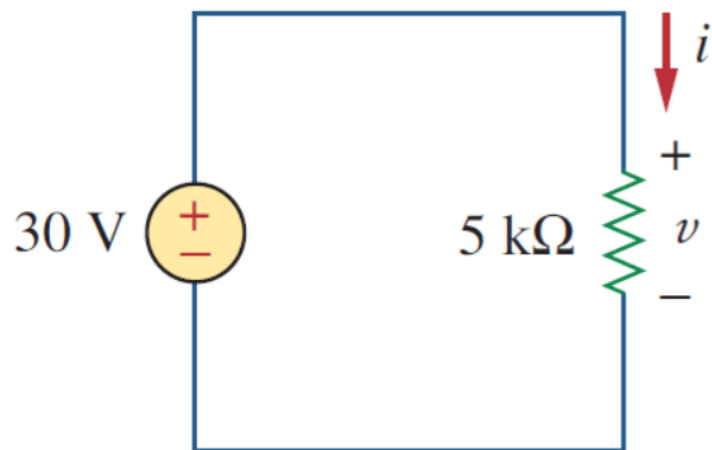2.1.2-masala: 2.8-rasmda ko'rsatilgan zanjirning tok kuchi i , o'tkazuvchanligi G va quvvati p ni hisoblang.



2.8-rasm.

Demak, tok kuchi

$$i = \frac{u}{R} = \frac{30}{5 \cdot 10^3} = 6 \text{ mA}$$

O'tkazuvchanlik,

$$G = \frac{1}{R} = \frac{1}{5 \cdot 10^3} = 0,2 \text{ mS}$$

Quvvatni turli usullar bilan hisoblashimiz mumkin.

$$p = ui = 30(6 \cdot 10^{-3}) = 180 \text{ mW}$$

$$p = i^2 R = (6 \cdot 10^{-3})^2 5 \cdot 10^3 = 180 \text{ mW}$$



$$p = u^2 G = (30)^2 0,2 \cdot 10^{-3} = 180 \text{ mW}$$

2.2. Tugun, shaxobcha va kontur.

Elektr zanjiridagi elementlarni joylashtirish va tarmoqning geometrik konfiguratsiyasi bilan bog‘liq xususiyatlarni o‘rganishimizda shaxobchalar (*branches*), tugunlar (*nodes*) va halqalar (*loops*) haqida umumiy ma‘lumotga ega bo‘lishimiz kerak.

b shaxobchalar, n tugunlar va l mustaqil halqalari bo‘lgan tarmoq topologiyasining asosiy teoremasini qanoatlantiradi:

$$b = l + n - 1 \quad (2.13)$$

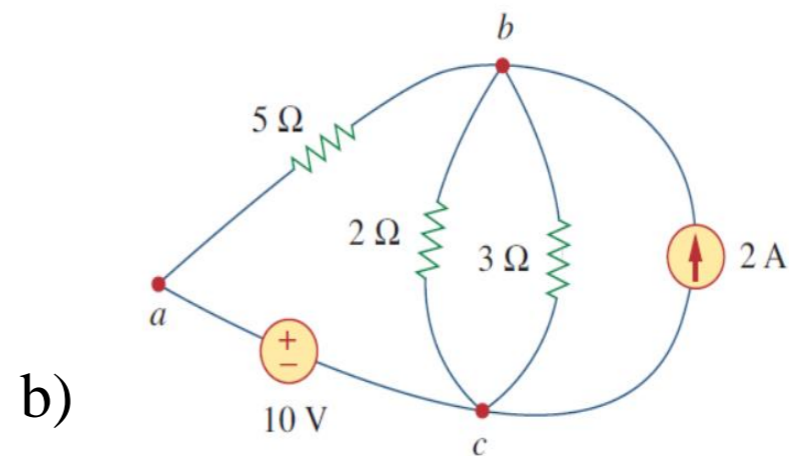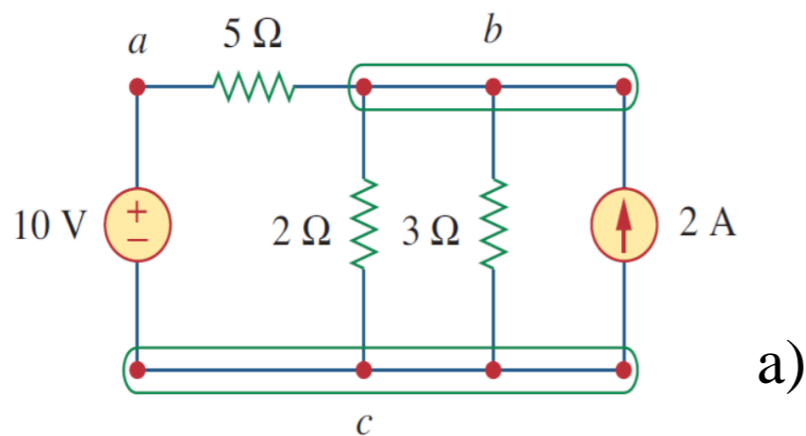


2.9-rasm.

a) tugunlar, shaxobchalar va halqalar; b) a ni uch tugunli zanjirini qayta chizilgan holati.

Elektr zanjirlari umumiy holda shaxobchalar, tugunlar va konturlardan iborat bo‘ladi.

Ikki tugun oralig‘iga ketma-ket ulangan elementlardan iborat bir xil tok o‘tadigan zanjirning qismi **shaxobcha** deb ataladi (2.10-rasm, a).

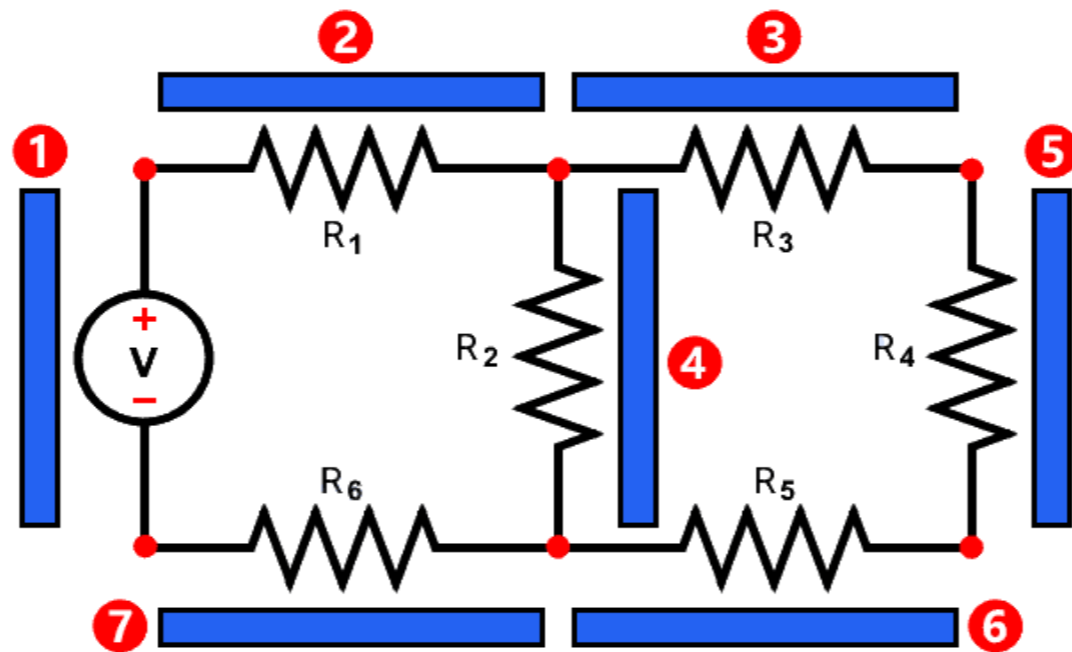Shaxobcha tarkibida ixtiyoriy miqdordagi ketme-ket ulangan qarshilik, kondensator, induktivlik elementlari, EYuK manbalari bo‘lishi mumkin.



a)

2.10-rasm.


a) elektr zanjirining shaxobchasi;

Photo source: [31] -

<https://www.electricaltechnology.org/wp-content/uploads/2013/12/How-to-Find-the-Number-of-Branches-in-an-Electric-Circuit.png>

Kamida uchta shaxobcha birlashgan nuqta esa, elektr zanjirining **tuguni** deyiladi.

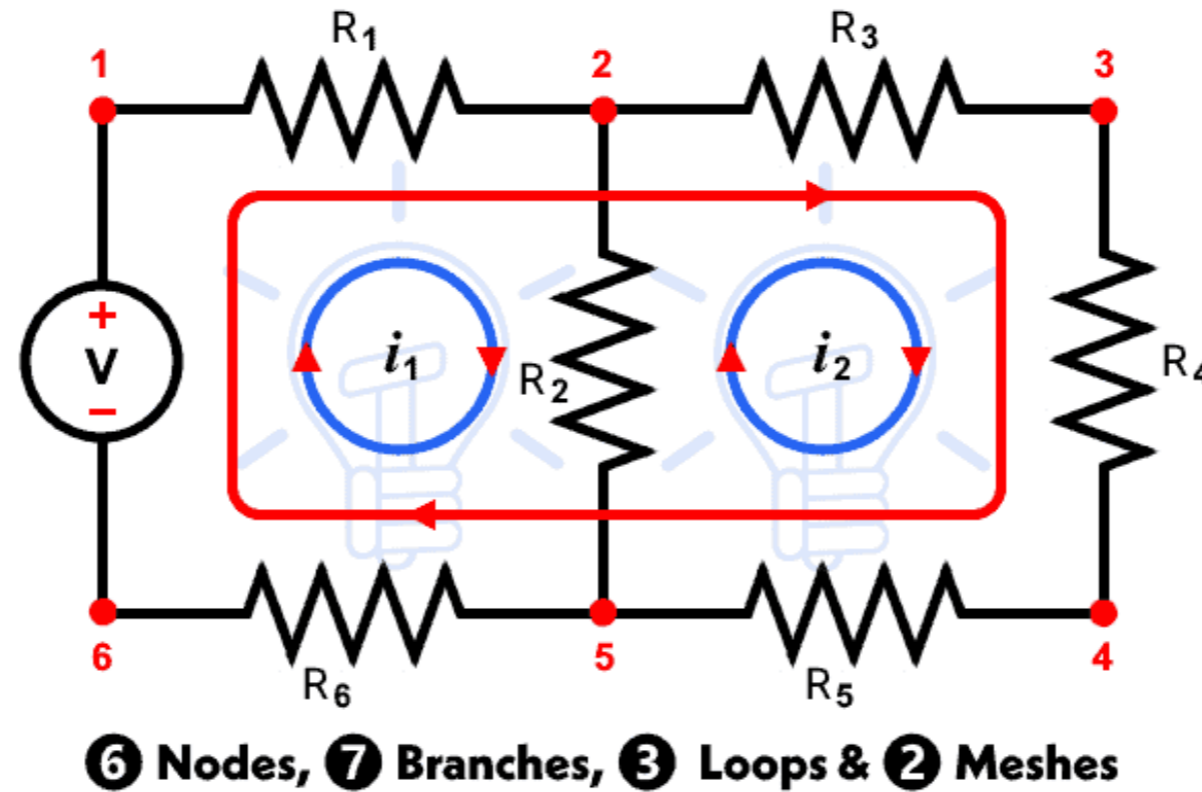Elektr zanjirining **konturi** deb, bir necha ketma-ket shaxobchalar orqali o'tgan ixtiyoriy berk yo'lga aytiladi (2.10-rasm, b 1,2,5,6,1; 2,3,4,5,6).



b)

2.10-rasm.

b) elektr zanjirining tuguni.

Photo source: [32] -

<https://www.electricaltechnology.org/wp-content/uploads/2013/12/How-to-Determine-the-Number-of-Nodes-Loops-Branched-and-Meshes-in-a-Circuit-.png>

Yuqoridagi zanjir elementlarining ta'riflaridan ko'rinib turibdiki, zanjir topologiyasi elektr zanjiridagi kuchlanish va tok kuchlarini o'rganish uchun katta ahamiyatga ega.



<p>Zanjir elementlarining joylashuvi</p>	<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>SERIES CIRCUIT</p>  </div> <div style="text-align: center;"> <p>PARALLEL CIRCUIT</p>  </div> </div>	
<p>Kuchlanish</p>	$U = U_1 + U_2 + U_3$	$U = U_1 = U_2 = U_3$
<p>Tok kuchi</p>	$I = I_1 = I_2 = I_3$	$I = I_1 + I_2 + I_3$

Photo source: [33] - <https://www.electricaltechnology.org/wp-content/uploads/2020/05/Difference-Between-Series-and-Parallel-Circuit.png>

FOYDALANILGAN MANBALAR:

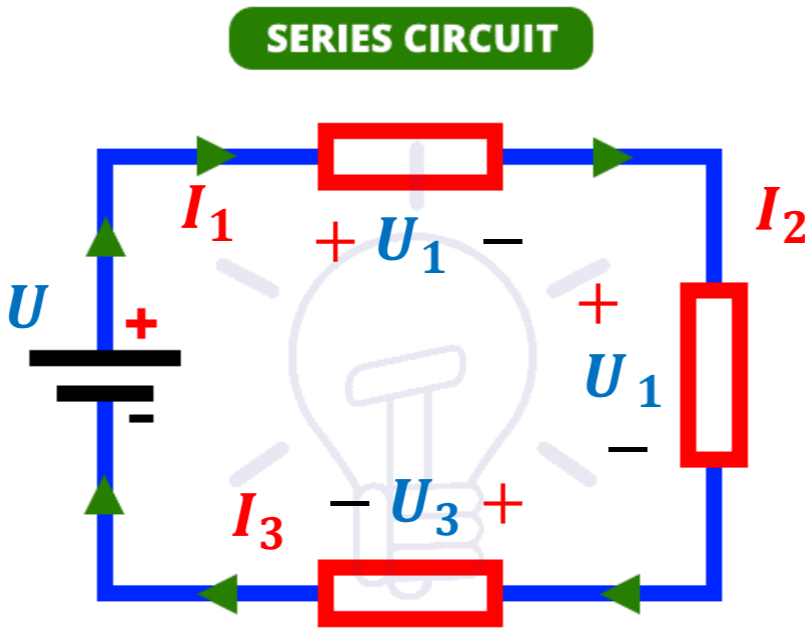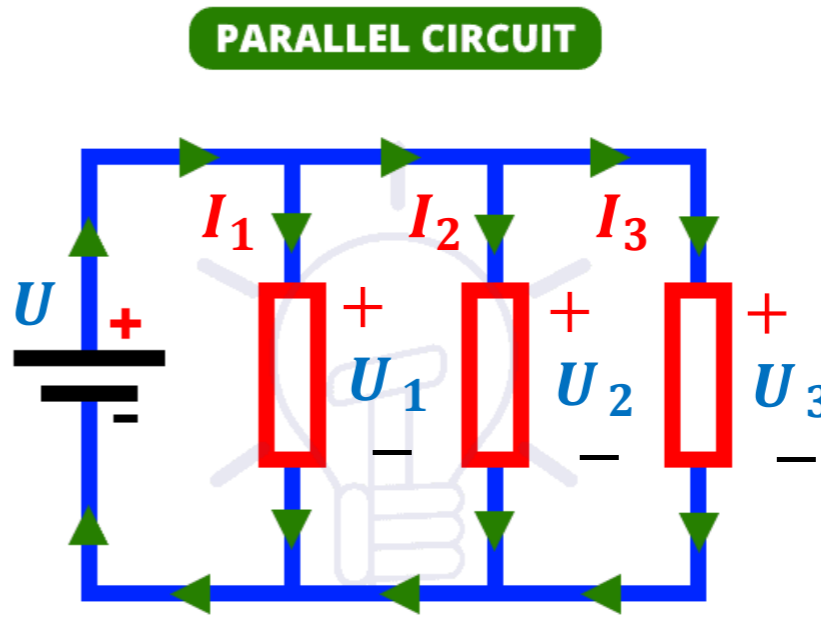1. <https://kaiserscience.files.wordpress.com/2016/03/small-vs-large-electrical-current1.gif>
2. https://encrypted-tbn0.gstatic.com/images?q=tbn:ANd9GcS4-nV0-C00jNyzDtgr9ub-sgOMYdO16d0e6dvYPx7Vc97Or8_xJ7UUCc0aE929M7hwhZQ&usqp=CAU
3. <https://1.bp.blogspot.com/-FokgDwMszuc/XbRy5vWcuSI/AAAAAAAAAKY/Ywgu8bXYNi0MDgbMYZjDv-vbhv6UZMaZAClCBGAsYHQ/s1600/resist3.gif>
4. <https://www.rfcafe.com/references/electrical/images2/resistivity.gif>
5. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – 30 (905) p.
6. https://www.allaboutcircuits.com/uploads/thumbnails/conductance_thumbnail.jpg
7. <https://www.shutterstock.com/image-vector/resistor-isolated-electrical-parts-vector-260nw-1562914033.jpg>
8. https://i.ytimg.com/vi/sR_uPI08a9c/maxresdefault.jpg
9. <https://www.nagwa.com/en/explainers/927152480586/>
10. <https://mammothmemory.net/images/user/base/Physics/Electricity/Ohms%20law/ohms-law.c1c09ec.jpg>
11. https://static.wixstatic.com/media/4cbe06_fed4edf5660c483ba4081eb6709029a2~mv2.jpg/v1/fill/w_640,h_426,al_c,lg_1,q_80,enc_auto/4cbe06_fed4edf5660c483ba4081eb6709029a2~mv2.jpg
12. <https://www.youtube.com/watch?v=Gc1wVdbVIOE>
13. <https://i.ytimg.com/vi/cgtSKaVTPmY/hqdefault.jpg>
14. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 32.
15. <https://www.dummies.com/wp-content/uploads/489264.image0.jpg>
16. <https://www.dummies.com/wp-content/uploads/489267.image3.jpg>
17. <https://www.electrokit.com/uploads/productimage/40810/40810233.png>
18. <https://components101.com/sites/default/files/inline-images/Resistor-Symbols.png>
19. https://www.ohmite.com/assets/images/buckets/TUM_1-updated.jpg
20. <https://blogmedia.testbook.com/blog/wp-content/uploads/2022/10/parts-of-carbon-resistor-39aec770.png>
21. <https://static4.arrow.com/-/media/arrow/images/miscellaneous/h/how-to-read-resistor-color-codes.jpg>
22. <https://www.electronics-tutorials.ws/wp-content/uploads/2018/05/dccircuits-dcp4.gif>
23. <https://www.circuitbasics.com/wp-content/uploads/2020/05/How-a-Potentiometer-Works-1024x655.png>
24. https://makeabilitylab.github.io/physcomp/electronics/assets/videos/Potentiometer_Overview_ByJonFroehlich.mp4
25. https://makeabilitylab.github.io/physcomp/electronics/assets/images/SchematicSymbolsOfVariableResistors_ByJonFroehlich.png
26. https://probots.co.in/pub/media/catalog/product/cache/ca2cd736c0c15942c77daffc8cf27b66/1/k/1k_ohm_variable_resistor_potentiometer1-1000x1000.jpg
27. <https://www.circuitbasics.com/wp-content/uploads/2020/05/Potentiometer-Voltage-Output-on-Arduino-Serial-Monitor-1024x848.jpg>
28. https://img.freepik.com/premium-photo/closeup-printed-circuit-board-with-components-such-as-resistors-integrated-circuits_483511-3552.jpg
29. <https://www.electronics-tutorials.ws/wp-content/uploads/2018/05/dccircuits-dcp25.gif>
30. <https://www.electronics-tutorials.ws/wp-content/uploads/2018/05/dccircuits-dcp4a.gif>
31. <https://www.electricaltechnology.org/wp-content/uploads/2013/12/How-to-Find-the-Number-of-Branches-in-an-Electric-Circuit.png>
32. <https://www.electricaltechnology.org/wp-content/uploads/2013/12/How-to-Determine-the-Number-of-Nodes-Loops-Branches-and-Meshes-in-a-Circuit-.png>
33. <https://www.electricaltechnology.org/wp-content/uploads/2020/05/Difference-Between-Series-and-Parallel-Circuit.png>



*E'TIBORINGIZ
UCHUN
RAHMAT!!!*