


8-Mavzu: Ikkinchi tartibli elektr zanjiri.

(8th Topic: Second-Order Circuit)

8-Mavzuning 2-qismi

(2nd part of the 8th Topic)

*9-hafta uchun
For the 9th week*

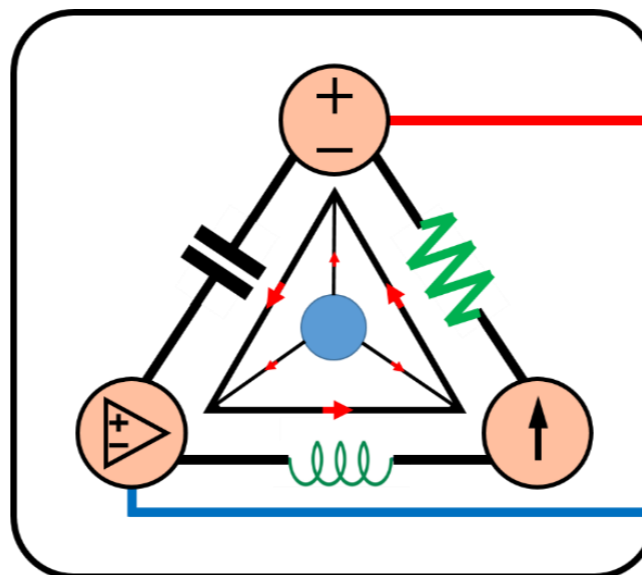

Lecturer: Ph.D., Yusupov Sarvarbek

*Toshkent Kimyo Xalqaro Universiteti
"Mashinasozlik texnologiyasi" kafedrasida
Toshkent shahri, Usmon Nosir, 156-uy.*

8-Mavzu: Ikkinchi tartibli elektr zanjiri.

(8th Topic: Second-Order Circuit)

O'quv rejasi:

8.1. Umumiy tushunchalar.

8.2. Boshlang'ich va yakuniy qiymatlarni topish.

8.3. Manbadan holi ketma-ket ulangan qarshilik, induktor va kondensator (RLC) zanjiri.


8.4. Manbadan holi parallel ulangan qarshilik, induktor va kondensator (RLC) zanjiri.

8.3. Manbadan holi ketma-ket ulangan qarshilik, induktor va kondensator (RLC) zanjiri.


RLC ketma-ketligidan iborat bo'lgan janjirning tabiiy reaksiyasini tushunish elektrotexnika muhandislari tomonidan kelajakdagi tadqiqotlarni olib borishda fundament hisoblanadi.

Zanjir kondensator va induktorda dastlabki saqlangan energiya bilan uyg'otiladi.

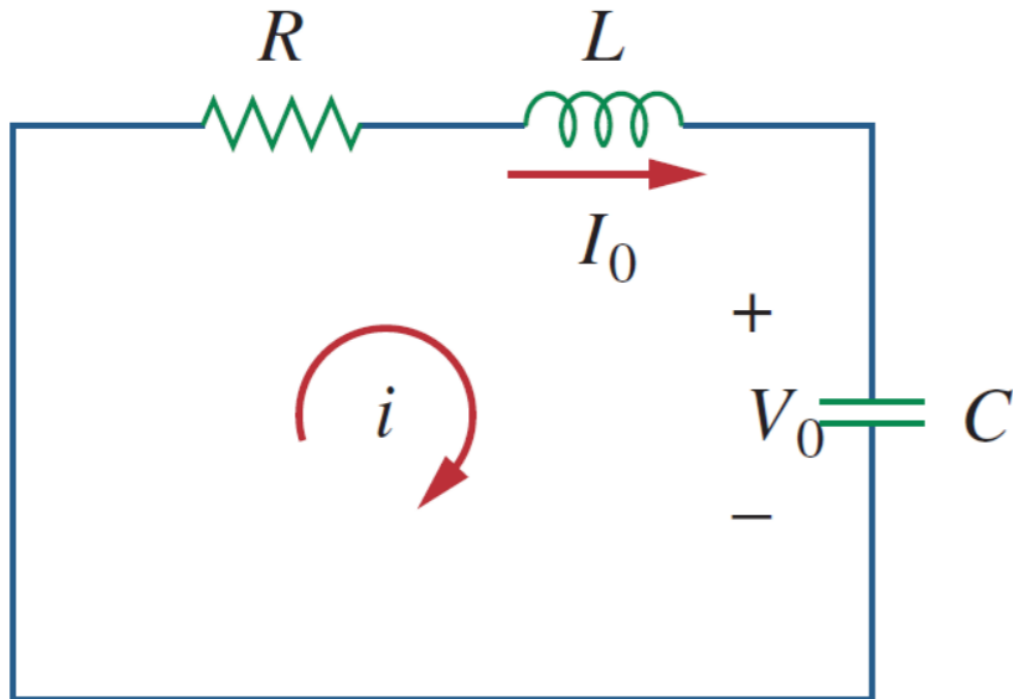Energiya kondensatorning boshlang'ich kuchlanishi U_0 va induktorning boshlang'ich toki kuchi I_0 bilan belgilanadi.



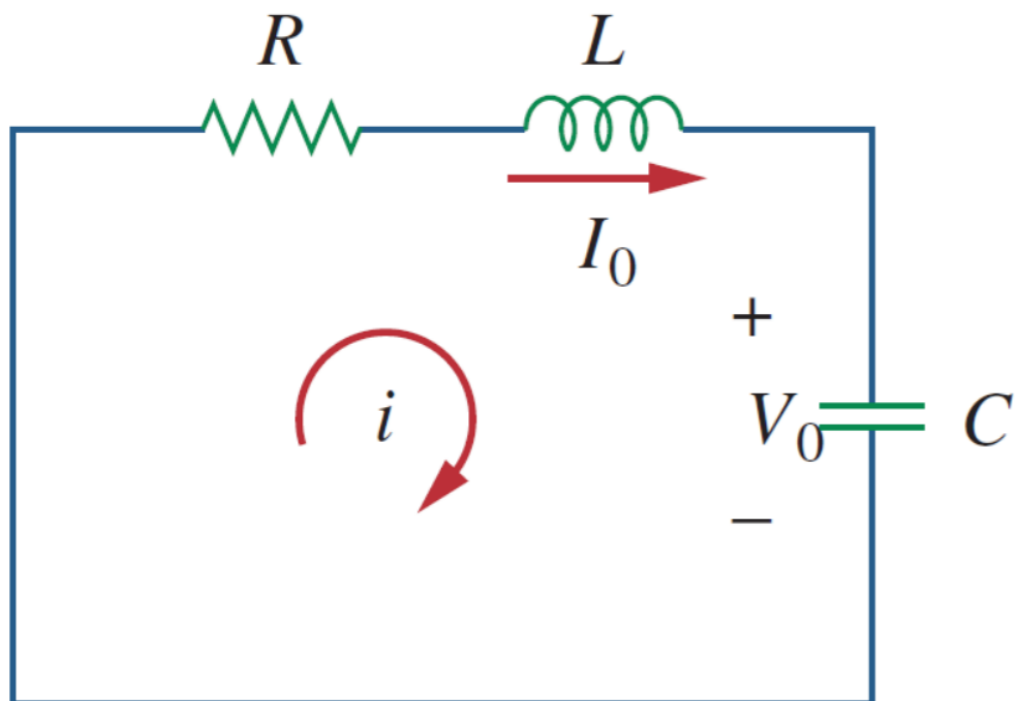8.4-rasm. Manbadan holi ketma-ket ulangan *RLC* zanjiri.



8.4-rasm.

Shunday qilib, $t = 0$ da,

$$u(0) = \frac{1}{C} \int_{-\infty}^0 i dt = U_0 \quad (8.2 a)$$

$$i(0) = I_0 \quad (8.2 b)$$

8.4-rasmdagi halqaga KVL ni qo'llaymiz.

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = 0 \quad (8.3)$$

Integralni yo'q qilish uchun biz t ga nisbatan differensiallaymiz va hadlarni o'zgartiramiz.

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \quad (8.4)$$

i ning boshlang‘ich qiymati (8.2b) tenglamada berilgan. (8.2a) va (8.3) tenglamalardan i hosilasining boshlang‘ich qiymatini olamiz. Ya’ni,

$$Ri(0) + L \frac{di(0)}{dt} + U_0 = 0 \quad \text{yoki,} \quad \frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + U_0) \quad (8.5)$$

(8.2b) va (8.5) tenglamalardagi ikkita boshlang‘ich shart bilan biz (8.4) tenglikni yechamiz. Birinchi tartibli zanjirlar bo‘yicha oldingi mavzudagi tajribamiz shuni ko‘rsatadiki, yechim eksponensial shaklda. Shunday qilib,

$$i = Ae^{st} \quad (8.6)$$

bu yerda: A va s aniqlanishi kerak bo‘lgan doimiylar.

Shunday qilib, (8.6) tenglamani (8.4) tenglamaga almashtiramiz.

$$As^2 e^{st} + \frac{AR}{L} s e^{st} + \frac{A}{LC} e^{st} = 0 \quad \text{yoki,} \quad Ae^{st} \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0 \quad (8.7)$$

$i = Ae^{st}$ biz topmoqchi bo‘lgan taxminiy yechim bo‘lgani uchun, faqat qavs ichidagi ifoda nolga teng bo‘lishi mumkin:

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad (8.8)$$

Bu kvadrat tenglama (8.4) differensial tenglamaning xarakteristik tenglamasi sifatida tanilgan, chunki tenglamaning ildizlari i ning xarakterini belgilaydi. (8.8) tenglamaning ikkita ildizi quyidagicha yoziladi.

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad (8.9 \text{ a})$$

$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad (8.9 \text{ b})$$

Ildizlarni ifodalashning yanada ixcham usuli.

$$s_{1,2} = -\alpha \pm \sqrt{(\alpha)^2 - \omega_0^2} \quad (8.10)$$

bu yerda:

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad (8.11)$$

s_1 va s_2 ildizlar sekundiga neperlar (Np/s) bilan o'lchanadigan tabiiy (natural) chastotalar deb ataladi, $1\text{Np}=0,868 \text{ bel} = 8,68 \text{ dB}$. Data source: [8] - <https://en.wikipedia.org/wiki/Neper>

ω_0 - rezonans chastotasi yoki qat'iy ravishda sekundiga radyanlarda (rad/s) ifodalangan so'nmagan tabiiy chastota sifatida tanilgan;

α sekundiga neperlarda ifodalangan neper chastotasi yoki so'ndiruvchi (damping) omili.

α va ω_0 (8.8) tenglamani ko‘rinishida yozish mumkin.

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \rightarrow s^2 + 2\alpha s + \omega_0^2 = 0 \quad (8.8 \text{ a})$$

s va ω_0 o‘zgaruvchilar biz mavzuning qolgan qismida muhokama qiladigan muhim miqdorlardir.

(8.10) tenglamadagi s ning ikkita qiymati i uchun ikkita mumkin bo‘lgan yechim mavjudligini ko‘rsatadi, ularning har biri (8.6) tenglamada qabul qilingan yechim shaklida bo‘ladi. Ya’ni,

$$s_{1,2} = -\alpha \pm \sqrt{(\alpha)^2 - \omega_0^2} \rightarrow \begin{aligned} i_1 &= A_1 e^{s_1 t}, & i_2 &= A_2 e^{s_2 t} \\ i &= A e^{st} \end{aligned} \quad (8.12)$$

Shunday qilib, ketma-ket ulangan RLC zanjirining tabiiy reaksiyasi.

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (8.13)$$

bu yerda A_1 va A_2 konstantalar tenglamadagi $i(0)$ va $di(0)/dt$ boshlang'ich qiymatlardan aniqlanadi.

$$i(0) = I_0 \quad \frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + U_0)$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

α va ω_0 yechimlarning uch turi mavjud:


1. Agar $\alpha > \omega_0$ bo'lsa, bizda yuqori so'ndirilgan holat mavjud;
2. Agar $\alpha = \omega_0$ bo'lsa, bizda kritik so'ndirilgan holat mavjud;
3. Agar $\alpha < \omega_0$ bo'sa, bizda quyi so'ndirilgan holat mavjud.

Ketma-ket ulangan *RLC* zanjirining tabiiy reaksiyasi:

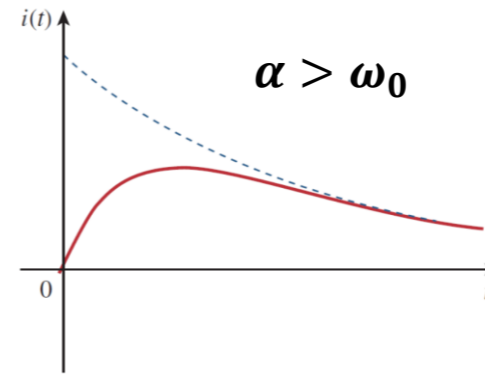1. Yuqori so'ndirilgan holat ($\alpha > \omega_0$) uchun:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{(\alpha^2 - \omega_0^2)}$$




$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \downarrow$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \downarrow$$

2. Kritik so'ndirilgan holat ($\alpha = \omega_0$) uchun:

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

$$s_{1,2} = -\alpha$$

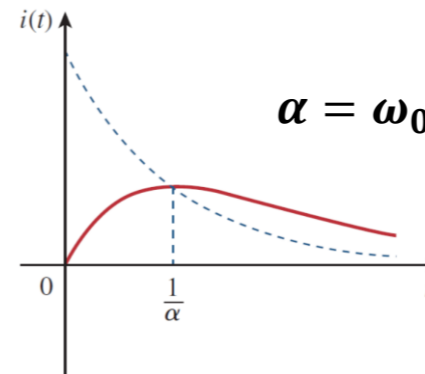

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

3. Quyi so'ndirilgan holat ($\alpha < \omega_0$) uchun:

$$i(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

$$j = \sqrt{-1} \text{ va } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$


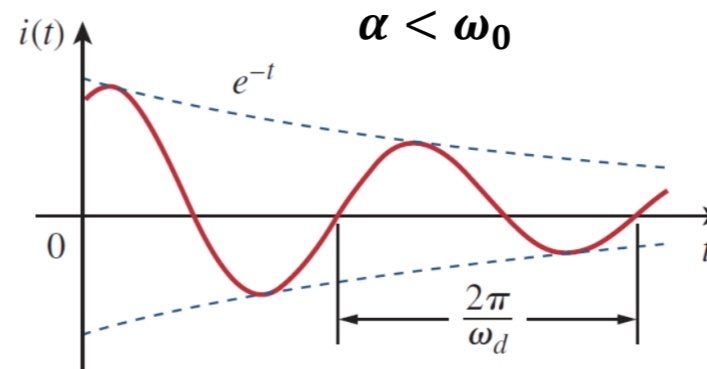


Photo source: [9] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 322.

8.5-rasm.

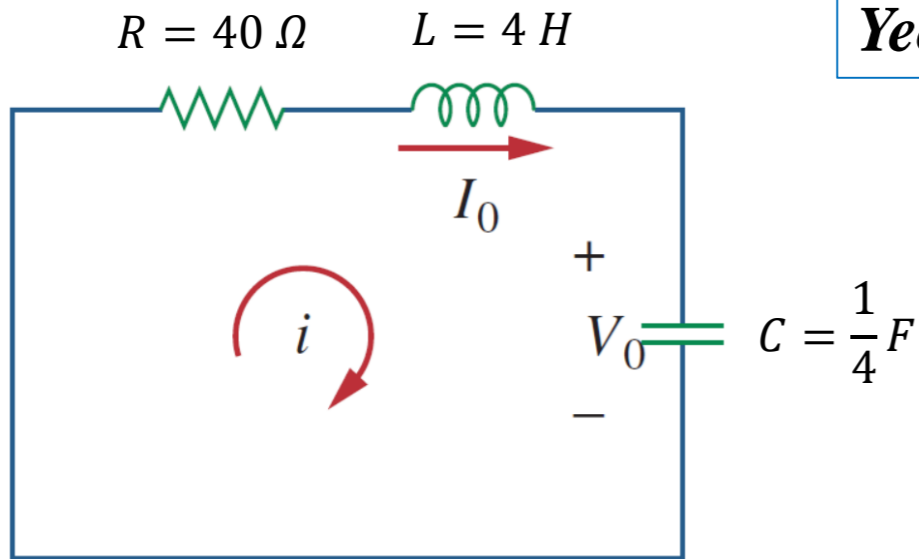8.3.1-masala: 8.4-rasmda zanjirning xarakterli ildizlarini hisoblang.

Tabiiy reaksiya yuqori soʻndirilganmi, quyi soʻndirilganmi yoki kritik soʻndirilganmi?



8.4-rasm.

Yechish:

$$\alpha = \frac{R}{2L} = \frac{40}{2(4)} = 5 \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \cdot \frac{1}{4}}} = 1$$

$\alpha > \omega_0$ - reaksiya yuqori soʻndirilgan


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{(\alpha)^2 - \omega_0^2} = -5 \pm \sqrt{25 - 1}$$

$$s_1 = -0,101, \quad s_2 = -9,899$$

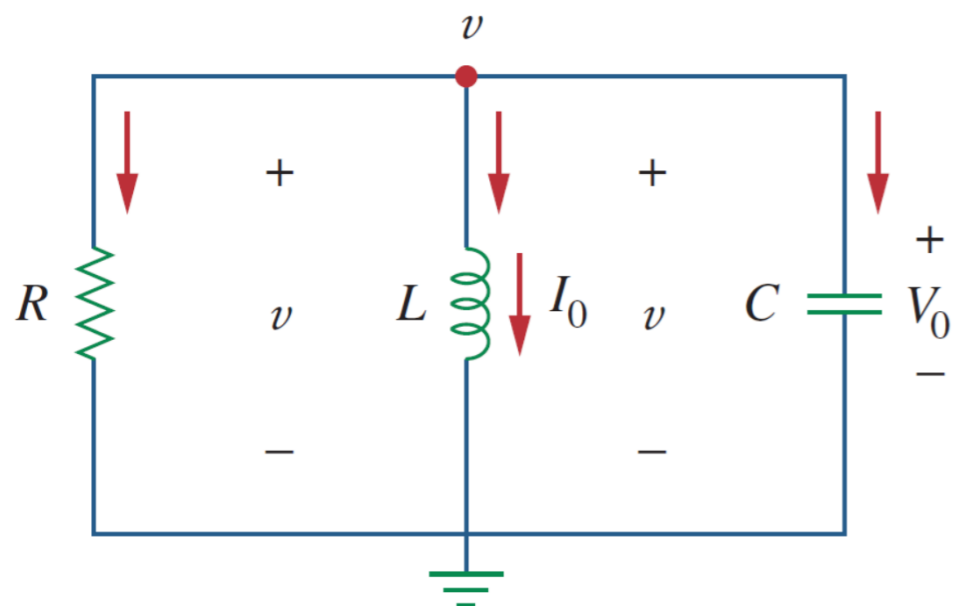8.4. Manbadan holi parallel ulangan qarshilik, induktor va kondensator (RLC) zanjiri.

Parallel *RLC* zanjirlari ko‘plab amaliy dasturlarda ayniqsa aloqa tarmoqlarida keng qo‘llaniladi.




8.6-rasm. Manbadan holi parallel ulangan *RLC* zanjiri.

Dastlabki induktor tok kuchi I_0 va dastlabki kondensator kuchlanishi U_0 deb faraz qilaylik,

$$i(0) = I_0 = \frac{1}{L} \int_{-\infty}^0 u(t) dt \quad (8.27 \text{ a})$$

$$u(0) = U_0 \quad (8.27 \text{ b})$$

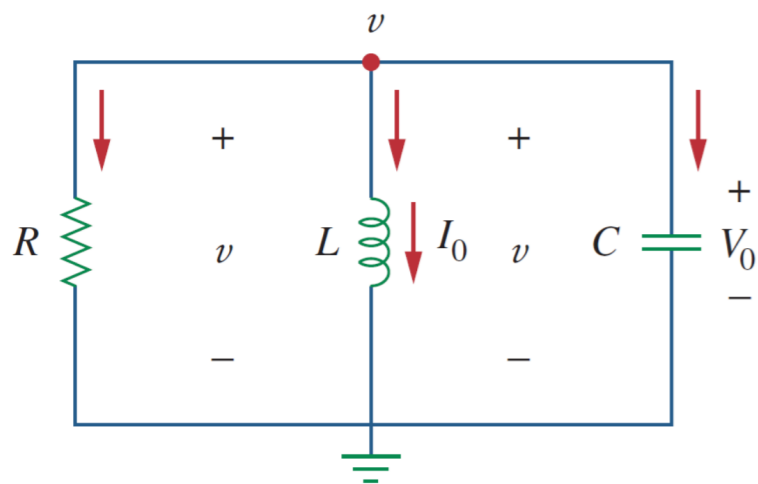Ucha element parallel bo‘lganligi sababli, ular bo‘ylab bir xil u kuchlanishga ega.



Passiv belgi konvensiyasiga ko'ra, tok kuchi har bir elementga kiradi.

Shunday qilib, yuqori tugunda KCLni qo'llaymiz:

$$i_R + i_L + i_C = 0$$

$$\frac{u}{R} + \frac{1}{L} \int_{-\infty}^t u(\tau) d\tau + C \frac{du}{dt} = 0 \quad (8.28)$$

Differensiallash orqali quyidagi ifodaga ega bo'lamiz.

$$C \frac{d^2 u}{dt^2} + \frac{1}{R} \frac{du}{dt} + \frac{1}{L} u = 0 \quad (8.29)$$

Xarakteristik tenglamani birinchi hosilani s ga, ikkinchi hosilani s^2 ga almashtirib olamiz.

$$u = Ae^{st}, \quad CA s^2 e^{st} + \frac{1}{R} A s e^{st} + \frac{1}{L} A e^{st} = 0, \quad A e^{st} \left(C s^2 + \frac{1}{R} s + \frac{1}{L} \right) = 0$$

$$C s^2 + \frac{1}{R} s + \frac{1}{L} = 0 \quad (8.29a)$$

Hosil bo‘lgan (8.29a) tenglamani C ga bo‘lish natijasida quyidagi tenglama hosil bo‘ladi.

$$Cs^2 + \frac{1}{R}s + \frac{1}{L} = 0 / C \rightarrow s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \quad (8.30)$$

Xarakteristik tenglamaning ildizlari,

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad \text{yoki,} \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad (8.31)$$

bu yerda:

$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad (8.32)$$

Parallel ulangan RLC zanjirining tabiiy reaksiyasi:

1. Yuqori so'ndirilgan holat ($\alpha > \omega_0$) uchun:

$$u(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{(\alpha^2 - \omega_0^2)}$$

2. Kritik so'ndirilgan holat ($\alpha = \omega_0$) uchun:

$$u(t) = (A_1 + A_2 t) e^{-\alpha t}$$


$$s_{1,2} = -\alpha$$

3. Quyi so'ndirilgan holat ($\alpha < \omega_0$) uchun:

$$u(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$$


$$s_{1,2} = -\alpha \pm j\omega_d$$
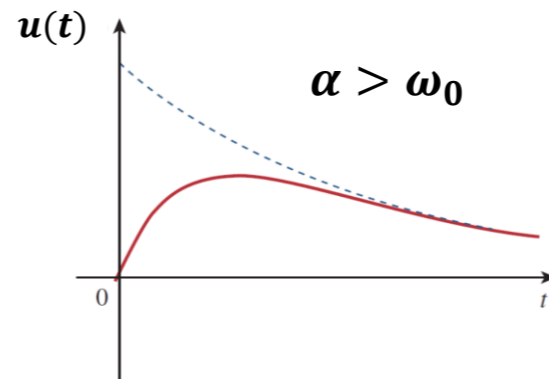
$$j = \sqrt{-1} \text{ va } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$



$$\frac{d^2 u}{dt^2} + \frac{1}{RC} \frac{du}{dt} + \frac{1}{LC} u = 0 \downarrow$$

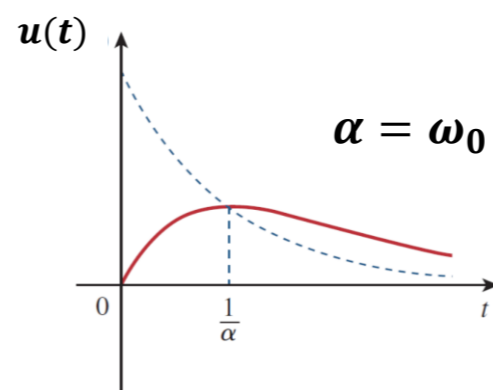
$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \downarrow$$



$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

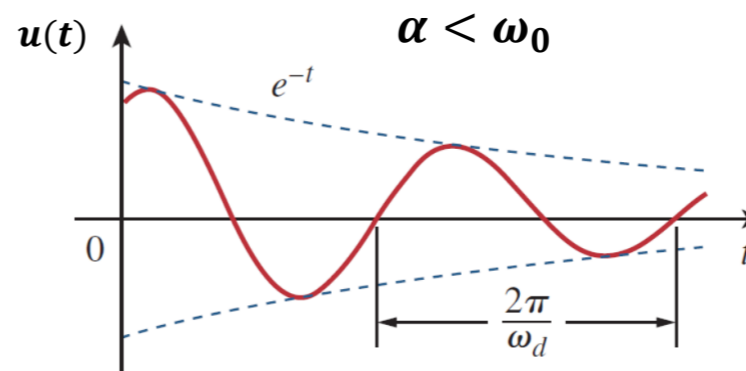


8.7-rasm.

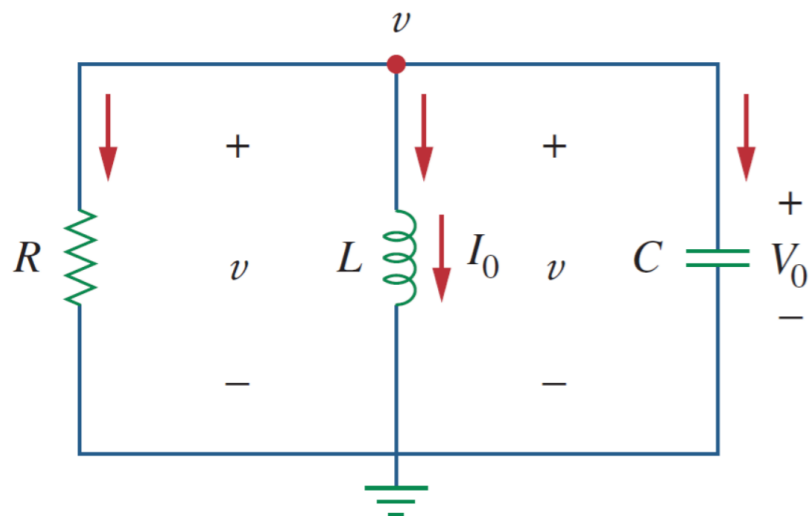8.4.1-masala: 8.6-rasmning parallel zanjiridagi $t > 0$ uchun $u(t)$ toping.

$u(0) = 5 V, i(0) = 0 A, L = 1 H$ va $C = 10 mF$ deb faraz qiling.

$R = 1,923 \Omega, R = 5 \Omega$ va $R = 6,25 \Omega$ holatlarni ko'rib chiqing.



8.6-rasm.

Yechish:

1-holat uchun $R = 1,923 \Omega$ bo'lganda.

1. $t < 0, u(0)$ va $i(0)$.

2. $\frac{du(0)}{dt}$ ni KCL qo'llanadi.

$$i_R(t) + i(t) + i_C(t) = 0;$$

$u(0) = 5 V, i(0) = 0 A$

$$i_R(0) + i(0) + i_C(0) = 0; \quad \frac{U_0}{R} + I_0 + C \frac{du(0)}{dt} = 0; \quad \frac{5}{1,923} + 0 + 10 mF \frac{du(0)}{dt} = 0;$$

$$10 mF \frac{du(0)}{dt} = -2,6;$$

$$\frac{du(0)}{dt} = -260 \frac{V}{s}.$$

$\alpha > \omega_0$ bu holda reaksiya yuqori so'ndirilgan.

3. α, ω_0

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 1,923 \cdot 10 \cdot 10^{-3}} = 26; \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \cdot 10 \cdot 10^{-3}}} = 10;$$

4. $u(t)=?, s_{1,2}$ yoki ω_d v.h.k.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2};$$

$$s_{1,2} = -26 \pm \sqrt{26^2 - 10^2} = -2; -50$$

$$u(t) = A_1 e^{-2t} + A_2 e^{-50t}$$

5. A_1 va $A_2 = ?$

$$t = 0 \downarrow$$

$$u(0) = A_1 + A_2$$

$$5 = A_1 + A_2$$

$u(t) = A_1 e^{-2t} + A_2 e^{-50t}$ tenglamani differensiallaymiz.

$$\frac{du}{dt} = -2A_1 e^{-2t} - 50A_2 e^{-50t};$$

$$t = 0 \downarrow$$

$$-260 = -2A_1 - 50A_2$$


$$\begin{cases} 5 = A_1 + A_2 & /(\cdot 2) \\ -260 = -2A_1 - 50A_2 \end{cases} \rightarrow \begin{cases} -250 = -48A_2 \downarrow \\ A_2 = 5,208 \\ 10 = 2A_1 + 2A_2 \\ -260 = -2A_1 - 50A_2 \end{cases} \rightarrow \begin{cases} A_1 = -0,2083 \end{cases}$$

$$u(t) = -0,2083 e^{-2t} + 5,208 e^{-50t} V$$

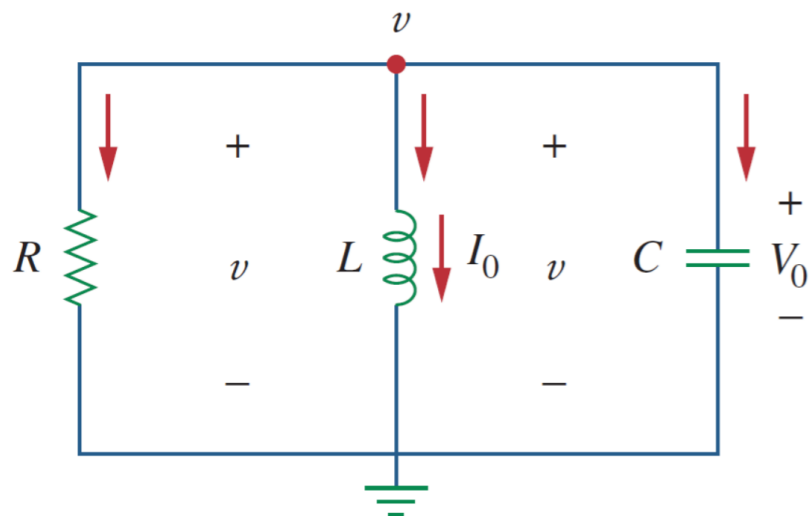8.4.1-masala: 8.6-rasmning parallel zanjiridagi $t > 0$ uchun $u(t)$ toping.

$u(0) = 5 V, i(0) = 0 A, L = 1 H$ va $C = 10 mF$ deb faraz qiling.

$R = 1,923 \Omega, R = 5 \Omega$ va $R = 6,25 \Omega$ holatlarni ko'rib chiqing.



8.6-rasm.

Yechish:

1-holat uchun $R = 5 \Omega$ bo'lganda.

1. $t < 0, u(0)$ va $i(0)$.

$u(0) = 5 V, i(0) = 0 A$

2. $\frac{du(0)}{dt}$ ni KCL qo'llanadi. $i_R(t) + i(t) + i_C(t) = 0;$

$$i_R(0) + i(0) + i_C(0) = 0; \quad \frac{U_0}{R} + I_0 + C \frac{du(0)}{dt} = 0; \quad \frac{5}{5} + 0 + 10 mF \frac{du(0)}{dt} = 0;$$

$$10 mF \frac{du(0)}{dt} = -1; \quad \frac{du(0)}{dt} = -100 \frac{V}{s}.$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 5 \cdot 10 \cdot 10^{-3}} = 10; \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \cdot 10 \cdot 10^{-3}}} = 10;$$

$\alpha = \omega_0$ bu holda reaksiya kiritik so'ndirilgan.

4. $u(t)=?, s_{1,2}$ yoki ω_d v.h.k.

5. A_1 va $A_2 = ?$

$u(t) = (A_1 + A_2 t)e^{-10t}$ tenglamani differensiallaymiz. $\begin{cases} 5 = A_1 & /(\cdot 10) \\ -100 = -10A_1 + A_2 \end{cases} \rightarrow$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2};$$

$$\alpha = \omega_0 = 10; \quad s_1 = s_2 = -10;$$

$$u(t) = (A_1 + A_2 t)e^{-\alpha t}$$

$$u(t) = (A_1 + A_2 t)e^{-10t}; \quad \frac{du}{dt} = e^{-10t}(A_2) + (A_1 + A_2 t)(-10)e^{-10t} =$$

$$= (-10A_1 - 10A_2 t + A_2)e^{-10t}$$

$$t = 0 \downarrow \\ u(0) = A_1$$

$$5 = A_1$$

$$t = 0 \downarrow$$

$$-100 = -10A_1 + A_2$$


$$+ \begin{cases} 50 = 10A_1 \\ -100 = -10A_1 + A_2 \end{cases} \rightarrow \\ A_2 = -50$$

$$u(t) = (5 - 50t)e^{-10t} V$$

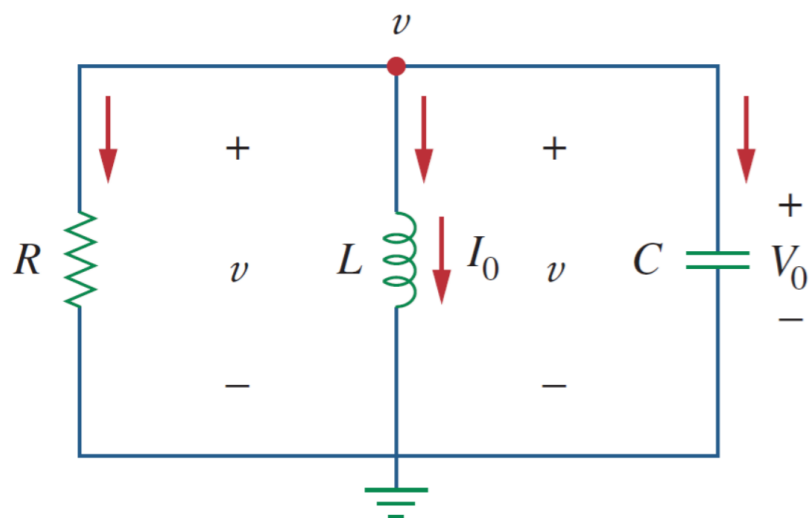8.4.1-masala: 8.6-rasmning parallel zanjiridagi $t > 0$ uchun $u(t)$ toping.

$u(0) = 5 V, i(0) = 0 A, L = 1 H$ va $C = 10 mF$ deb faraz qiling.

$R = 1,923 \Omega, R = 5 \Omega$ va $R = 6,25 \Omega$ holatlarni ko'rib chiqing.



8.6-rasm.

Yechish:

1-holat uchun $R = 6,25 \Omega$ bo'lganda.

1. $t < 0, u(0)$ va $i(0)$.

2. $\frac{du(0)}{dt}$ ni KCL qo'llanadi.

$$i_R(t) + i(t) + i_C(t) = 0;$$

$u(0) = 5 V, i(0) = 0 A$

$$i_R(0) + i(0) + i_C(0) = 0; \quad \frac{U_0}{R} + I_0 + C \frac{du(0)}{dt} = 0; \quad \frac{5}{6,25} + 0 + 10 mF \frac{du(0)}{dt} = 0;$$

$$10 mF \frac{du(0)}{dt} = -0,8;$$

$$\frac{du(0)}{dt} = -80 \frac{V}{s}$$

$\alpha = \omega_0$ bu holda reaksiya quyida so'ndirilgan.

3. α, ω_0

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 6,25 \cdot 10 \cdot 10^{-3}} = 8; \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \cdot 10 \cdot 10^{-3}}} = 10;$$

4. $u(t)=?, s_{1,2}$ yoki ω_d v.h.k.

5. A_1 va $A_2 = ?$

$u(t) = e^{-8t} [A_1 \cos 6t + A_2 \sin 6t]$ tenglamani differensiallaymiz.

$$s_{1,2} = -\alpha \pm j\omega_d = -8 \pm j6;$$

$$u(t) = e^{-8t} [A_1 \cos 6t + A_2 \sin 6t]$$

$$\frac{du}{dt} = (-8A_1 \cos 6t - 8A_2 \sin 6t - 6A_1 \sin 6t + 6A_2 \cos 6t)e^{-8t}$$

$$\begin{cases} 5 = A_1 & /(\cdot 8) \\ -80 = -8A_1 + 6A_2 \end{cases} \rightarrow \begin{cases} 40 = 8A_1 \\ -80 = -8A_1 + 6A_2 \end{cases}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^2 - 8^2} = 6;$$

$t = 0 \downarrow$

$$u(0) = A_1$$

$t = 0 \downarrow$

$$-80 = -8A_1 + 6A_2$$


$$A_2 = 6,67$$

$$u(t) = e^{-\alpha t} [A_1 \cos \omega_d t + A_2 \sin \omega_d t]$$


$$5 = A_1$$

$$u(t) = (5 \cos 6t - 6,667 \sin 6t)e^{-8t} V$$

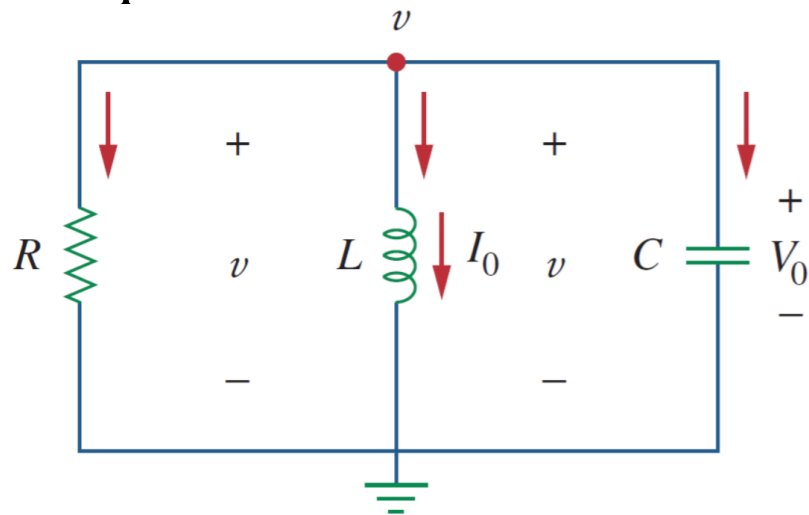R qiymatini oshirib, soʻndirish darajasi pasayadi va reaksiyalar farqlanadi.



8.6-rasm.

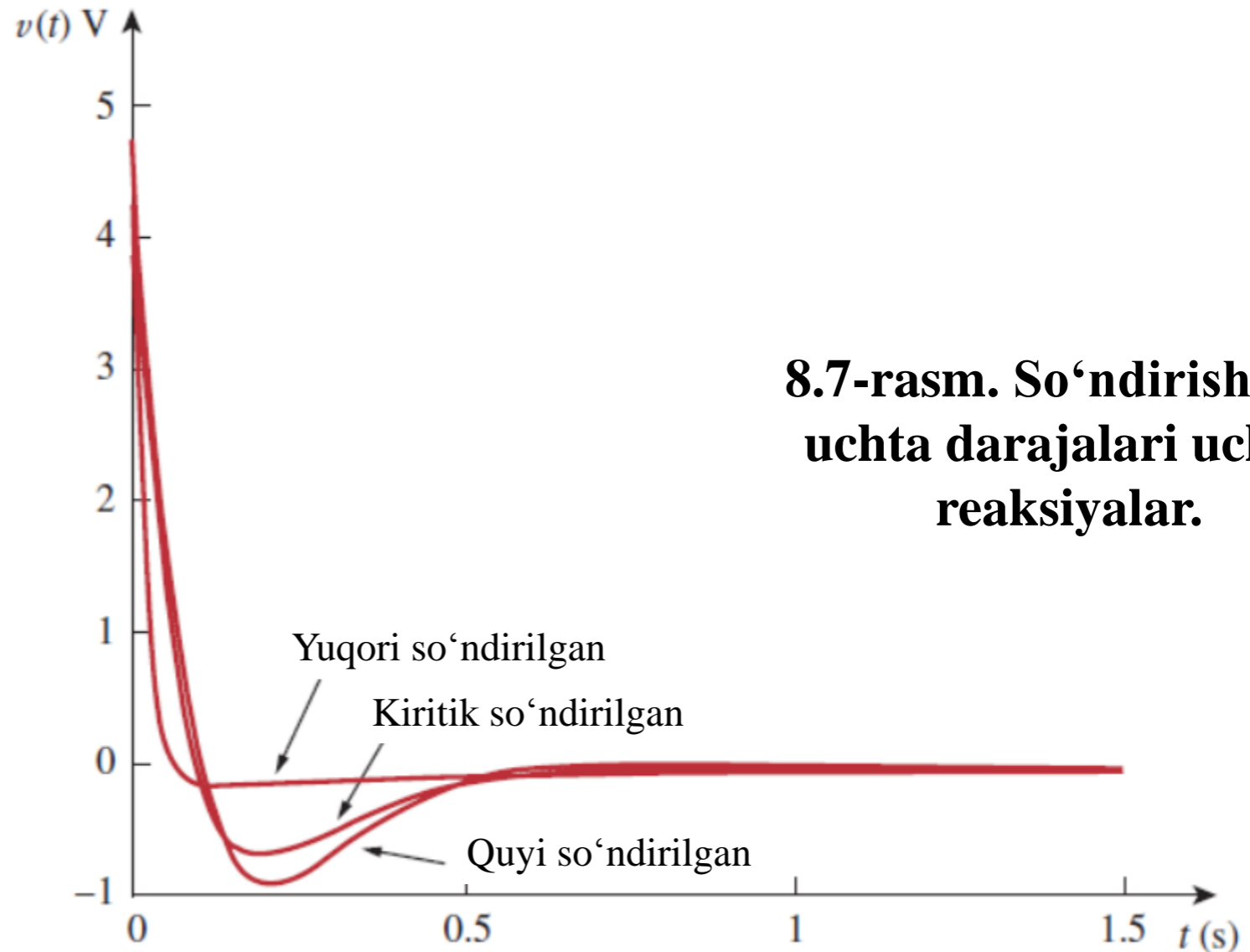

8.7-rasm. Soʻndirishning uchta darajalari uchun reaksiyalar.

Photo source: [11] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 329.



FOYDALANILGAN MANBALAR:

8. <https://en.wikipedia.org/wiki/Neper>
9. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 322.
10. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 326.
11. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 329.



*E'TIBORINGIZ
UCHUN
RAHMAT!!!*