


**9-Mavzu: O'zgaruvchan tok zanjiri. Sinusoidlar va fazalar (*davomi*).**

(9<sup>th</sup> Topic: AC Circuit. Sinusoids and Phasors.)

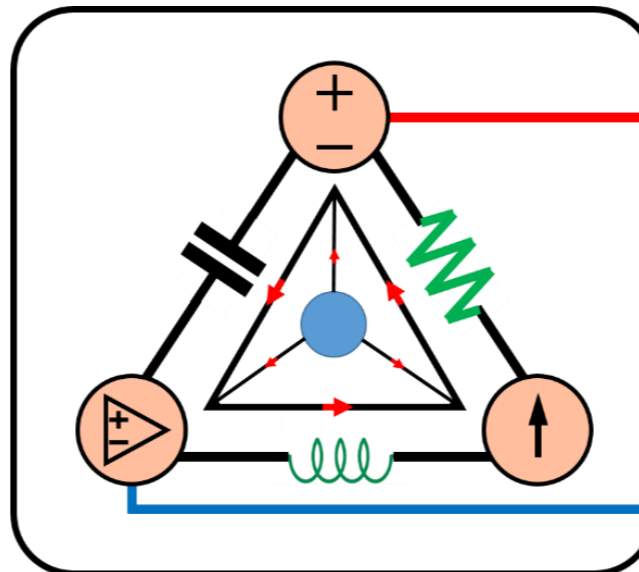**9-Mavzuning 4-qismi**

(4<sup>th</sup> part of the 9<sup>th</sup> Topic)

*12-hafta uchun*  
*For the 12<sup>th</sup> week*



**Lecturer: Ph.D., Yusupov Sarvarbek**

*Toshkent Kimyo Xalqaro Universiteti*  
*“Mashinasozlik texnologiyasi” kafedrası*  
*Toshkent shahri, Usmon Nosir, 156-uy.*



## 9-Mavzu: O'zgaruvchan tok zanjiri. Sinusoidlar va fazalar (*davomi*).

(9<sup>th</sup> Topic: AC Circuit. Sinusoids and Phasors.)

### O'quv rejasi:

9.5. Qarshilik va o'tkazuvchanlik (impidance and admittance).

9.6. Chastotalar sohasida Kirxgof qonunlari.

**9.7. Qarshilik kombinatsiyalari.**


**9.8. Qo'llanilishi.**

## 9.7. Qarshilik kombinatsiyalari.

$N$  ta ketma-ket ulangan impedenslarni ko‘rib chiqaylik. Xuddi shu tok kuchi  $I$  impedenslar orqali oqadi. Kontur bo‘ylab KVLni qo‘llaymiz.

$$U = U_1 + U_2 + \dots + U_N = I(Z_1 + Z_2 + \dots + Z_N) \quad (9.58)$$

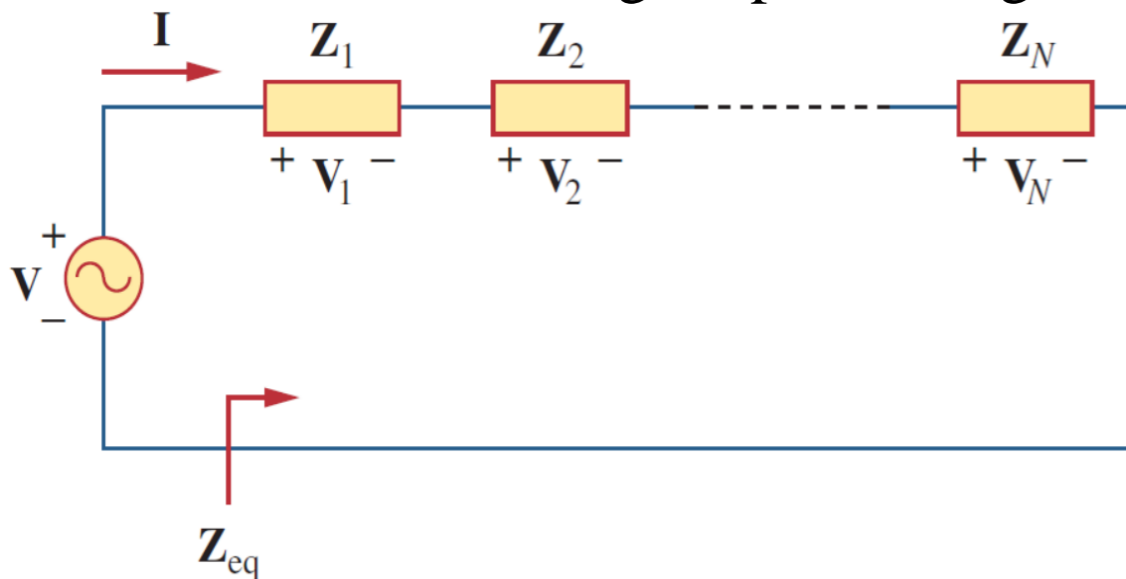Kirish terminalidagi impedensning ekvivalenti quyidagicha aniqlanadi.



$$Z_{um} = Z_{eq} = \frac{U}{I} = Z_1 + Z_2 + \dots + Z_N$$

yoki,

$$Z_{um} = Z_1 + Z_2 + \dots + Z_N \quad (9.59)$$


ketma-ket bog‘langan impedenslarning umumiy yoki ekvivalent impedensi individual impedenslarning yig‘indisi ekanligini ko‘rsatadi.

**9.17-rasm. Ketma-ket ulangan  $N$  ta impedenslar.**

Photo source: [18] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., - 2013. – p 390.

Bu qarshiliklarning ketma-ket ulanishiga o‘xshaydi.

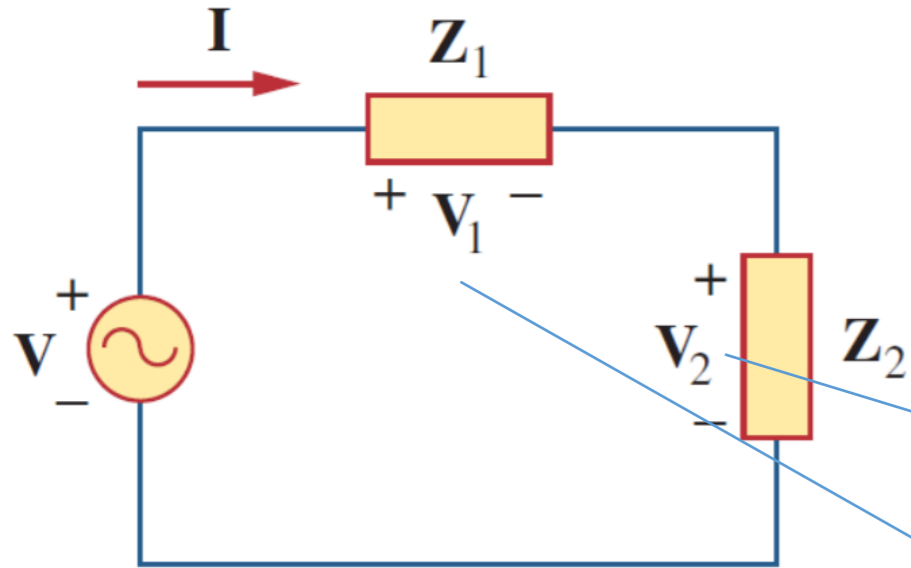$N=2$  bo‘lsa, impedanslar orqali to kuchi quyidagicha hisoblanadi.



$$I = \frac{U}{Z_1 + Z_2} \quad (9.60)$$

Shunday qilib,  $U_1 = Z_1 I$  va  $U_2 = Z_2 I$ , u holda kuchlanishni bo‘linish qoidasi quyidagicha yoziladi.

**9.18-rasm. Kuchlanishni bo‘linishi.**

$$U_1 = \frac{Z_1}{Z_1 + Z_2} U;$$

$$U_2 = \frac{Z_2}{Z_1 + Z_2} U. \quad (9.61)$$


**Photo source:** [19] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., - 2013. – p 391.

$N$  ta parallel ulangan impedensning ekvivalent impedensini olishimiz mumkin.

Har bir impedensdagi kuchlanish bir xil.

Tugunda KCL ni qo‘llaymiz,
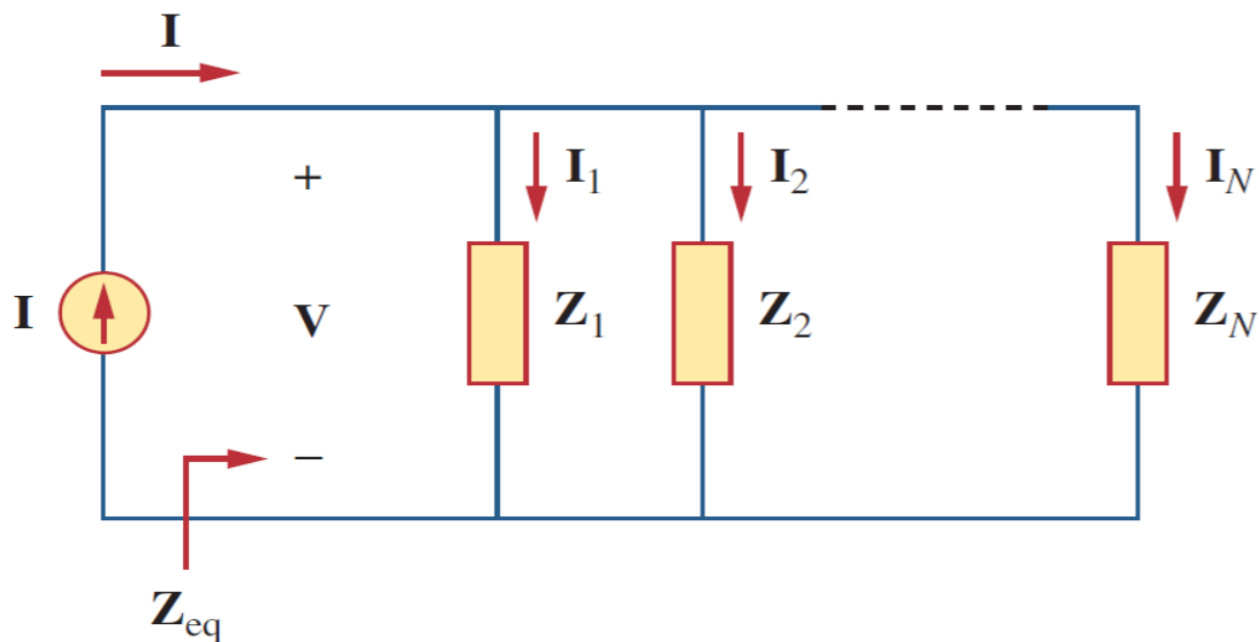
$$I = I_1 + I_2 + \dots + I_N = U \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right) \quad (9.62)$$



**9.19-rasm. Parallel ulangan  $N$  ta impedenslar.**

Kirish terminalidagi impedensning ekvivalenti quyidagicha aniqlanadi.

$$\frac{1}{Z_{um}} = \frac{1}{Z_{eq}} = \frac{I}{U} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \quad (9.63)$$


Ekvivalent admittensi esa,

$$Y_{um} = Y_{eq} = Y_1 + Y_2 + \dots + Y_N \quad (9.64)$$

$N=2$  bo'lsa, ekvivalent impedans aylanadi.

$$Z_{um} = \frac{1}{Y_{um}} = \frac{1}{Y_1+Y_2} = \frac{1}{\frac{1}{Z_1}+\frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1+Z_2} \quad (9.65)$$

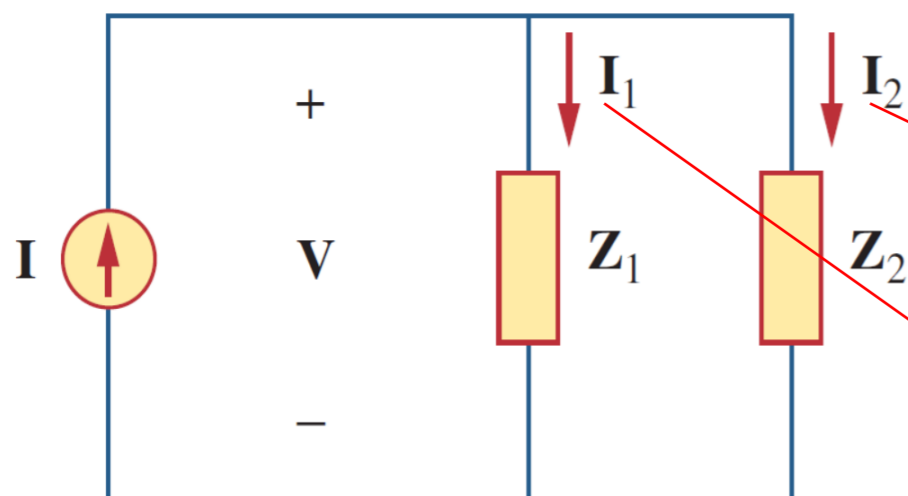Shunday qilib,  $U = Z_{um}I = I_1 Z_1 = I_2 Z_2$




Impidenslardagi tok kuchilarining bo'linish qoidasi quyidagicha yoziladi.

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I \quad (9.66)$$

**9.20-rasm. Tok kuchini bo'linishi.**

Photo source: [19] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., - 2013. – p 391.

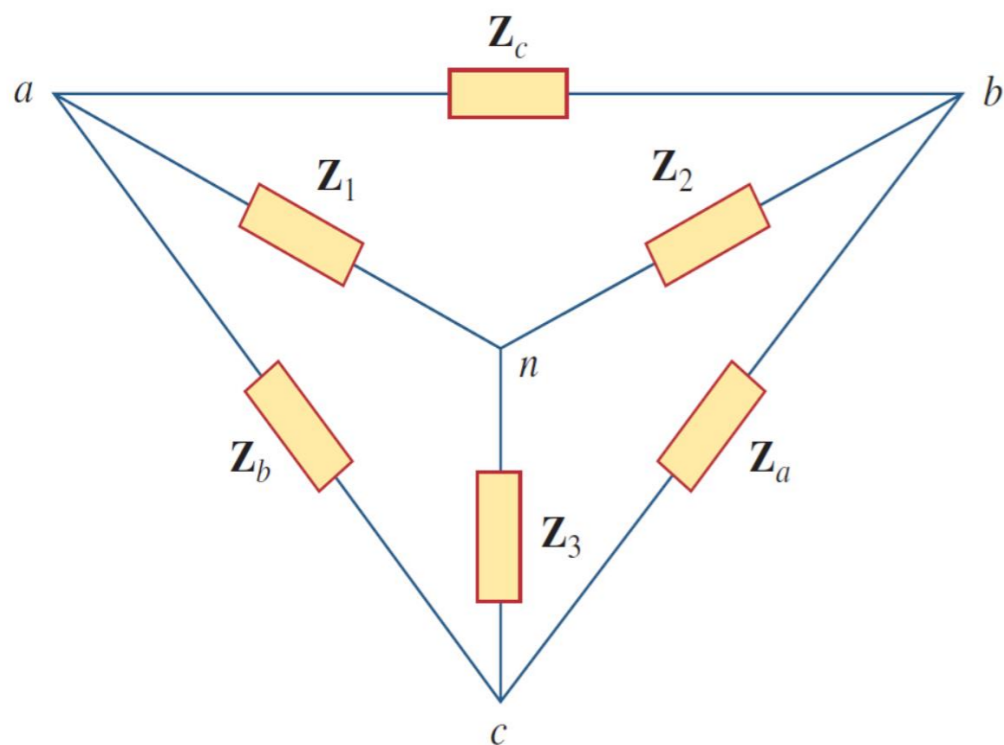Rezistorli zanjirlarga qoʻllagan delta-to-wye va wye-to-delta transformatsiyalari impedenslar uchun ham amal qiladi.



**9.21-rasm. Y va Δ qatlamli tarmoqlar.**

**Photo source:** [20] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., - 2013. – p 392.

**Y – Δ konvertatsiyasi:**

$$\begin{aligned}
 Z_a &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1} \\
 Z_b &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2} \\
 Z_c &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}
 \end{aligned}
 \tag{9.67}$$

**Δ – Y konvertatsiyasi:**

$$\begin{aligned}
 Z_1 &= \frac{Z_b Z_c}{Z_a + Z_b + Z_c} \\
 Z_2 &= \frac{Z_c Z_a}{Z_a + Z_b + Z_c} \\
 Z_3 &= \frac{Z_a Z_b}{Z_a + Z_b + Z_c}
 \end{aligned}
 \tag{9.68}$$

$\Delta$  yoki Y zanjiri, agar u uchta tarmoqda teng impedenslarga ega bo'lsa, muvozanatli deyiladi.

$\Delta$  - Y zanjir muvozanatlanganda (9.67) va (9.68) tenglamalar quyidagicha bo'ladi.


$$Z_{\Delta} = 3Z_Y \text{ yoki, } Z_Y = \frac{1}{3}Z_{\Delta} \quad (9.69)$$

bu yerda:  $Z_Y = Z_1 = Z_2 = Z_3$  va  $Z_{\Delta} = Z_a = Z_b = Z_c$ .

O'zgaruvchan tok zanjirlari uchun kuchlanishni bo'linishi, tok kuchini bo'linishi, zanjirni qisqartirish, impedens ekvivalenti va transformatsiya tamoyillari tahlil qilindi.

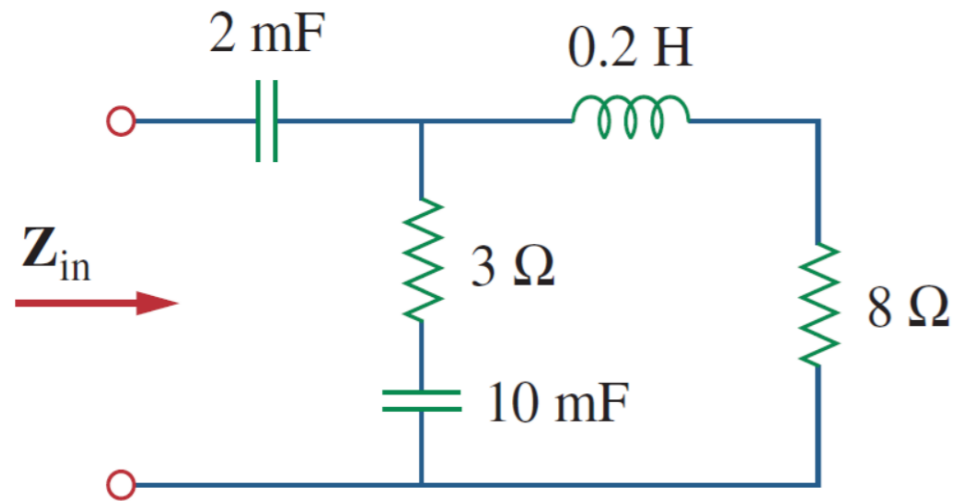**9.7.1-masala:** 9.22-rasmdagi zanjirning kirish impedansini toping. Faraz qilaylik, zanjir

$\omega = 50 \text{ rad/s}$  da ishlaydi.



**Yechish:**

Zanjir elementlarini chastota sohasiga o'tkazib olamiz.

$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j50 \cdot 2 \cdot 10^{-3}} = -j10 \Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \cdot 10 \cdot 10^{-3}} = (3 - j2) \Omega$$

$$Z_3 = 8 + j\omega L = 8 + j50 \cdot 0,2 = (8 + j10) \Omega$$

**9.22-rasm.**

Kiruvchi impedans,

$$Z_{in} = Z_1 + Z_2 || Z_3 = -j10 + \frac{(3 - j2)(8 + j10)}{11 + j8} = -j10 + \frac{(44 + j14)(11 - j8)}{11^2 + 8^2} = -j10 + 3,22 - j1,07 \Omega$$

$$\boxed{Z_{in} = 3,22 - j11,07 \Omega}$$

## 9.8. Qo'llanilishi.


O'zgarmas tok sharoitlarida  $RC$ ,  $RL$  va  $RLC$  zanjirlaridan foydalanishni ko'rib chiqdik. Bu zanjrlar ham o'zgaruvchan toklarda ishlatiladi.

Ularning o'zaro ulanish tartiblari, fazani o'zgartirish zanjirlari, filtrlar, rezonans zanjirlar, o'zgaruvchan tok ko'prigi zanjirlari va transformatorlarda mavjud hisoblanadi.


Quyida ikkita holatlarni ko'rib chiqamiz:

- $RC$  fazasini o'zgartirish zanjirlari;
- O'zgaruvchan tok ko'prigi zanjirlari.

### 9.8.1. Faza o'zgartirgichlar.

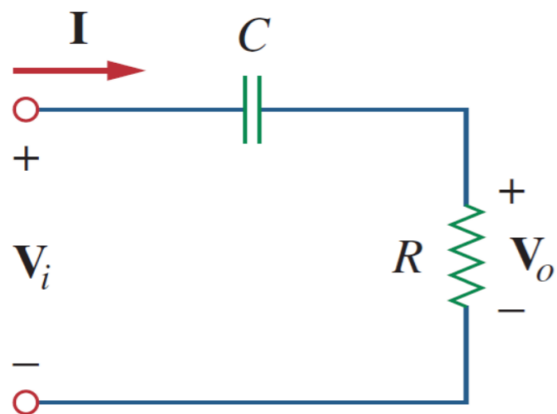

a) yetakchi chiqish;

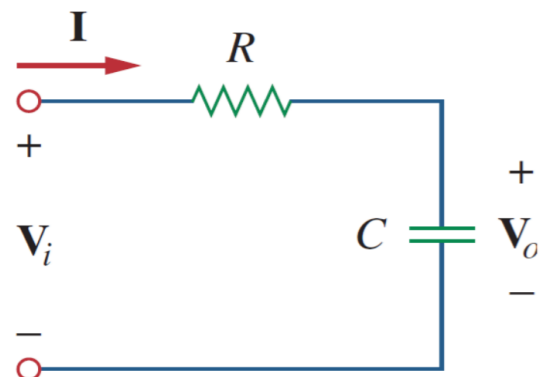


b) ortda qoladigan chiqish.

#### 9.23-rasm. Ketma-ket ulangan RC faza o'zgartirgich zanjiri:

Fazani o'zgartirish zanjiri ko'pincha zanjirga kiruvchi faza almashinuvini tuzatish yoki maxsus kerakli effektlarni yaratish uchun ishlatiladi.

RC zanjiri bu maqsad uchun mos keladi, chunki uning sig'imi qo'llaniladigan kuchlanishni zanjir tok kuchiga olib keladi.

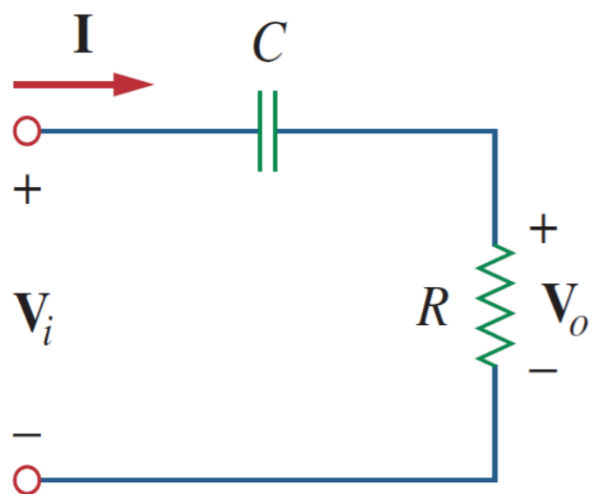Ikkita ko'p ishlatiladigan RC zanjiri 9.22-rasmda ko'rsatilgan (*RL zanjirlari yoki har qanday reaktiv zanjirlar ham xuddi shu maqsadga xizmat qilishi mumkin*).



a) yetakchi chiqish;

zanjirdagi tok kuchi  $I$  qo'llaniladigan kuchlanish  $U_{in}$  ni ba'zi bir faza burchagi  $\theta$  bilan olib boradi, bu yerda  $0 < \theta < 90^\circ$ ,  $R$  va  $C$  qiymatlariga bog'liq.

Agar  $X_C = -1/\omega C$  bo'lsa, u holda umumiy impedans  $Z = R + jX_C$  bo'ladi va fazaning siljishi quyidagicha hisoblanadi:

$$\theta = \tan^{-1} \frac{X_C}{R} \quad (9.70)$$


Bu shuni ko'rsatadiki, faza almashinuvi miqdori  $R$ ,  $C$  va ish chastotasi qiymatlariga bog'liq.

Rezistor bo‘ylab chiqish kuchlanishi  $U_0$  tok kuchi bilan fazada bo‘lgani uchun, 9.24-rasm, *a* da ko‘rsatilganidek,  $U_0$   $U_i$  dan oldinda boradi (musbat faza siljishi).

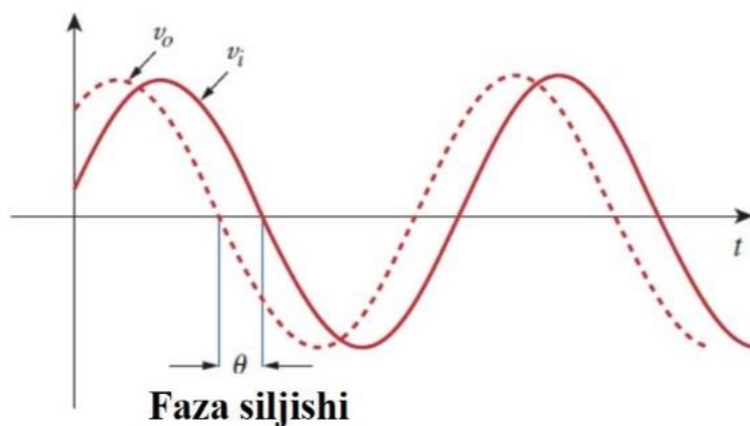
9.24-rasm, *b* da chiqish kondensator bo‘ylab olinadi.

$I \rightarrow U_i$  dan  $\theta$  ga oldinda boradi.

$C$  dagi  $u_o(t)$   $u_i(t)$  dan kechikadi.



a) oldinga chiqish,

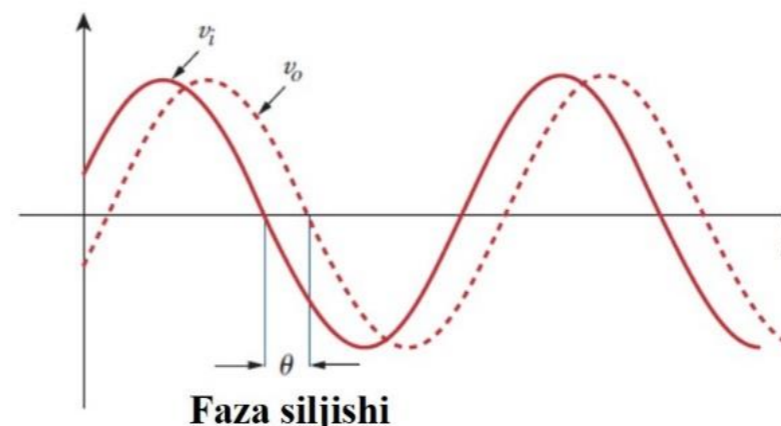


b) kechikish bilan chiqish.



### 9.24-rasm. *RC* davrlarida faza siljishi.

**Photo source:** [21] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 396.
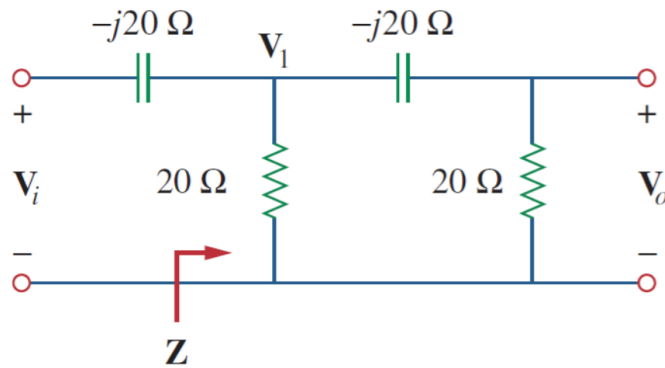
### 9.8.1-masala: $90^\circ$ yetakchi fazani ta'minlash uchun RC zanjirini loyihalang.



9.25-rasm.

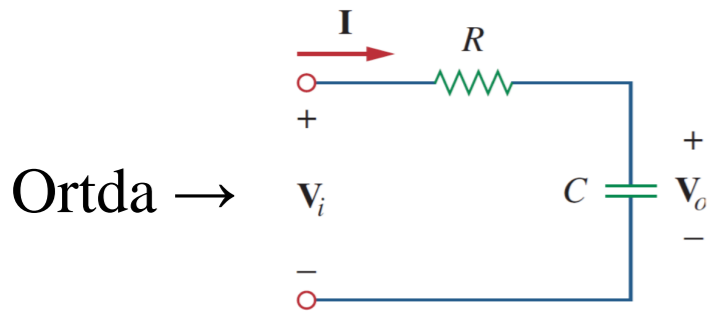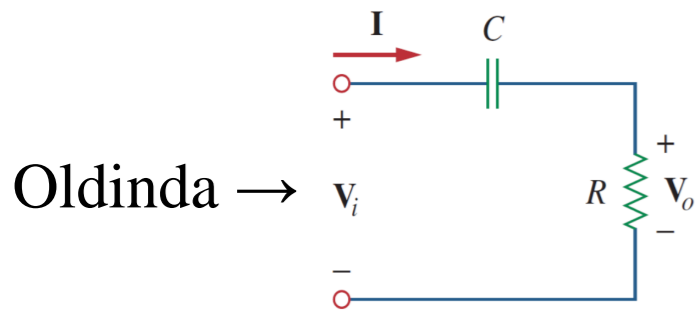

**Yechish:**

$$R = |X_C| = 20 \Omega;$$

$$\theta = \tan^{-1} \frac{X_C}{R} \rightarrow \theta = \tan^{-1} 1 \rightarrow \theta = 45^\circ$$

$$Z = 20 \parallel (20 - j20) = \frac{20(20 - j20)}{40 - j20} = 12 - j4 \Omega$$

Kuchlanishni bo'linish qoidasi,

$$U_1 = \frac{Z}{Z - j20} U_i = \frac{12 - j4}{12 - j24} U_i = \frac{\sqrt{2}}{3} \angle 45^\circ U_i \quad (9.8.1)$$

va

$$U_0 = \frac{20}{20 - j20} U_i = \frac{\sqrt{2}}{3} \angle 45^\circ U_i \quad (9.8.2)$$

(9.8.1) tenglamani (9.8.2) tenglamaning hadlari o'rniga qo'yamiz.

$$U_0 = \left( \frac{\sqrt{2}}{3} \angle 45^\circ \right) \left( \frac{\sqrt{2}}{3} \angle 45^\circ U_i \right) = \frac{1}{3} \angle 90^\circ U_i$$

Shunday qilib, chiqish kirishni  $90^\circ$  ga oldinda boradi, lekin uning kattaligi kirishning atigi 33 foizini tashkil qiladi.

### 9.8.2. AC ko‘priklar.


Induktor  $L$  ning induktivligini yoki kondansator  $C$  ning sig‘imini o‘lchashda o‘zgaruvchan tok ko‘prigi zanjiridan foydalaniladi.

U noma’lum qarshilikni o‘lchash uchun Wheatstone ko‘prigiga o‘xshash va xuddi shu prinsipga amal qiladi.

$L$  va  $C$  ni o‘lchash uchun galvanometr o‘rniga o‘zgaruvchan tok manbai va o‘zgaruvchan tok o‘lchagich kerak bo‘ladi.

O‘zgaruvchan tok o‘lchagich sezgir o‘zgaruvchan tok ampermetri yoki voltmetr bo‘lishi mumkin.

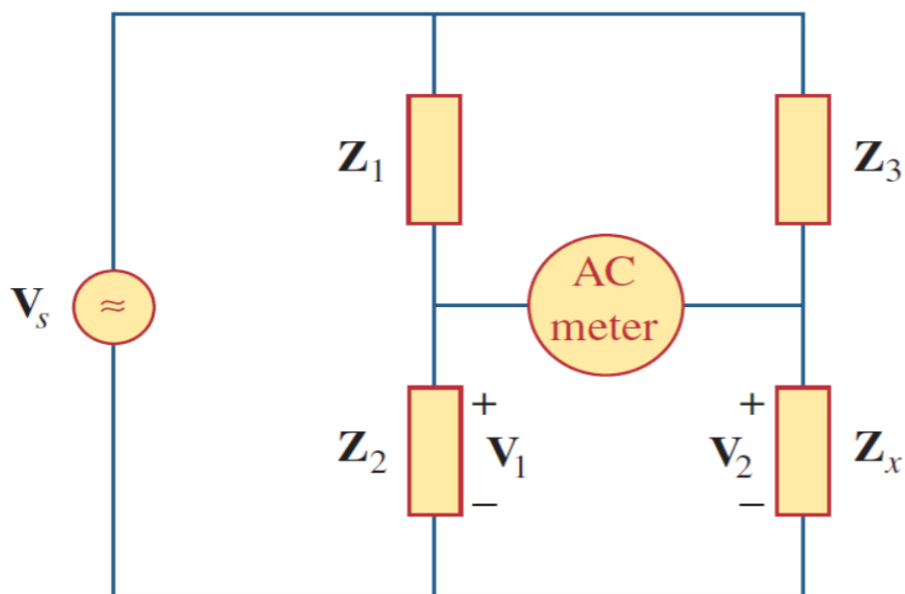9.26-rasmda ko‘rsatilgan umumiy o‘zgaruvchan tok ko‘prigi zanjirini ko‘rib chiqaylik. Hisoblagich orqali tok kuchi o‘tmasa, ko‘prik muvozanatlanadi. Bu shuni anglatadiki  $U_1 = U_2$ .



Kuchlanishni bo‘linish qoidasini qo‘llash,

$$U_1 = \frac{Z_2}{Z_1 + Z_2} U_s = U_2 = \frac{Z_x}{Z_3 + Z_x} U_s \quad (9.71)$$

Demak,

$$\frac{Z_2}{Z_1 + Z_2} = \frac{Z_x}{Z_3 + Z_x} \rightarrow Z_2 Z_3 = Z_1 Z_x \quad (9.72)$$

yoki,

$$Z_x = \frac{Z_3}{Z_1} Z_2 \quad (9.73)$$

### 9.26-rasm. Umumiy o‘zgaruvchan tok ko‘prigi.

Photo source: [22] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., - 2013. – p 399.

Bu o'zgaruvchan tok ko'prigi uchun muvozanatli tenglama bo'lib, qarshilik ko'prigi uchun tenglama (4.30) ga o'xshaydi, bundan tashqari  $R$  lar  $Z$  bilan almashtiriladi.

$$R_x = \frac{R_3}{R_1} R_2 \quad (4.30)$$


$L$  va  $C$  ni o'lchash uchun maxsus o'zgaruvchan ko'priklar 9.27-rasmda ko'rsatilgan, bu yerda  $L_x$  va  $C_x$  o'lchanadigan noma'lum induktiv va sig'im,  $L_s$  va  $C_s$  esa standart induktiv va sig'imdir (ularning qiymatlari katta aniqlik bilan ma'lum).

Har bir holatda, ikkita rezistor,  $R_1$  va  $R_2$  o'zgaruvchan tok o'lchagich nolga teng bo'lguncha o'zgaradi. Keyin ko'priklar muvozanatlanadi. (9.73) tenglamadan biz quyidagini olamiz.


$$L_x = \frac{R_2}{R_1} L_s \quad (9.74)$$

va
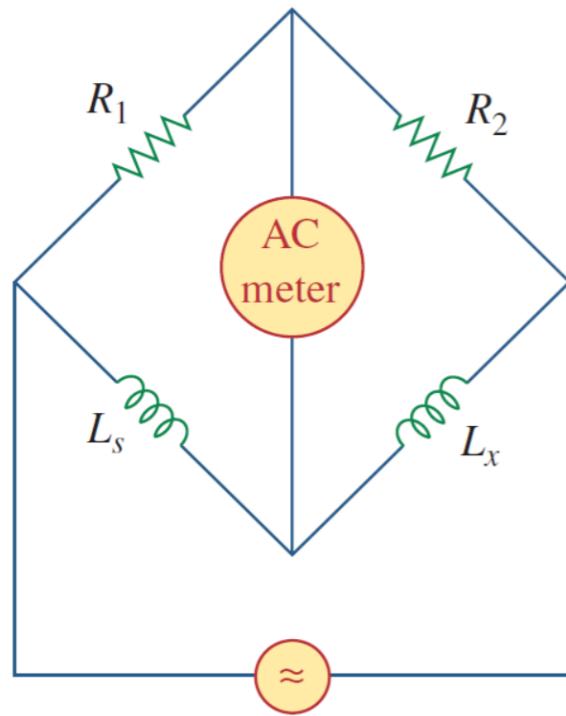
$$C_x = \frac{R_1}{R_2} L C_s \quad (9.75)$$



a) L o'lchash uchun;

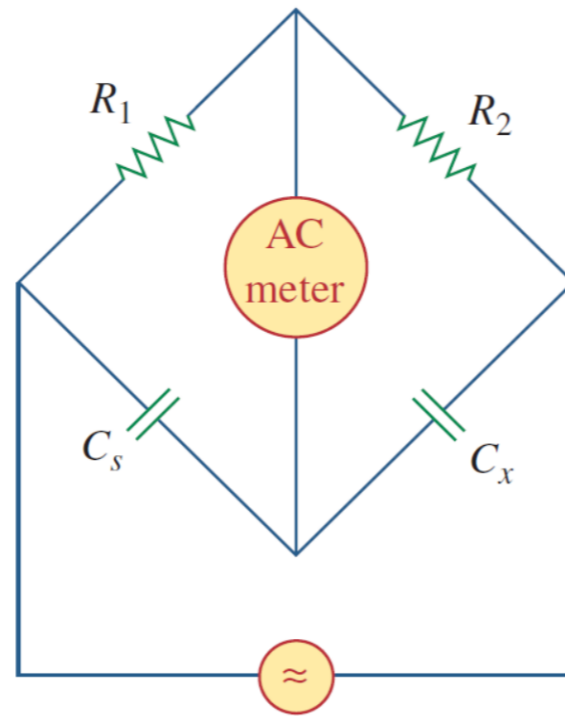

b) C o'lchash uchun.

9.27-rasmdagi o'zgaruvchan tok ko'priklarini muvozanatlash o'zgaruvchan tok manbasining  $f$  chastotasiga bog'liq emas, chunki  $f$  (9.74) va (9.75) tenglamalardagi munosabatlarda ko'rinmaydi.

**9.27-rasm. Maxsus o'zgaruvchan tok ko'prigi:**

Photo source: [22] -Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 399.

## ***FOYDALANILGAN MANBALAR:***

18. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 390.
19. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 391.
20. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 392.
21. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 396.
22. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 399.

# TEKSHIRISH UCHUN SAVOLLAR!

9.1. Quyidagilardan qaysi biri sinusoid  $A \cos \omega t$  ni ifodalashning to'g'ri usuli emas?

- A)  $A \cos 2\pi ft$ .                      B)  $A \cos(2\pi t/T)$ .  
 C)  $A \cos \omega(t - T)$ .                D)  $A \sin(\omega t - 90^\circ)$ .

9.2. Belgilangan oraliqlardan keyin takrorlanadigan funksiya deyiladi:

- A) faza.                      B) garmonik.                      C) davriy.                      D) reaktiv.

9.3. Ushbu chastotalarning qaysi birining davri qisqaroq?

- A) 1 krad/s.                      B) 1 kHz.

9.4. Agar  $u_1 = 30 \sin(\omega t + 10^\circ)$  va  $u_2 = 20 \sin(\omega t + 50^\circ)$  bo'lsa, ushbu bayonotlarning qaysi biri to'g'ri?

- A)  $u_1 u_2$  dan oldinda.                      A)  $u_2 u_1$  dan oldinda.  
 B)  $u_1 u_2$  dan ortda.                      C)  $u_2 u_1$  dan ortda.  
 D)  $u_1$  va  $u_2$  fazada.

9.5. Induktordagi kuchlanish tok kuchini  $90^\circ$  ga olib boradi.

- A) To'g'ri.                      B) Xato.

9.6 Impidansning hayoliy qismi deyiladi:


- A) resistance.                      B) admittance.  
 C) susceptance.                      D) conductance.                      E) reactance.

9.7 Kondensatorning empedansi chastotaning ortishi bilan ortadi.

- A) To'g'ri.                      B) Xato.

9.8. 9.28-rasmdagi chiqish kuchlanishi  $u_0(t)$  qaysi chastotada kirish kuchlanishiga  $u(t)$  teng bo'ladi?

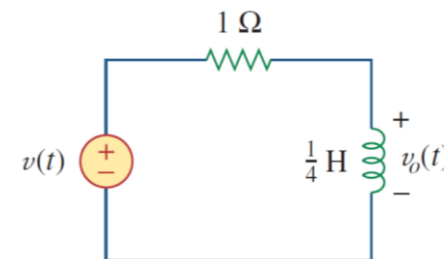- A) 0 rad/s.                      B) 1 rad/s.                      C) 4 rad/s.  
 D) rad/s.                      E) yuqoridagilarning hech biri.



9.28-rasm.

9.9. Ketma-ket RC zanjiri  $|U_R| = 12 V$  va  $|U_C| = 5 V$  ga ega. Ta'minot kuchlanishining kattaligi:

- A) -7 V.                      B) 7 V.                      C) 13 V.                      D) 17 V.

9.10. Ketma-ket RCL zanjiri  $R = 30 \Omega$ ,  $X_C = 50 \Omega$  va  $X_L = 90 \Omega$  ga ega. Zanjirning impedansi:

- A)  $30 + j140 \Omega$ .                      B)  $30 + j40 \Omega$ .  
 C)  $30 - j40 \Omega$ .                      D)  $-30 - j40 \Omega$ .  
 E)  $-30 + j40 \Omega$ .



*E'TIBORINGIZ  
UCHUN  
RAHMAT!!!*