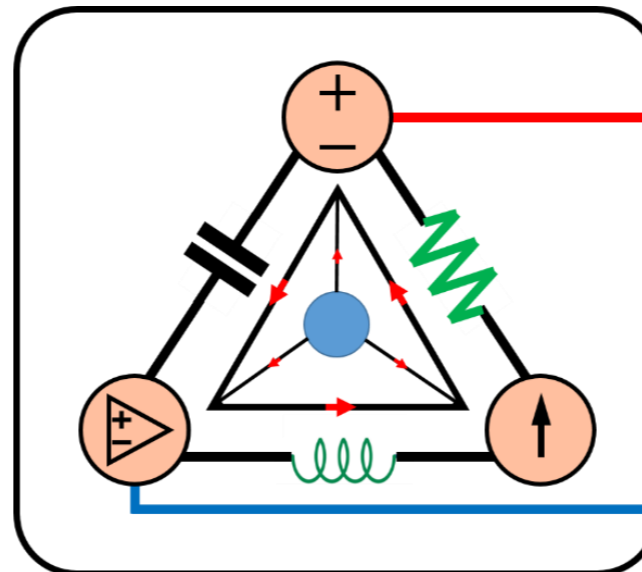


12-Mavzu: Uch fazali zanjirlar.
(12th Topic: Three-Phase Circuits.)

12-Mavzuning 2-qismi
(2nd part of the 12th Topic)

15-hafta uchun
For the 15th week



Lecturer: Ph.D., Yusupov Sarvarbek

Toshkent Kimyo Xalqaro Universiteti
“Mashinasozlik texnologiyasi” kafedrası
Toshkent shahri, Usmon Nosir, 156-uy.



12-Mavzu: Uch fazali zanjirlar.

(12th Topic: Three-Phase Circuits.)

O'quv rejasi:

12.1. Umumiy tushunchalar.

12.2. Muvozanatlangan uch fazali kuchlanishlar.

12.3. Muvozanatlangan yulduz-yulduz shakldagi (Y-Y) ulanish.

12.4. Muvozanatlangan yulduz-uchburchak shakldagi (Y- Δ) ulanish.

12.5. Muvozanatlangan uchburchak-uchburchak shakldagi (Δ - Δ) ulanish.

12.6. Muvozanatlangan uchburchak-yulduz shakldagi (Δ -Y) ulanish.

What are the 4 Types of 3 Phase Connections?

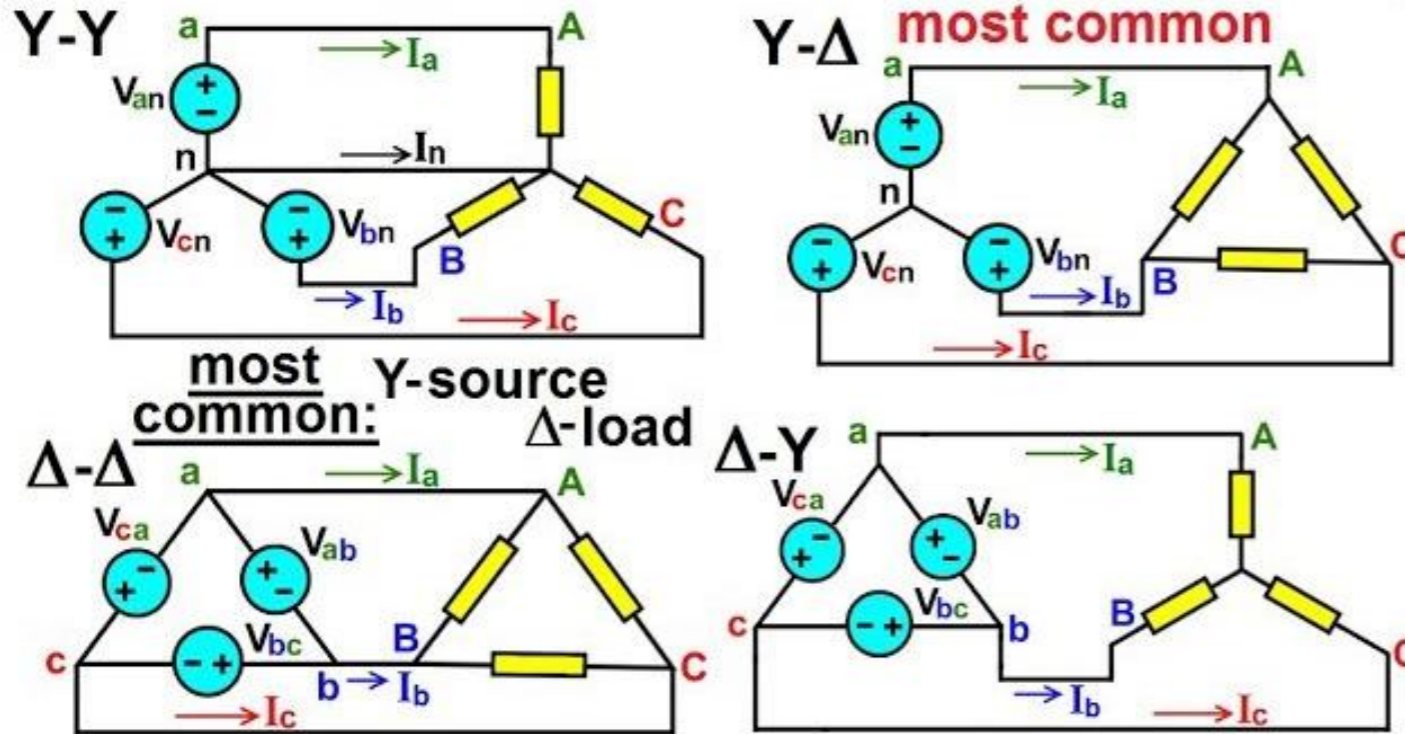


Photo source: [11] - <https://i.ytimg.com/vi/NdEqUfUiCBU/sddefault.jpg>

Determining the Line Voltage in a Y-Y System

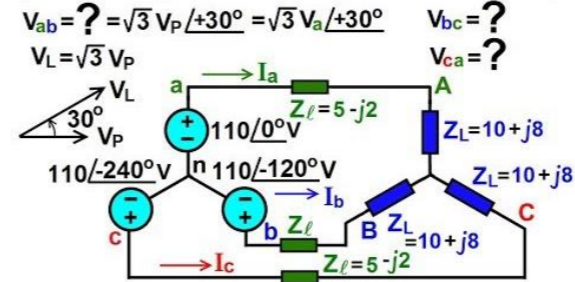


Photo source: [12] -

<https://i.ytimg.com/vi/84-oxotGYGM/hqdefault.jpg>

The Balanced Y-Δ Circuit

the current at the load: $I_{AB} = \frac{V_{AB}}{Z_{\Delta}}$ $I_{BC} = \frac{V_{BC}}{Z_{\Delta}}$ $I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$

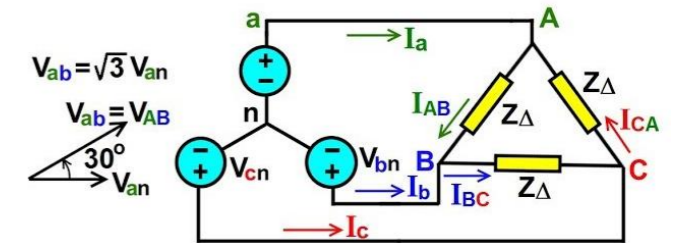


Photo source: [13] -

<https://i.ytimg.com/vi/4anR5Zcsx0Y/sddefault.jpg>

A Balanced Delta-Delta Circuit

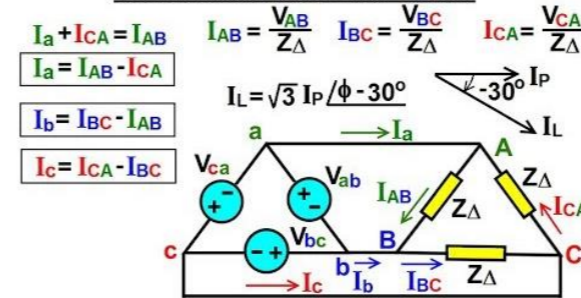


Photo source: [14] -

<https://i.ytimg.com/vi/XMpJullzM1M/hqdefault.jpg>

A Balanced Δ-Y Circuit: How to Obtain the Line Currents using Kirchoff's rule:


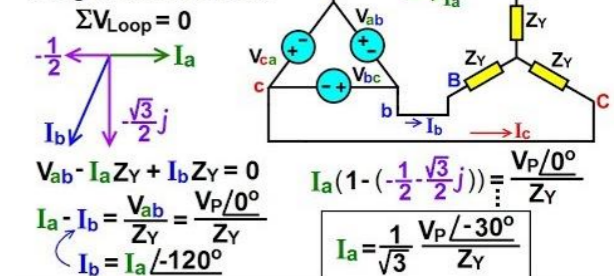


Photo source: [15] -

<https://i.ytimg.com/vi/nd-O1ifRhpl/hqdefault.jpg>

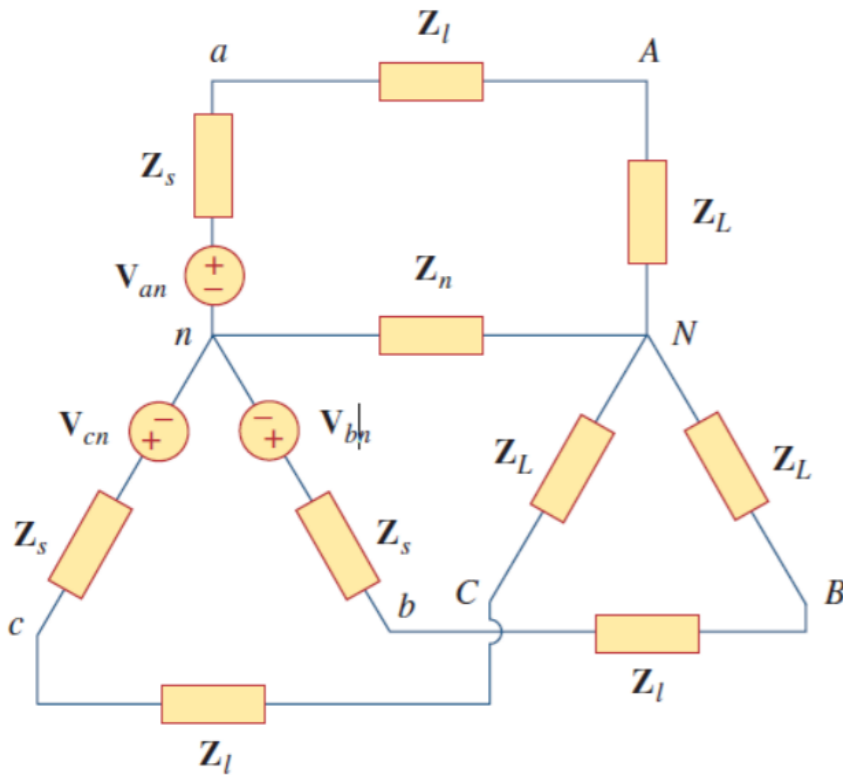12.3. Muvozanatlangan yulduz-yulduz shakldagi (Y-Y) ulanish.

Har qanday muvozanatli uch fazali tizim ekvivalenti qarshiliklari yulduz shaklida ulangan (Y-Y) tizimiga qisqartirilishi mumkin. Shu sababli, ushbu tizimni tahlil qilish barcha muvozanatlangan uch fazali tizimlarni hal qilish imkonini beradi.



12.10-rasm. Manba, tarmoq va yuklama impedenslarini ko'rsatadigan muvozanatlangan Y-Y tizim.

Muvozanatlangan Y-Y tizimi – bu muvozanatli yulduz shaklida ulangan manba va muvozanatli yulduz shaklida ulangan yuklamadan iborat tizimdir.

$$Z_Y = Z_s + Z_\ell + Z_L$$


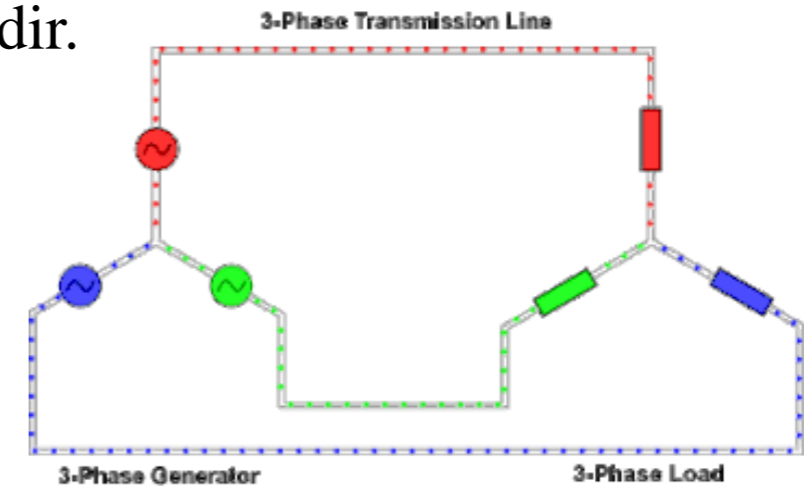


Photo source: [16] - https://upload.wikimedia.org/wikipedia/commons/thumb/4/48/3-phase_flow.gif/357px-3-phase_flow.gif

Z_S va Z_L ko‘pincha Z_L bilan solishtirganda juda kichikdir, shuning uchun hech qanday manba yoki tarmoq impedansi berilmasa $Z_Y = Z_L$ deb taxmin qilish mumkin.

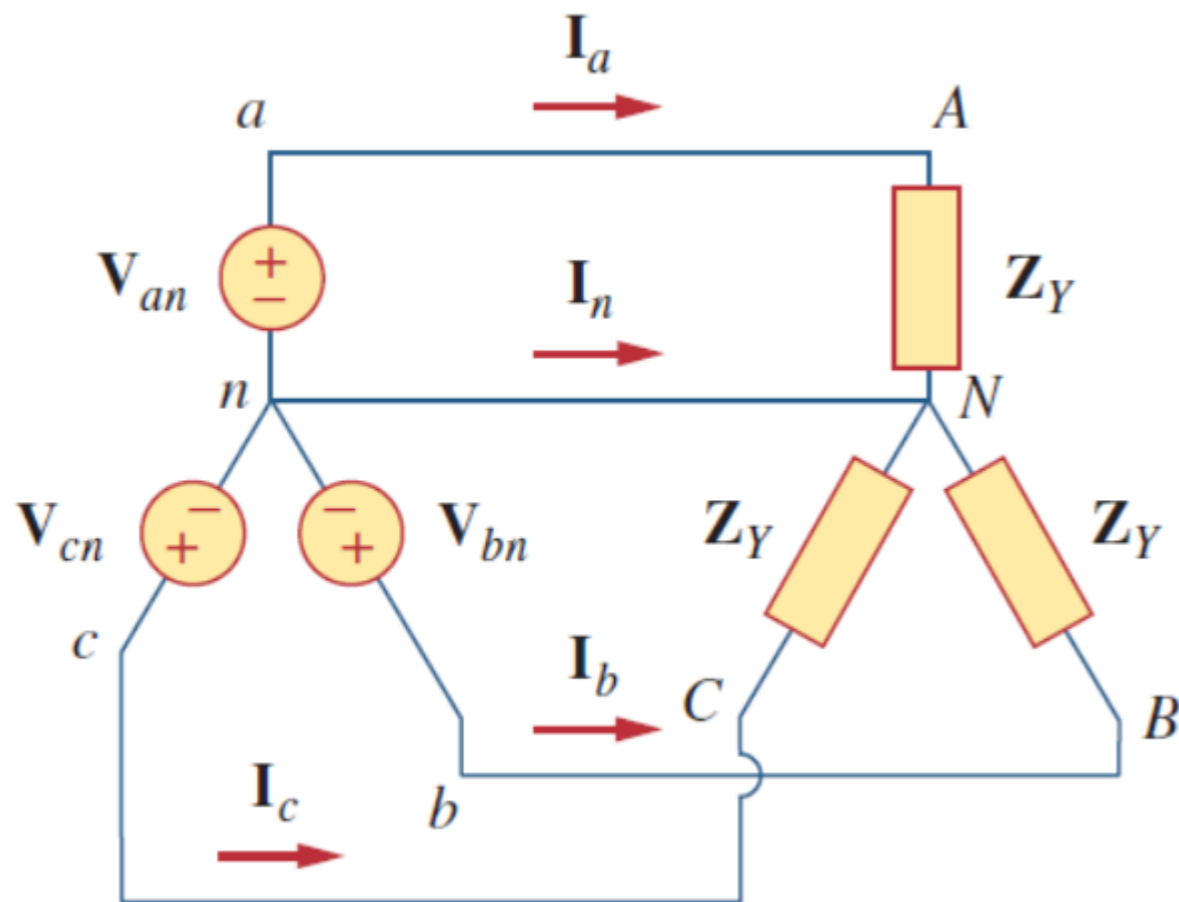Har qanday holatda, impedenslarni birlashtirib, 12.10-rasmdagi Y-Y tizimini 12.11-rasmda ko‘rsatilgandek soddalashtirish mumkin.



$$\begin{aligned}
 V_{an} &= V_p \angle 0^\circ \\
 V_{bn} &= V_p \angle -120^\circ, & V_{cn} &= V_p \angle +120^\circ
 \end{aligned}$$

12.11-rasm. Muvozanatlangan Y-Y shaklida ulanish.

Tarmoq kuchlanish U_{ab} , U_{bc} va U_{ca} faza kuchlanishlari bilan bog‘liq.

$$\begin{aligned}
 \mathbf{V}_{ab} &= \mathbf{V}_{an} + \mathbf{V}_{nb} = \mathbf{V}_{an} - \mathbf{V}_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\
 &= V_p \left(1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ \\
 \mathbf{V}_{bc} &= \mathbf{V}_{bn} - \mathbf{V}_{cn} = \sqrt{3} V_p \angle -90^\circ \\
 \mathbf{V}_{ca} &= \mathbf{V}_{cn} - \mathbf{V}_{an} = \sqrt{3} V_p \angle -210^\circ
 \end{aligned}$$

Shunday qilib, tarmoq kuchlanishlarining kattaligi U_L faza kuchlanishi U_p ning qiymatidan $\sqrt{3}$ barobar kattadir.


$$V_L = \sqrt{3} V_p$$

$$V_L = |\mathbf{V}_{ab}| = |\mathbf{V}_{bc}| = |\mathbf{V}_{ca}| \qquad V_p = |\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$$

Bundan tashqari, tarmoq kuchlanishlari mos keladigan faza kuchlanishlaridan 30° ga ilgarilaydi.

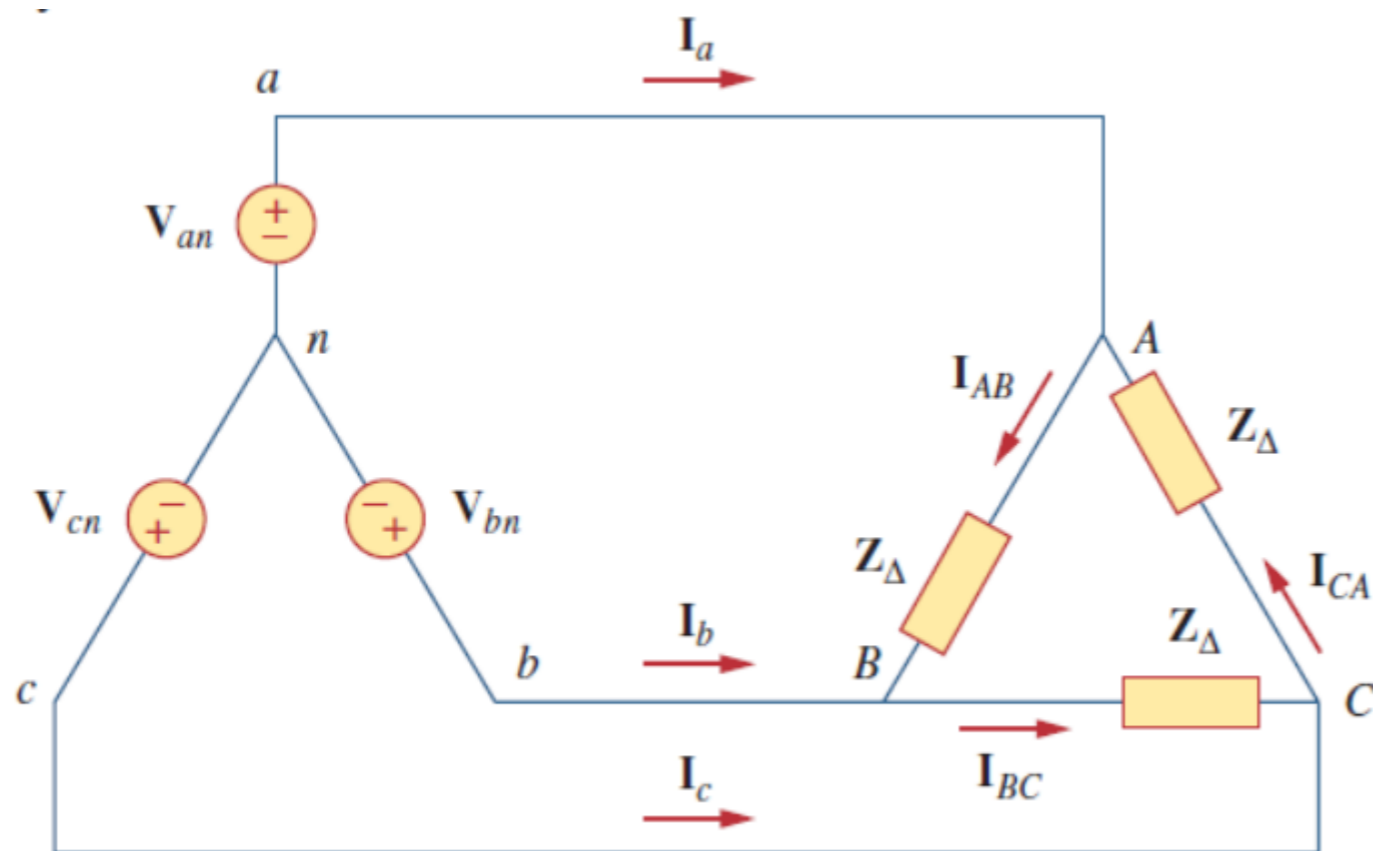12.4. Muvozanatlangan yulduz-uchburchak shakldagi (Y- Δ) ulanish.

Muvozanatlangan yulduz-uchburchak tizimi muvozanatli uchburchak shaklida ulangan yuklamani ta'minlaydigan muvozanatli yulduz shaklida ulangan manbadan iborat.



Muvozanatlangan yulduz-uchburchak tizimi 12.12-rasmda ko'rsatilgan.

Bu yerda manba “yulduz” sxemasiga muvofiq, yuklama esa “uchburchak” sxema bo'yicha ulanadi.

Albatta, bu holda manbadan yuklamaga neytral aloqa yo'q.

12.12-rasm. Muvozanatlangan Y- Δ shaklida ulanish.

Ijobiy ketma-ketlikni hisobga olib, faza kuchlanishlari:

$$\begin{aligned} \mathbf{V}_{an} &= V_p \angle 0^\circ \\ \mathbf{V}_{bn} &= V_p \angle -120^\circ, & \mathbf{V}_{cn} &= V_p \angle +120^\circ \end{aligned}$$

Tarmoq kuchlanishlari:

$$\begin{aligned} \mathbf{V}_{ab} &= \sqrt{3}V_p \angle 30^\circ = \mathbf{V}_{AB}, & \mathbf{V}_{bc} &= \sqrt{3}V_p \angle -90^\circ = \mathbf{V}_{BC} \\ \mathbf{V}_{ca} &= \sqrt{3}V_p \angle -150^\circ = \mathbf{V}_{CA} \end{aligned}$$

Tarmoq kuchlanishlari ushbu tizim konfiguratsiyasi uchun yuklama impedenslaridagi kuchlanishlarga teng ekanligini ko'rsatadi. Ushbu kuchlanishlardan biz fazali toklarni olishimiz mumkin. Ya'ni,

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_\Delta}, \quad \mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_\Delta}$$

Bu toklar bir xil kattalikka ega, lekin bir-biridan 120° fazadan farqlanadi.

Tarmoq toklari A, B va C tugunlarida KCLni qo‘llash orqali faza toklardan olinadi.

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$

Shuning bilan $\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle -240^\circ$,

$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB}(1 - 1 \angle -240^\circ) \\ &= \mathbf{I}_{AB}(1 + 0.5 - j0.866) = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ \end{aligned}$$

Shunday qilib, tarmoq toklarining kattaligi I_L faza toki I_p ning qiymatidan $\sqrt{3}$ barobar kattadir.

$$I_L = \sqrt{3}I_p$$

$$I_L = |\mathbf{I}_a| = |\mathbf{I}_b| = |\mathbf{I}_c|$$


$$I_p = |\mathbf{I}_{AB}| = |\mathbf{I}_{BC}| = |\mathbf{I}_{CA}|$$

$$\mathbf{Z}_Y = \frac{\mathbf{Z}_\Delta}{3}$$

Bundan tashqari, tarmoq toklar mos keladigan faza toklaridan 30° ga kechikadi.

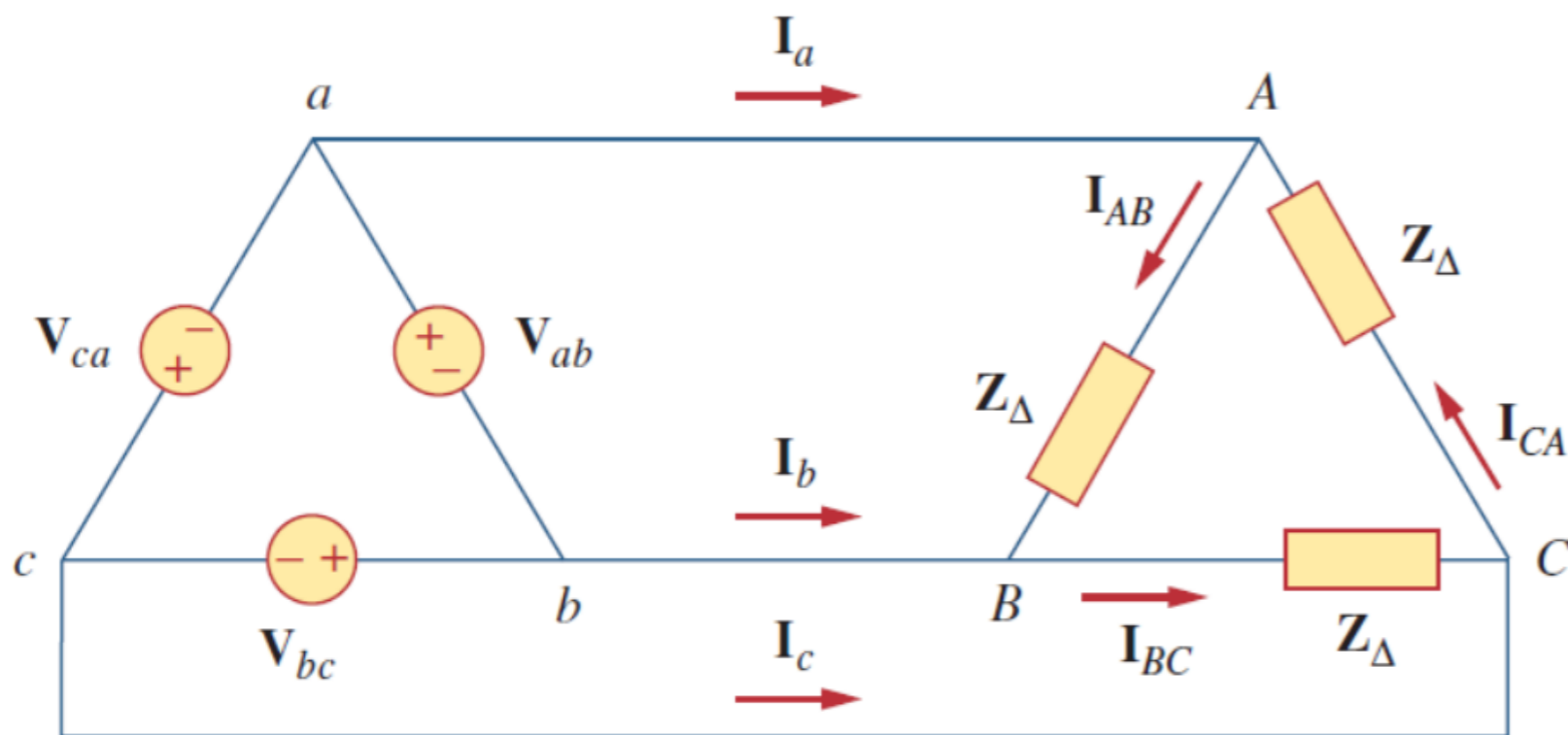12.5. Muvozanatlangan uchburchak-uchburchak shakldagi (Δ - Δ) ulanish.

Muvozanatlangan uchburchak-uchburchak tizimi - bu muvozanatlangan har ikkala manba va yuklamalar uchburchak shaklida ulangan bo‘ladi.



Ijobiy ketma-ketlikni nazarda tutsak, uchburchak shaklida ulangan manba uchun faza kuchlanishlari:

$$V_{bc} = V_p \angle -120^\circ, \quad V_{ab} = V_p \angle 0^\circ, \quad V_{ca} = V_p \angle +120^\circ$$

12.13-rasm. Muvozanatlangan Δ - Δ shaklda ulanish.

Tarmoq kuchlanishlari faza kuchlanishlari bilan bir xil. 12.13-rasmdan tarmoq impedenslar yo‘q deb hisoblasak, uchburchak shaklida ulangan manbaning fazali kuchlanishlari impedenslardagi kuchlanishlarga teng.

$$\mathbf{V}_{ab} = \mathbf{V}_{AB}, \quad \mathbf{V}_{bc} = \mathbf{V}_{BC}, \quad \mathbf{V}_{ca} = \mathbf{V}_{CA}$$

Demak, faza toklari

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{Z_{\Delta}} = \frac{\mathbf{V}_{ab}}{Z_{\Delta}}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{Z_{\Delta}} = \frac{\mathbf{V}_{bc}}{Z_{\Delta}}$$
$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{Z_{\Delta}} = \frac{\mathbf{V}_{ca}}{Z_{\Delta}}$$

Yuklama uchburchak shaklida ulanganligi sababli, u yerda olingan ba'zi ifodalar bu yerda qo'llaniladi.

Tarmoq toklari A, B va C tugunlarida KCLni qo'llash orqali faza toklaridan olinadi:

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$

Har bir tarmoq toki mos keladigan faza tokidan 30° ga orqada qoladi.


Tarmoq tokining kattaligi I_L faza toki I_p ning qiymatidan $\sqrt{3}$ barobar kattadir.

$$I_L = \sqrt{3}I_p$$

Δ - Δ shaklida sxemani tahlil qilishning muqobil usuli ham manbani, ham yuklamani ularning Y ekvivalentlariga aylantirishdan iborat.

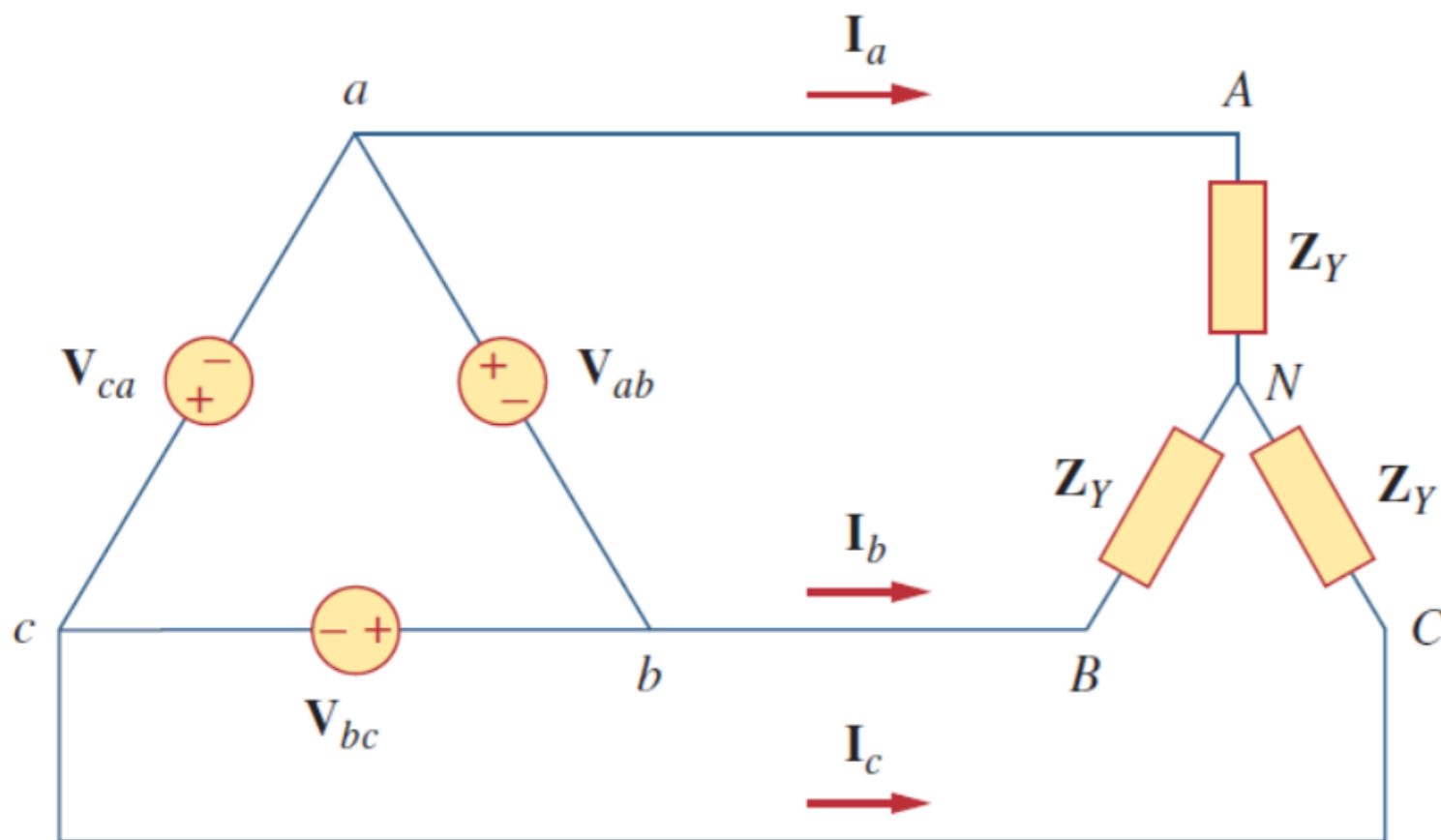12.6. Muvozanatlangan uchburchak-yulduz shakldagi (Δ -Y) ulanish.

Muvozanatlangan uchburchak-yulduz tizimi – bu muvozanatli yulduz shaklida ulangan yuklamani ta’minlovchi muvozanatli uchburchak shaklida ulangan manbadan iborat.



abc ketma-ketligini hisobga olsak, uchburchak bilan bog‘langan manbaning fazali kuchlanishlari:

$$\begin{aligned} V_{ab} &= V_p \angle 0^\circ, & V_{bc} &= V_p \angle -120^\circ \\ V_{ca} &= V_p \angle +120^\circ \end{aligned}$$

12.14-rasm. Muvozanatlangan Δ -Y shaklda ulanish.

Shuningdek, tarmoq (liniya) kuchlanishlari faza kuchlanishlari bilan bir xil.

Tarmoq toklarini ko‘p usullar bilan olishimiz mumkin.

$aANBba$ kontur uchun KVL ni qo‘llaymiz.

$$-V_{ab} + Z_Y I_a - Z_Y I_b = 0 \quad \text{yoki,} \quad Z_Y(I_a - I_b) = V_{ab} = V_p \angle 0^\circ$$

Demak,

$$I_a - I_b = \frac{V_p \angle 0^\circ}{Z_Y}$$

Lekin I_b I_a dan 120° ga orqada qoladi, chunki abc ketma-ketlida deb hisobga qildik.

Ya’ni $I_b = I_a \angle -120^\circ$. Demak,

$$\begin{aligned} I_a - I_b &= I_a(1 - 1 \angle -120^\circ) \\ &= I_a \left(1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = I_a \sqrt{3} \angle 30^\circ \end{aligned} \quad \longrightarrow \quad I_a = \frac{V_p / \sqrt{3} \angle -30^\circ}{Z_Y}$$

Bu yerdan biz to'g'ridan-to'g'ri fazalar ketma-ketligidan foydalanib, I_b va I_c gachasi boshqa tarmoq toklarini olamiz, ya'ni $I_b = I_a \angle - 120^\circ$, $I_c = I_a \angle + 120^\circ$.

Faza toklari tarmoq toklariga teng.


Uchburchak shaklida ulangan manbani uning ekvivalent yulduz shaklida ulangan manba bilan almashtirish mumkin.

Shuning uchun, biz uchburchak shaklida ulangan manbaning mos keladigan tarmoqli kuchlanishini $\sqrt{3}$ ga bo'lish va uning fazasini -30° ga almashtirish orqali ekvivalent Y bog'langan manbaning har bir fazali kuchlanishini olamiz.

Muvozanatlangan uch fazali tizimlar uchun faza va

tarmoq kuchlanish / toklarining qisqacha mazmuni*.

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p / 0^\circ$ $V_{bn} = V_p / -120^\circ$ $V_{cn} = V_p / +120^\circ$ Same as line currents	$V_{ab} = \sqrt{3} V_p / 30^\circ$ $V_{bc} = V_{ab} / -120^\circ$ $V_{ca} = V_{ab} / +120^\circ$ $I_a = V_{an} / Z_Y$ $I_b = I_a / -120^\circ$ $I_c = I_a / +120^\circ$
Y-Δ	$V_{an} = V_p / 0^\circ$ $V_{bn} = V_p / -120^\circ$ $V_{cn} = V_p / +120^\circ$ $I_{AB} = V_{AB} / Z_\Delta$ $I_{BC} = V_{BC} / Z_\Delta$ $I_{CA} = V_{CA} / Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3} V_p / 30^\circ$ $V_{bc} = V_{BC} = V_{ab} / -120^\circ$ $V_{ca} = V_{CA} = V_{ab} / +120^\circ$ $I_a = I_{AB} \sqrt{3} / -30^\circ$ $I_b = I_a / -120^\circ$ $I_c = I_a / +120^\circ$
Δ-Δ	$V_{ab} = V_p / 0^\circ$ $V_{bc} = V_p / -120^\circ$ $V_{ca} = V_p / +120^\circ$ $I_{AB} = V_{ab} / Z_\Delta$ $I_{BC} = V_{bc} / Z_\Delta$ $I_{CA} = V_{ca} / Z_\Delta$	Same as phase voltages $I_a = I_{AB} \sqrt{3} / -30^\circ$ $I_b = I_a / -120^\circ$ $I_c = I_a / +120^\circ$
Δ-Y	$V_{ab} = V_p / 0^\circ$ $V_{bc} = V_p / -120^\circ$ $V_{ca} = V_p / +120^\circ$ Same as line currents	Same as phase voltages $I_a = \frac{V_p / -30^\circ}{\sqrt{3} Z_Y}$ $I_b = I_a / -120^\circ$ $I_c = I_a / +120^\circ$

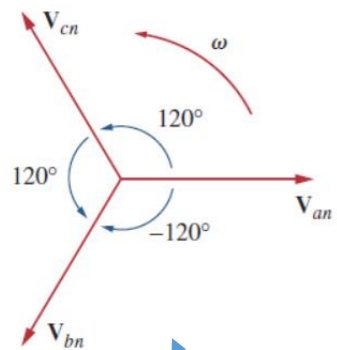

Shunday qilib, ekvivalent Y-ulangan manba fazali kuchlanishlarga ega:

$$V_{an} = \frac{V_p}{\sqrt{3}} \angle -30^\circ$$

$$V_{bn} = \frac{V_p}{\sqrt{3}} \angle -150^\circ, \quad V_{cn} = \frac{V_p}{\sqrt{3}} \angle +90^\circ$$

*Ijobiy yoki *abc* ketma-ketligi qabul qilinadi.

Photo source: [17] - Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 518.

FOYDALANILGAN MANBALAR:

1. <https://i.ytimg.com/vi/NdEqUfUiCBU/sddefault.jpg>
2. <https://i.ytimg.com/vi/84-oxotGYGM/hqdefault.jpg>
3. <https://i.ytimg.com/vi/4anR5Zcsx0Y/sddefault.jpg>
4. <https://i.ytimg.com/vi/XMpJuIzM1M/hqdefault.jpg>
5. <https://i.ytimg.com/vi/nd-O1ifRhpI/hqdefault.jpg>
6. https://upload.wikimedia.org/wikipedia/commons/thumb/4/48/3-phase_flow.gif/357px-3-phase_flow.gif
7. Fundamentals of Electric Circuits, Charles K. Alexander and Matthew N. O. Sadiku / 5th edition, the McGraw-Hill Companies, Inc., -2013. – p 518.



*E'TIBORINGIZ
UCHUN
RAHMAT!!!*