

# **Course: Automatic Control System Technology**

**Lecture 5: Model electrical systems**

**Lecturer: UWASEKURU GISA Jean De Dieu**

# Model electrical systems

## Session objectives:

**By the end of this session, students will be able to :**

- ❖ Define modeling a system
- ❖ Model passive electrical elements
- ❖ Model Electrical networks

# Define modeling a system

- ❖ Modeling a system means to find a mathematical or graphical representation of a system.
- ❖ A system may have a mathematical or graphical representation/model.

# Define modeling a system

- ❖ A mathematical model of a dynamic system is a set of equations that represents the dynamics of the system accurately.
- ❖ A graphical model of a system is a visual or pictorial representation of functions performed by each system component

# Define modeling a system

- ❖ A control system can mathematically be represented by a *differential equation, transfer function* or *state space equation*.

Farid Golnaraghi & Benjamin C. Kuo (2010), Automatic Control Systems, 9<sup>th</sup> Edition, John Wiley&Sons, page 147.

- ❖ A control system can graphically be represented **by a block diagram or a signal flow graph**.

# Define modeling a system

- ❖ System models are useful for analysis and design of control systems.
- ✓ **The analysis of control system** means *finding the output* when *we know the input* and *mathematical model*.
- ✓ **Design of control system** means *finding the mathematical model* when we know *the input and the output*.

# Define modeling a system


- ❖ In this lecture, we will focus on **determining differential equation models** of electrical networks with simple passive elements such as resistors, inductors, and capacitors.
- ❖ Differential equation model is a time domain mathematical model of control system.

# Define modeling a system

- ❖ Other system models such as transfer function model, block diagram model, signal flow graph model and state space model will be taught in other lectures

# Model passive electrical elements

- ❖ The basic passive electrical elements: resistors, inductors, and capacitors.

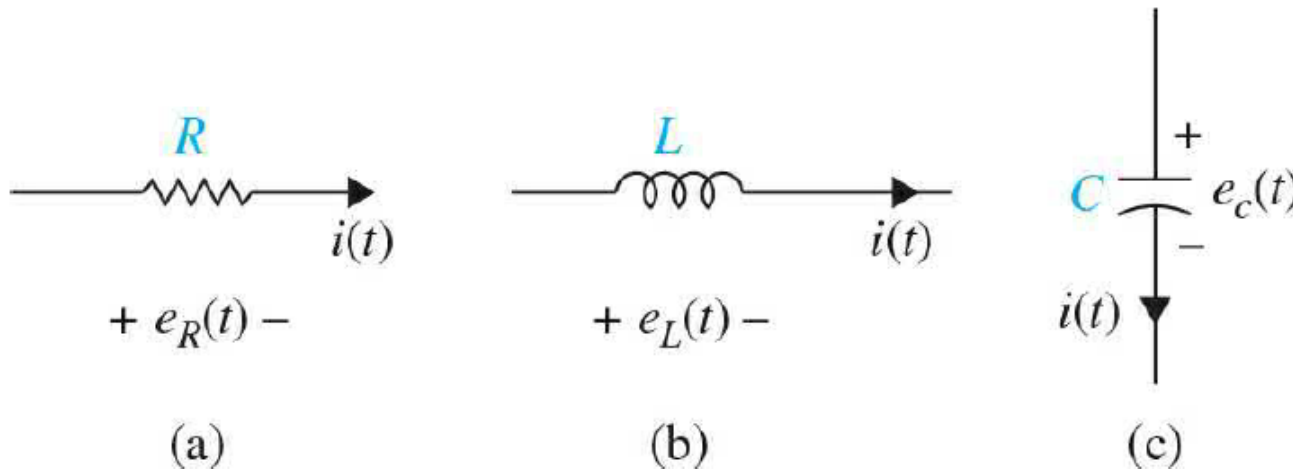

**Figure 1.** Basic passive electrical elements.  
(a) A resistor, (b) An inductor, (c) A capacitor

Farid Golnaraghi & Benjamin C. Kuo (2019), Automatic Control Systems, 10<sup>th</sup> Edition, McGraw-Hill Education, page 103.

# Model passive electrical elements

- ❖ *Resistors*. Ohm's law states that the voltage drop,  $e_R(t)$ , across a resistor  $R$  is proportional to the current  $i(t)$  going through the resistor.

$$e_R(t) = Ri(t)$$

# Model passive electrical elements

❖ *Inductors*. The voltage drop,  $e_L(t)$ , across an inductor  $L$  is proportional to the variation of current  $i(t)$  going through the inductor with respect to time. Thus,

$$e_L(t) = L \frac{di(t)}{dt}$$

# Model passive electrical elements

❖ *Capacitor.* The voltage drop,  $e_C(t)$ , across a capacitor  $C$  is proportional to the integral of current  $i(t)$  going through the capacitor with respect to time. Therefore:

$$e_C(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$$

# Model passive electrical elements

- ❖ By differentiating both sides of this equation representing the voltage drop across the capacitor , we get the current in the capacitor because the derivative is the inverse of integral.

$$\frac{de_c(t)}{dt} = \frac{1}{C} i(t) , \text{ which gives } i(t) = C \frac{de_c(t)}{dt}$$

# Model Electrical networks

- ❖ Follow these two steps to find a differential equation model of electrical networks
  - ✓ *Apply Kirchhoff's laws to electrical circuit.*
  - ✓ Get the differential equation in terms of *input and output* by eliminating the *intermediate variable(s)*

# Model Electrical networks


❖ Kirchhoff's laws state:

✓ *Current law* : The algebraic summation of all currents entering a node is zero.

✓ *Voltage law* : The algebraic sum of all voltage drops around a complete closed loop is zero.

# Model Electrical networks

**Example 1:** Consider the RLC network shown in the figure 2. Find the differential equation of the system. The **output** is the **voltage**  $e_c(t)$  across the capacitor.

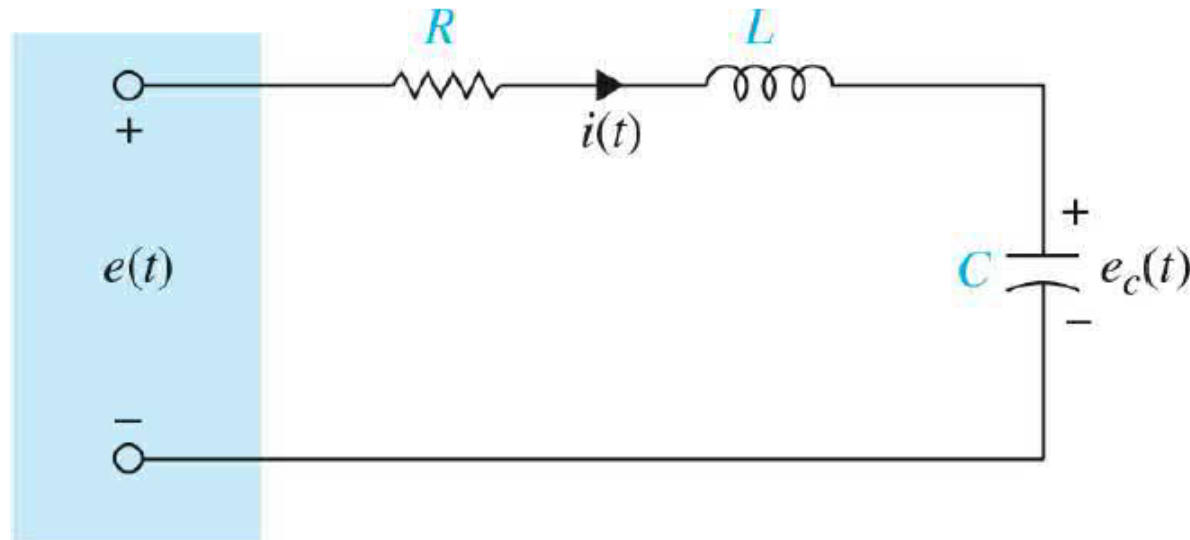

**Figure 2.** RLC circuit

Farid Golnaraghi & Benjamin C. Kuo (2019), Automatic Control Systems, 10<sup>th</sup> Edition, McGraw-Hill Education, page 104.

# Model Electrical networks

- ❖ Applying Kirchhoff's voltage law to the RLC circuit shown in figure 2, we get:

$$e(t) = e_R(t) + e_L(t) + e_C(t)$$

where  $e_R(t) = Ri(t)$  , and  $e_L(t) = L \frac{di(t)}{dt}$

- ❖ Hence, we have:

$$e(t) = Ri(t) + L \frac{di(t)}{dt} + e_C(t) \text{ ----- eq1}$$

# Model Electrical networks

❖ **Note:**  $e(t)$  and  $e_C(t)$  are respectively input and output voltage.

Thus, the differential equation of the RLC circuit will be expressed in terms of those variables only. The current  $i(t)$  is the intermediate variable and has to be eliminated from the differential equation.

❖ The voltage  $e_C(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$  and hence the current in the

capacitor is  $i(t) = C \frac{de_C(t)}{dt}$

# Model Electrical networks

- ❖ By substituting the current  $i(t)$  in the eq1, we get the differential equation of the RLC network:


$$e(t) = R_c \frac{de_c(t)}{dt} + LC \frac{d^2 e_c(t)}{dt^2} + e_c(t)$$

- ❖ This equation can be rearranged from the highest derivative of the output as follows:

$$LC \frac{d^2 e_c(t)}{dt^2} + R_c \frac{de_c(t)}{dt} + e_c(t) = e(t)$$

# Model Electrical networks

**Example 2:** Consider the RC circuit shown in figure 3. Find the differential equation of the system. The **output** is the **voltage  $e_C(t)$  across the capacitor.**

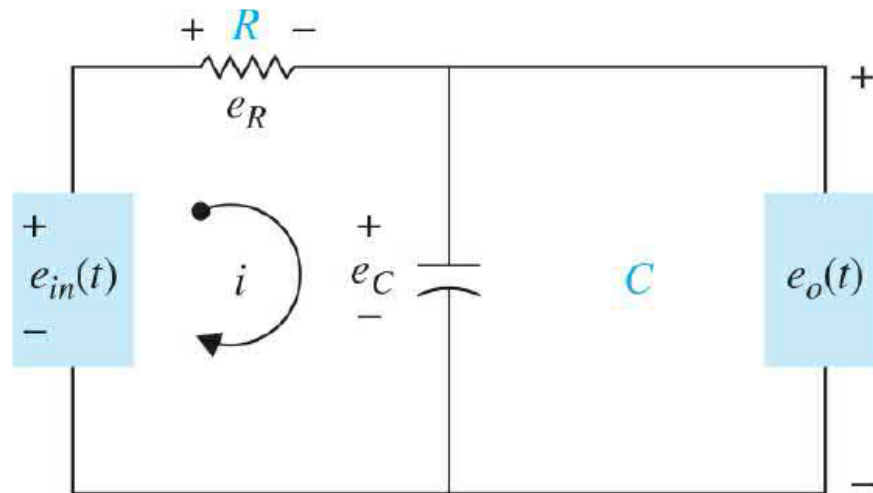

**Figure 3.** RC circuit

Farid Golnaraghi & Benjamin C. Kuo (2019), Automatic Control Systems, 10<sup>th</sup> Edition, McGraw-Hill Education, page 106.

# Model Electrical networks

- ❖ Applying Kirchhoff's voltage law to the RC circuit shown in figure 3, we get:

$$e_{in}(t) = e_R(t) + e_C(t)$$

$$\text{where } e_R(t) = Ri(t)$$

- ❖ Hence, we have:

$$e_{in}(t) = Ri(t) + e_C(t) \text{ ---- eq2}$$

# Model Electrical networks

- ❖ From the figure 3., the output voltage  $e_c(t) = e_o(t)$  and then, the current in the capacitor is  $i(t) = C \frac{de_c(t)}{dt} = C \frac{de_o(t)}{dt}$  and by substituting these variables in the equation eq2, we find the differential equation of RC network:


$$e_{in}(t) = RC \frac{de_o(t)}{dt} + e_o(t)$$

- ❖ This equation can be rearranged from the highest derivative of the output as follows:

$$RC \frac{de_o(t)}{dt} + e_o(t) = e_{in}(t)$$

# Model Electrical networks

**Example 3:** Consider the RC circuit shown in figure 4. Find the differential equation of the system. The **output** is the **voltage  $e_R(t)$  across the Resistor**.

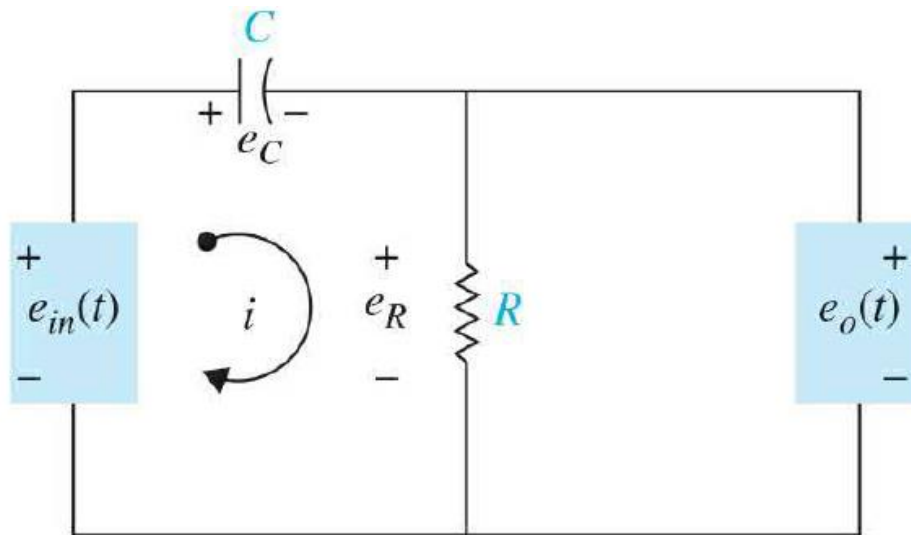

**Figure 4.** RC circuit

Farid Golnaraghi & Benjamin C. Kuo (2019), Automatic Control Systems, 10<sup>th</sup> Edition, McGraw-Hill Education, page 108.

# Model Electrical networks

- ❖ Again, by applying Kirchhoff's voltage law to the RC circuit shown in figure 4, we get:

$$e_{in}(t) = e_C(t) + e_R(t)$$

With:  $e_R(t) = e_o(t)$ , and  $e_C(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$

- ❖ Hence, we have:

$$e_{in}(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + e_o(t) \text{ ---- eq3}$$

# Model Electrical networks

❖ The output voltage  $e_R(t) = Ri(t) = e_o(t)$ ,

$$\text{and } i(t) = \frac{e_R(t)}{R} = \frac{e_o(t)}{R}$$

❖ By substituting the current  $i(t)$  in the eq3, we get the differential equation of the RC network with the output take across the resistor:

$$e_{in}(t) = \frac{1}{C} \int_0^t \frac{e_o(\tau)}{R} d\tau + e_o(t)$$

# Model Electrical networks

❖ Rearranging the previous equation, we get:

$$e_{in}(t) = \frac{1}{RC} \int_0^t e_o(\tau) d\tau + e_o(t) \text{ ----eq4}$$

❖ To solve this equation, we can differentiate it with respect to time:


$$\dot{e}_{in}(t) = \frac{1}{RC} e_o(t) + \dot{e}_o(t)$$

❖ This equation can be written from the highest derivative of the output as follows:

$$\dot{e}_o(t) + \frac{1}{RC} e_o(t) = \dot{e}_{in}(t)$$

# Model Electrical networks

**Example 4:** Consider the voltage divider shown in figure 5. Find the mathematical model of the system. The **output** is the **voltage  $e_{R_2}(t)$**  across the resistor  $R_2$  .

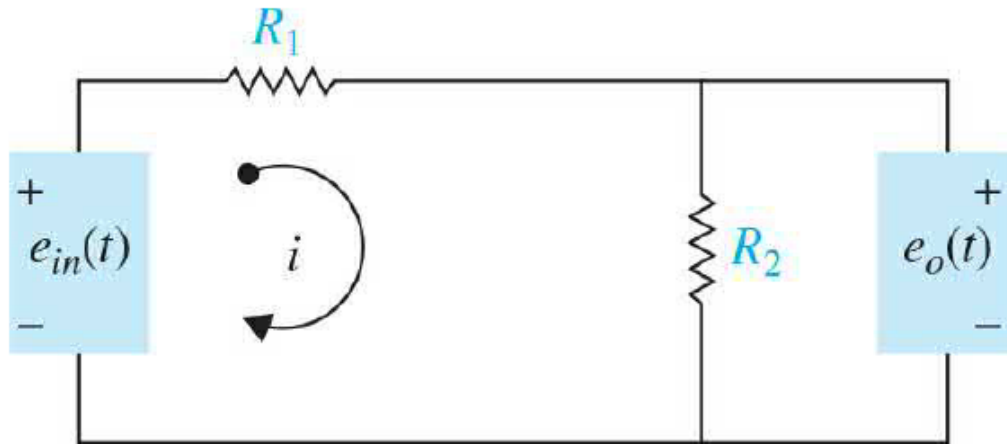

**Figure 5.** A voltage divider

Farid Golnaraghi & Benjamin C. Kuo (2019), Automatic Control Systems, 10<sup>th</sup> Edition, McGraw-Hill Education, page 109.

# Model Electrical networks

❖ From figure 5, we can write:

$$e_{in}(t) = e_{R_1}(t) + e_{R_2}(t)$$

where  $e_{R_2}(t) = e_o(t)$ , and  $e_{R_1}(t) = R_1 i(t)$

❖ Hence, we have:

$$e_{in}(t) = R_1 i(t) + e_o(t) \text{-----eq4}$$

❖ The current  $i(t)$  through the resistor  $R_2$  is the intermediate variable and it has to be eliminated from the above equation.

# Model Electrical networks

❖ From the figure 5, it is clear that  $e_{R_2}(t) = e_o(t) = R_2 i(t)$ ,

hence  $i(t) = \frac{e_o(t)}{R_2}$ .

❖ Substituting  $i(t) = \frac{e_o(t)}{R_2}$  in the equation eq4, we get:

$$e_{in}(t) = R_1 \frac{e_o(t)}{R_2} + e_o(t)$$

# Model Electrical networks

- ❖ Rearranging the previous equation gives the following equation for voltage divider:

$$e_{in}(t) = \left( \frac{R_1}{R_2} + 1 \right) e_o(t)$$

$$e_o(t) = \frac{R_1}{R_1 + R_1} e_{in}(t)$$

# References

1. Farid Golnaraghi & Benjamin C. Kuo (2019), Automatic Control Systems, 10<sup>th</sup> Edition, McGraw-Hill Education
2. Farid Golnaraghi & Benjamin C. Kuo (2010), Automatic Control Systems, 9<sup>th</sup> Edition, John Wiley&Sons

**THANK YOU**